

EDN

THE DESIGN MAGAZINE OF THE ELECTRONICS INDUSTRY

COVER STORY

ASIC TEST: IT'S A NEW BALL GAME

PG 24

SEPTEMBER 29, 1994

Out in Front pg 11


Drive amplifiers
for ADCs pg 53

Data-acquisition software development pg 63

Design Ideas pg 73

Building low-voltage data-acquisition systems: know your ICs pg 89

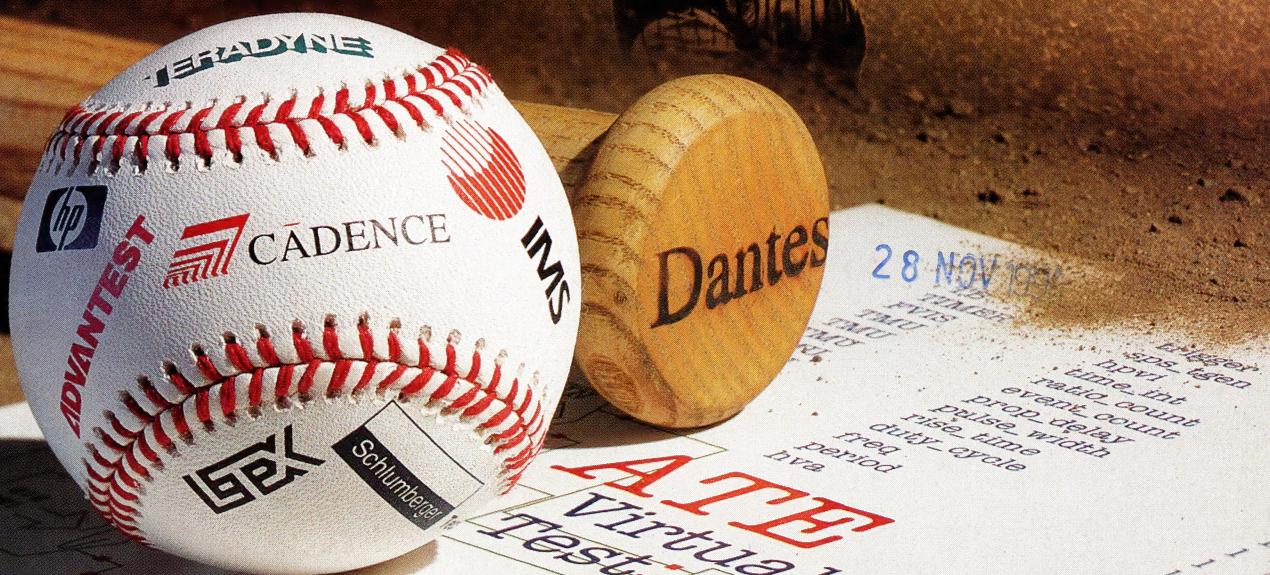Jack Ganssle Troubleshooting: Avoiding the bog



A CAHMEERS PUBLICATION

The Flat Out Winner



BELDEN

Who leads the pack in flat cable value? The same front-runner who sets the pace in all areas of cable quality and technology – Belden.

Thanks to our superior technical capabilities and dedicated manufacturing facilities, we've been able to bring our cost on flat cable down . . . *to the wire!* So, whether you're specifying for OEM applications or creating flat cable assemblies, you can get the product you need. And, it's available packaged on reels for automatic termination equipment compatibility. How's that for blue-ribbon value?

Find out more about our complete line of mass-termination flat cables, including our round-to-flat MASS-TER®, 9K ribbon coaxial, shielded data link, and new 1mm and .025" miniatures. For your copy of our Flat Cable Catalog, call:




1-800-BELDEN-4.

Belden

CIRCLE NO. 48

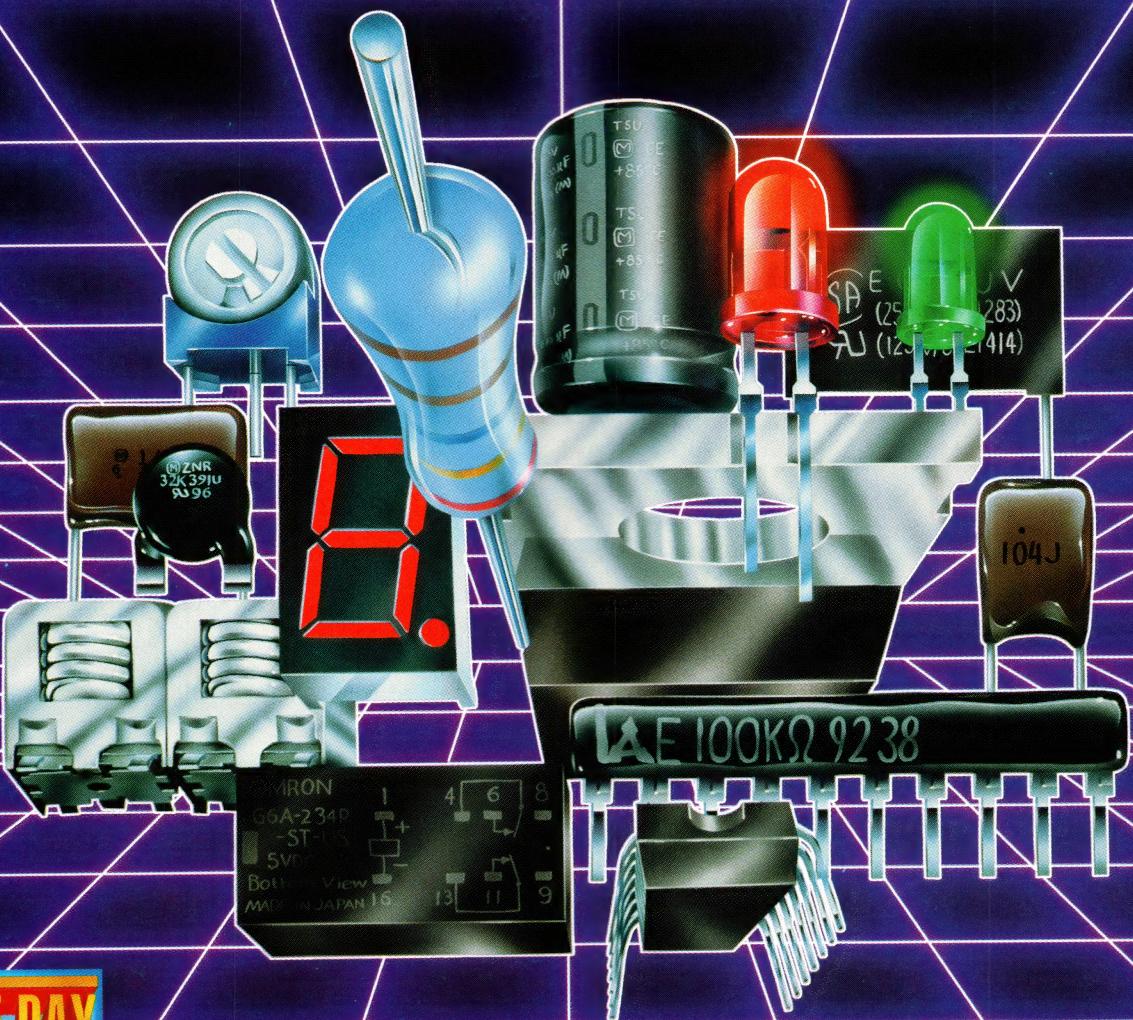Quality Electronic Components Superior Service



On orders placed by
5:00 pm central time.

**Rated #1 for...
On-Time Delivery!
Availability of Product!
Overall Performance!**

Call, write or fax for your
FREE CATALOG today!

Digi-Key
CORPORATION

701 Brooks Ave. South, Thief River Falls, MN 56701

Toll Free: 1-800-344-4539


Fax: 218-681-3380

Siliconix drives lower on-resistance and incredibly shrinking boards.



Introducing Siliconix's new TrenchFET™ power MOSFETs. Low on-resistance dramatically reduces parts count and increases board reliability.

Thanks to a new process developed and patented by Siliconix, our new family of TrenchFETs feature 8 million cells per square inch and deliver on-resistance as low as 8mΩ with a 60-V breakdown voltage and 175°C maximum junction temperature. The result is fewer parts and smaller, more reliable board designs for automotive applications such as airbags, ABS, power steering, window lifts, motors and fuel pumps.

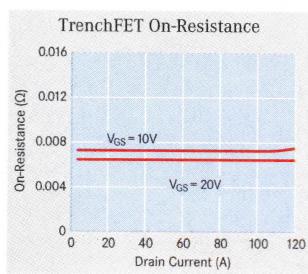

In addition, these TrenchFET devices provide lower conduction

and switching losses, virtually eliminating the need for heatsinks. Siliconix offers five new TrenchFET devices in TO-220 or surface-mount TO-263 (D²PAK) packages and are as cost effective as relays.

New TrenchFETs from Siliconix. They're so power- and cost-efficient, you can satisfy your drive for better, smaller and more reliable board designs. For samples or more information, call us at **1-800-554-5565, ext. 930**.

TEMIC


Siliconix, A Member of TEMIC

TEMIC is a company of AEG Daimler-Benz Industrie. 2201 Laurelwood Road, Santa Clara, CA 95054 Fax: 408-970-3995.
Members of TEMIC Semiconductors: Telefunken Semiconductors, Siliconix, Matra MHS, Dialog Semiconductor.
TEMIC International Sales: UNITED KINGDOM: 0344-485757. GERMANY: 0310 857 320. FRANCE: 130 60 70 00. ITALY: 02-332 121.
SCANDINAVIA: 08-733 0090. SINGAPORE: 65-788 6668, ext. 249. HONG KONG: 852-3789 789. JAPAN: 3-5562 3321.
TrenchFET is a trademark of Siliconix. ©1994 Siliconix/TEMIC. All rights reserved.

RF TRANSFORMERS

Over 80 off-the-shelf models...

3KHz- 2000MHz from **\$195**

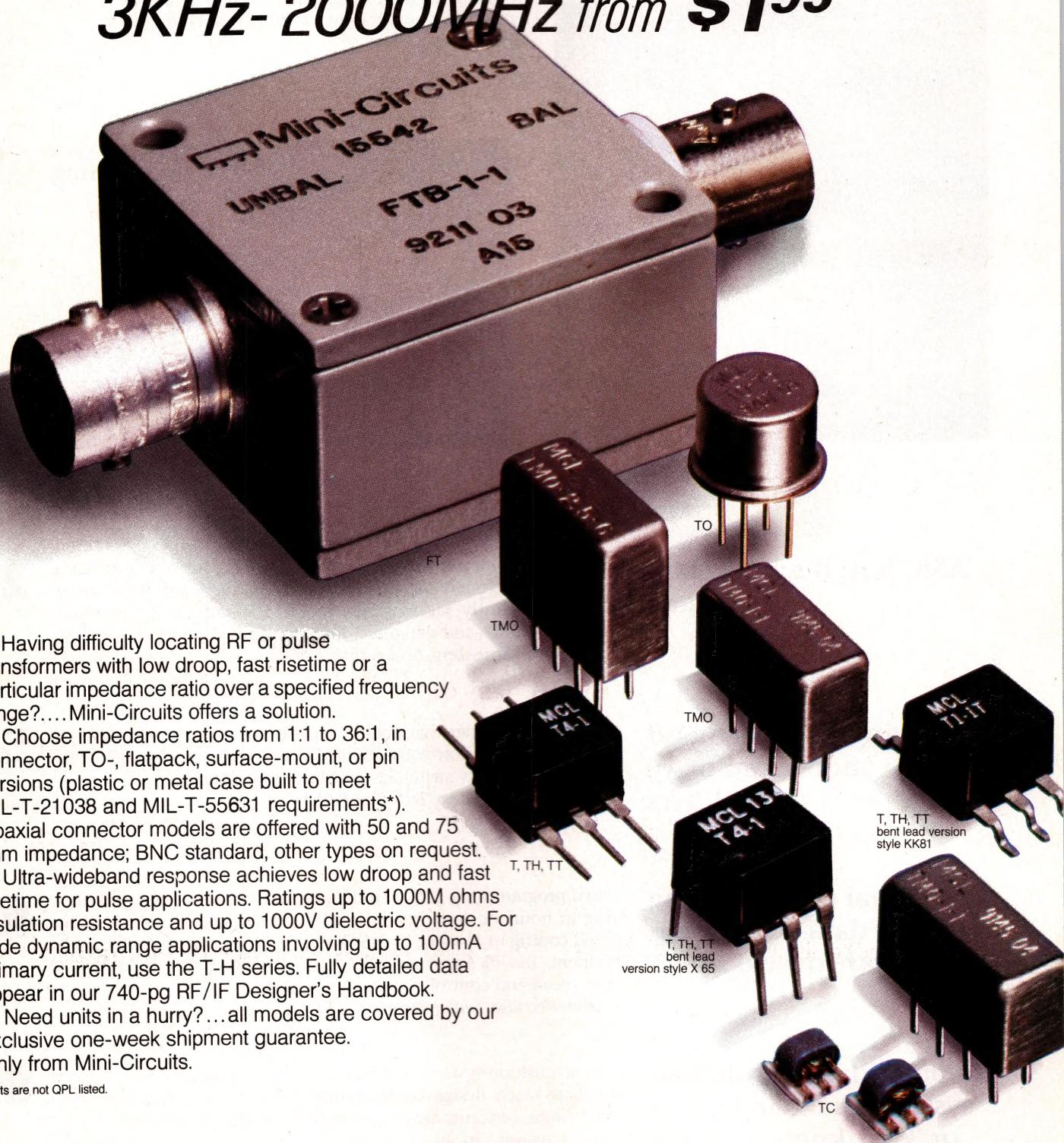

Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specified frequency range?... Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, in connector, TO-, flatpack, surface-mount, or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55631 requirements*). Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard, other types on request.

Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100mA primary current, use the T-H series. Fully detailed data appear in our 740-pg RF/IF Designer's Handbook.

Need units in a hurry?... all models are covered by our exclusive one-week shipment guarantee. Only from Mini-Circuits.

*units are not QPL listed.



Mini-Circuits®


P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS... Let Our Experience Work For You.

CIRCLE NO. 83

F 71 Rev F

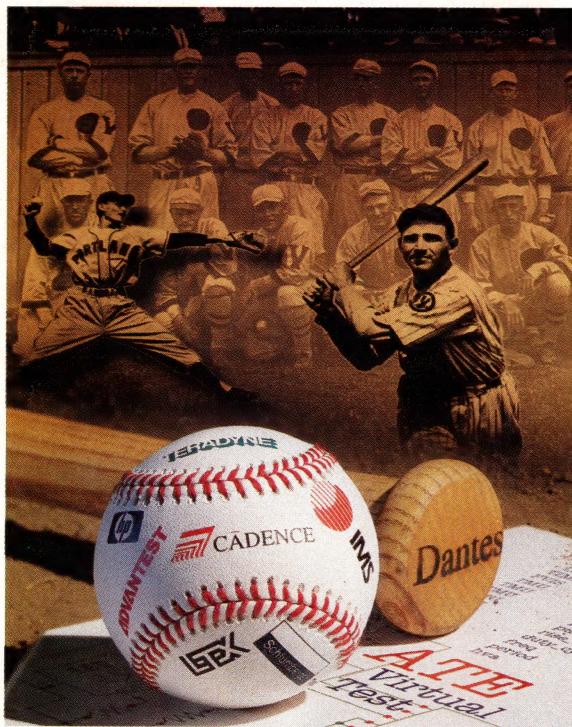

COVER STORY

ASIC test. Photo courtesy Cadence/IMS; historic images provided by the Oregon Historical Society. Design by Richard Anderson, Communications by Design; photography by Dahlstrom Photography Inc.

24

Visual Programming



63

EDN

DESIGN FEATURES

ASIC test: it's a new ball game

Testing ASICs means more than just designing for test. Although today's sophisticated DFT tools are a big step forward from earlier ones, intelligently tackling test requires a partnership between design and test—and designers' full appreciation of what test is all about.—*Dan Strassberg, Senior Technical Editor*

24

Evolving ADCs demand more from drive amplifiers

Finding an amplifier that doesn't tarnish an ADC's performance is hard enough. But now you also have to deal with single-supply voltages and the quirky switched-capacitor input structure.

—*Anne Watson Swager, Technical Editor*

53

Visual programming pervades data-acquisition software development

Visual programming gets your data-acquisition system up and running in hours or days, instead of the months needed to use traditional coding in Basic or C. MS Windows is the most popular environment, but its interrupt latency can threaten data integrity in high-speed and control-system applications.

—*Brian Kerridge, Senior Technical Editor*

63

To build data-acquisition systems that run from 5 or 3.3V, know your ICs


Data-acquisition systems that take power from a single 3.3 or 5V supply share many design considerations with systems that run from ±15V. Some concerns are unique to low-voltage, single-supply operation, however. To avoid problems, you need a thorough understanding of the ICs you use.

—*Kerry Lakanette, National Semiconductor Corp*

89

OUT IN FRONT

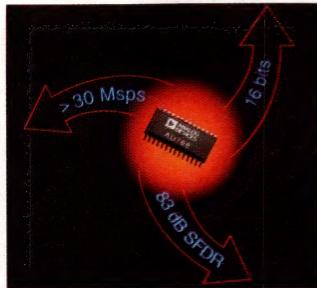16-bit DAC extends ac performance 11
Awards recognize outstanding engineers and products 11
Interface IC allows multiple functions on PCMCIA card 11
ADC fits 14-bit, 10-MHz performance in small package 12



11

PCMCIA card connects PC to MIL-STD-1553 bus 12
Dilbert 12

EDN

DESIGN IDEAS

Spice does digital filters
PC acts as RS-232C protocol analyzer
Maximum voltage sorter uses analog multiplexers
Frequency comparer produces binary results
Power amplifier has transient rail-to-rail swing

EDN

COLUMNISTS

73 Troubleshooting: Avoiding the bog—by Jack Ganssle, Embedded-Systems Contributing Editor
74
76
78
80

EDN

PRODUCTS

Integrated Circuits
Embedded Systems
Electronic Design Automation
Power Sources
Test & Measurement Instruments
Computers & Peripherals

EDN

DEPARTMENTS

105 Staff 8
110 Editorial 21
112 International Advertisers Index 118
113 Career Opportunities 122

EDN® (ISSN 0012-7515, GST Reg. #123397457, C.P.C. Int'l Pub Mail #0280844) is published 38 times per year, bi-weekly with one additional issue per month, by Cahners Publishing Company, A Division of Reed Publishing USA, 275 Washington Street, Newton, MA 02158-1630. Robert L. Krakoff, Chairman and Chief Executive Officer; Timothy C. O'Brien, Executive Vice President/Finance and Administration; Michael Wisner, Senior Vice President/General Manager, Boston Division; Michael Wisner, Vice President/Publishing Director. Circulation records are maintained at Cahners Publishing Company, 8773 South Ridgeline Blvd., Highlands Ranch, CO 80126-2329. Telephone (303) 470-4445. Second-class postage paid at Littleton CO 80126 and additional mailing offices. **POSTMASTER:** Send address changes to EDN®, PO Box 7500, Highlands Ranch, CO 80126-7500. EDN® copyright 1994 by Reed Publishing USA. Rates for non-qualified subscriptions, including all issues: US, \$140.00 one year, \$238.00 two year; Canada, \$209.00 one year, \$355.00 two year [includes 7% GST, GST# 123397457]; Mexico, \$195.00 one year, \$332.00 two year; Foreign surface \$245.00 one year, \$417.00 two year; Foreign air expedited surcharge, add \$152.00 one year, \$304.00 two year. Except for special issues where price changes are indicated, single copies are available for \$10.00 US and \$15.00 foreign. Please address all subscription mail to EDN®, 8773 South Ridgeline Blvd., Highlands Ranch, CO 80126-2329. EDN® is a registered trademark of Reed Properties Inc., used under license.


(Printed in USA)



Squeeze the most out of your design cycle.

You know time is money. And at Texas Instruments, we can help you speed your product to market. Meaning you are free to do what you do best – create the next breakthrough products.

Be first to market with leading-edge designs. From notebooks and PDAs to wireless communications and multimedia, you can harness the power of TI's DSP solutions, low-power 486 microprocessors and mixed-signal devices to design unique products fast. Our industry-leading TMS320 DSP family offers a road map with the flexibility of software-programmable solutions that can migrate into highly integrated, custom DSPs that deliver cost-effective high performance. And compatible logic families and memory devices also help you move your designs easily from 5 V to 3 V.

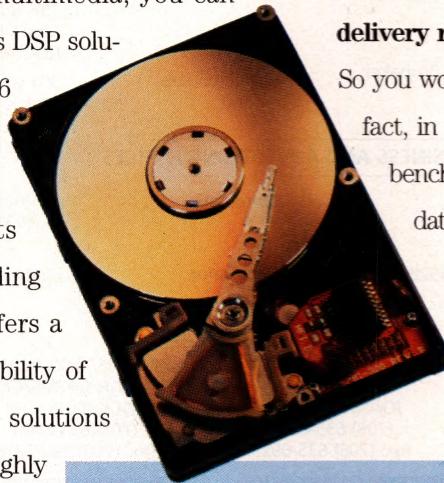

Total Integration in action.

Seagate Technology put the power of Total Integration to work when creating their hard disk drives. In addition to combining TI's high-performance DSP cores and application-specific logic with memory and analog cells, TI had the tools and service to help Seagate produce a highly differentiated product. And TI's on-time delivery made a difference. TI provides high-volume, quick-ramp manufacturing capability to meet Seagate's needs as an industry leader.

Technical support that gets you up to speed, fast. Move quickly from selection to prototype with clear, concise technical information and real-world application notes. And C compilers, emulators, development tools, behavioral models and SPICE rules can help you create DSP solutions in record time.

Setting the benchmark: A 94% on-time delivery record. At TI, we deliver what we promise. So you won't be left waiting for your ICs to arrive. In fact, in an expanding market, we set an industry benchmark by having a 94% on-time-to-commit-date delivery record.

Win the race to market. Getting to market faster with a better product.

That's what business is all about. And with TI, you'll find a unique blend of silicon,

support and service. We call it Total Integration.TM You'll call it your competitive edge. To find out more and receive a free subscription to *Integration*, simply call 1-800-477-8924, ext. 3922.

E X T E N D I N G Y O U R R E A C HTM

 **TEXAS
INSTRUMENTS**

EDN

Home Office: 275 Washington St, Newton, MA 02158. EDN Bulletin Board: (617) 558-4241; MCI: EDNBOS; fax (617) 558-4470; phone (617) 964-3030.

PUBLISHER **Jeffrey Patterson (617) 558-4454**

EDN'S EDITORIAL OFFICES

EDITOR-IN-CHIEF
EXECUTIVE EDITOR
MANAGING EDITOR

Steven H Leibson (617) 558-4214; MCI: ednleibson
Gary Legg (617) 558-4404; MCI: ednlegg
Joan Lynch (617) 558-4215; MCI: ednmorrow

**SENIOR TECHNICAL
EDITORS**

Charles Small (617) 558-4556; MCI: ednsmall
Dan Strassberg (617) 558-4205
MCI: ednstrassberg
Brian Kerridge 22 Mill Rd, Loddon,
Norwich, NR14 6DR, UK; (508) 528435;
fax: (508) 528430; MCI: ednkerridge

**EDITORIAL AND ART
PRODUCTION**

Diane Malone, Manager (617) 558-4303
Kenneth Racicot, Senior Art Director
(617) 558-4708
Chinsoo Chung, Associate Art Director
(617) 558-4446
Patricia Shaughnessy, Production Editor
(617) 558-4206

TECHNICAL EDITORS

John Gallant (617) 558-4666; MCI: edngallant
Richard Quinnell (408) 685-8028 (phone and
fax); MCI: ednquinnell
Anne Watson Swager (215) 645-0544 (phone
and fax); MCI: ednswager
Markus Levy (916) 939-1642; fax: (916) 939-
1650; MCI: ednlevy

**ADVERTISING
PRODUCTION**

Andrew Jantz, Group Manager
(617) 558-4372
Karen Banks, Manager (617) 558-4441
Alice Dorsey, Associate (617) 558-4601

SPECIAL-PROJECTS EDITOR

Doug Conner (805) 461-9669; fax (805) 461-
9640; MCI: edndconner

EDITORIAL SERVICES

Kathy Leonard (617) 558-4405
Helen Benedict (617) 558-4681

**SENIOR ASSOCIATE
EDITORS**

Frances T Granville (617) 558-4344
James P Leonard (617) 558-4324

EDN ASIA

Mike Markowitz, Editor
19F, 8 Commercial Tower, 8 Sun Yip St,
Chai Wan, Hong Kong. phone (011)
(852) 965 1555; fax: (011) (852) 976-0706
301 Gibraltar Dr, Box 650
Morris Plains, NJ 07950
Phone (201) 292-5100; fax (201) 292-0783

ASSOCIATE EDITOR

Anne Coyle (617) 558-4333

**CONTRIBUTING TECHNICAL
EDITORS**

Robert Pease, Jack Ganssle, David Brubaker,
Bill Travis, Don Powers

EDN PRODUCTS

EDN'S BUSINESS AND ADVERTISING OFFICES

ADVERTISING SALES DIRECTOR

Paul Rothkopf (617) 558-4651

CONTRACTS

Muriel Murphy (617) 558-4451
Julie Waelde (617) 558-4250

**MARKETING/BUSINESS
DIRECTOR**

Deborah Virtue (617) 558-4779

**CUSTOM PUBLISHING
SERVICES**

Patricia Tyler, Director (617) 558-4526

CIRCULATION

Debbie Barela (303) 470-4000

ASSISTANT TO PUBLISHER

Maria McGrath (617) 558-4346

NEW ENGLAND
CHRIS PLATT
(617) 964-3730
fax: (617) 332-7128

**NEW YORK/NEW JERSEY/
MID/SOUTH ATLANTIC**
DIANE DRISCOLL
(203) 326-5161
fax: (203) 326-5160

**IL/IN/KY/OH/TN/
TX/OK/FL/SC**
JOANN CANNON
(708) 635-8800
fax: (708) 635-0929

**IL/MI/MN/NE/IA/KS/ND/SD/WI/
MO/AL/AR/GA/MS/CANADA**
JACK JOHNSON
(708) 635-8800
fax: (708) 390-2815

ARIZONA
DONNIE JONES ADAMS
(408) 243-8838
fax: (408) 243-2144

**ORANGE/RIVERSIDE/SAN DIEGO
COUNTIES/LOS ANGELES/**
Southern CA/NV
SUSAN N GREEN
(714) 851-9422
fax: (714) 752-6867

**COLORADO/
WASHINGTON/OREGON**
ROGER GAW
(408) 243-8838
fax: (408) 243-2144

NORTHERN CA/SILICON VALLEY
DONNIE JONES ADAMS
BETTINA MCGOWAN
ROGER GAW
(408) 243-8838
fax: (408) 243-2144

EUROPEAN OPERATIONS
TULLY GIACOMAZZI
(011) 49 89 769 02 391
fax: (011) 49 89 769 02 144

UK
JOHN WADDELL
(011) 44 81 312 4696
fax: (011) 44 81 312 1078

NORWAY/SWEDEN/FINLAND
ROLAND NIHLMAR
LARS GRUNBERGER
(011) 46 8616 0760
fax: (011) 46 8616 0777

DENMARK
AASE KISBORG
(011) 45 33 14 9888
fax: (011) 45 33 14 9288

**NETHERLANDS/BELGIUM/
GERMANY ZIP CODES 0-5**
ALBERT TICHELER
(011) 31 40 41 37 27
fax: (011) 31 40 42 0430

GERMANY ZIP CODES 6-7
RENATE MUNK
(011) 49 6272 2345
fax: (011) 49 6272 2167

GERMANY ZIP CODES 8-9
MARGARETHE MUNCHMEIER
(011) 49 89 222 015
fax: (011) 49 89 299 160

SPAIN
LUIS GINER
(011) 343 894 43 26
fax: (011) 343 894 88 37

AUSTRIA
SVEN KOLLENSPERGER
(011) 43 732 79 34 55
fax: (011) 43 732 79 34 58

ISRAEL
ASA TALBAR
(011) 972 35 223 621
fax: (011) 972 35 242 177

ITALY
ROBERTO LAURERI
(011) 39 2 236 2500
fax: (011) 39 2 236 4411

SWITZERLAND
ROSWITHA N BRIAND
(011) 41 1261 4690
fax: (011) 41 1251 4542

FRANCE
ALAIN FAURE
(011) 331 4629 4629
fax: (011) 331 4093 0337

HONG KONG
ADONIS MAK
(011) 852 965 1555
fax: (011) 852 976 0706

JAPAN
KAORU HARA
(011) 813 3389 1822
fax: (011) 813 3389 1761

KOREA
JEONG-GWON SEO
(011) 82 2752 4392
fax: (011) 82 2752 4394

SINGAPORE/MALAYSIA
HOO SIEW SAI
(011) 65 738 0122
fax: (011) 65 738 2108

TAIWAN
PARSON LEE
JOHN SHIH
(011) 886 2711 4833
fax: (011) 886 2741 5110

AUSTRALIA
ALEXANDRA HARRIS-PEARSON
(011) 612 299 5677
fax: (011) 612 299 6178

TURKEY
CENGIZ EREN
(011) 90 216 345 3473
fax: (011) 90 216 346 2464

INSIDE SALES
LISA BARRIERE
(617) 558-4361
fax: (617) 558-4328

**INFO CARDS/
LITERATURE LINK**
MELISSA BACHMAN
(617) 558-4282
fax: (617) 558-4328

RECRUITMENT
JACQUELINE DANIELS
(617) 558-4488
(617) 630-3925



PRODUCT MART
JOANNE DORIAN
(212) 463-6415
fax: (212) 463-6404

CAHNERS MAGAZINE DIVISION
ROBERT KRAKOFF,
President, CEO
Cahners Publishing

CAHNERS MAGAZINE DIVISION
MICHAEL WISNER
Senior VP/General Manager
Boston Division

CAHNERS MAGAZINE DIVISION
TOM DELLMARIA
Senior VP/
Production & Manufacturing

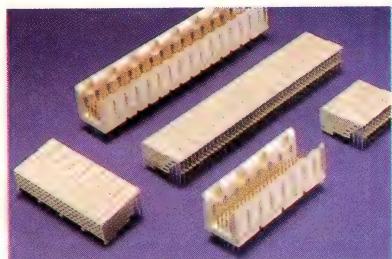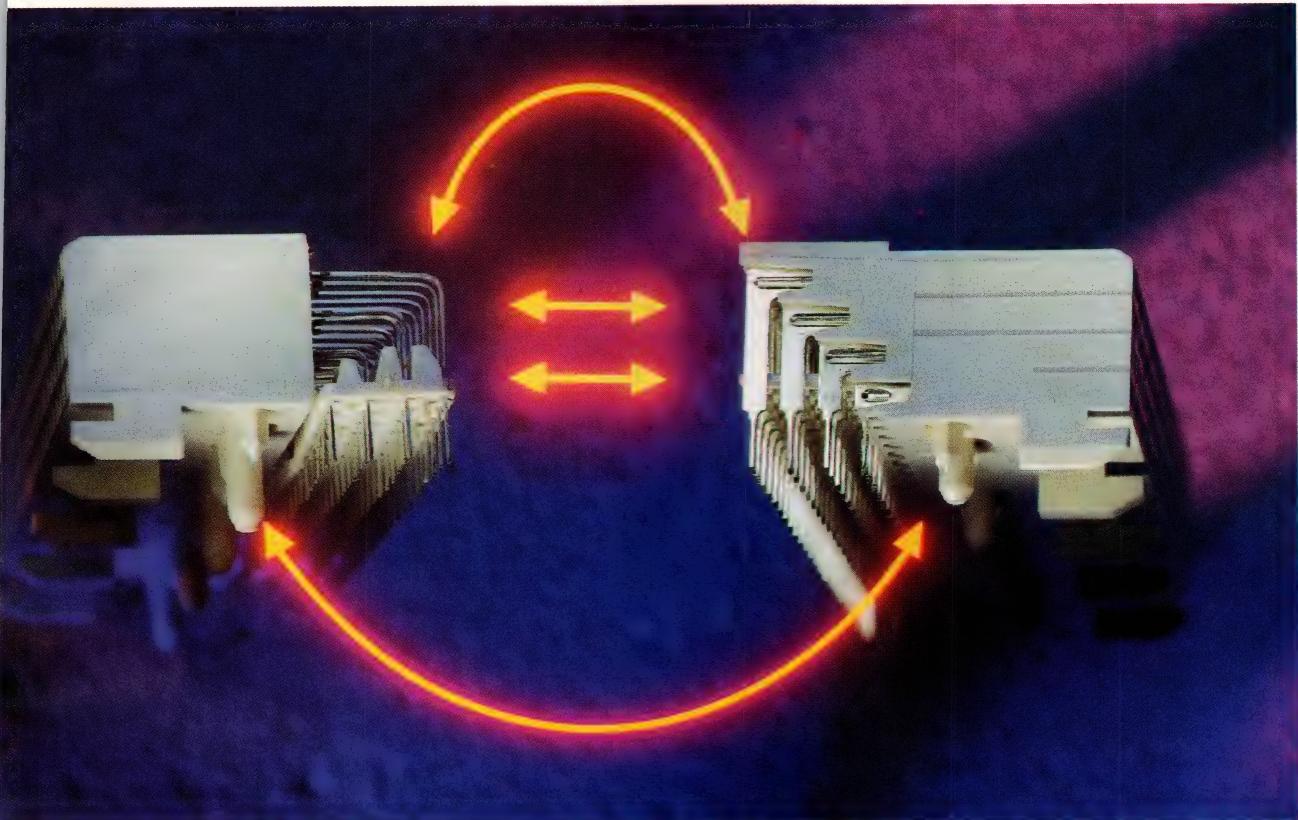*Before you go back to the same old future,
compare it with ours.*



Modular and one-piece "monoblock" versions of AMP Futurebus+ connectors offer significant advantages in handling, production, and use.

If the interchangeability and intermateability of the Futurebus+ standard are important to you, we've got news worth hearing: our Z-Pack 2mm FB line offers just what you want, at a very competitive price—with significant added advantages in production, and in the field.

Compare it with what you may be specifying right now, and the differences are obvious. Their leads are exposed—subject to damage during handling, insertion, rework, and field use. Ours are covered, providing protection and allowing simple, flat-rock tooling for our press-fit versions. Their lead organizers are loose, separate pieces; ours are an integral part of the connector body. With this connector, truer position means

easier insertion. Note that their leads are bent to shape. Ours are stamped in shape for structural strength, and use more metal.

Their connectors require heat-staking, or—with press-peg holddowns—high board insertion forces. Ours has a patented "Cold Hold" system, with a metal spring barb embedded in the plastic post. This gives a low force fit with excellent strength and retention.

And we offer one-piece "monoblock" styles to simplify inventory and cut manufacturing effort even more. The bottom line: our version of the future offers you a whole lot more. Just give us a call.

AMP and Z-Pack are trademarks.

For more information on the Z-Pack 2mm FB product line, call our Product Information Center at 1-800-522-6752 (fax 717-986-7575). AMP, Harrisburg, PA 17105-3608. In Canada, call 905-470-4425.

AMP



Our EMI filters help keep your briefcase from becoming a battleground.

If business is war, this is where the fight gets serious.

Cellular phones, notebook computers, pagers and soon, PCS devices – the potential for interference among them is surpassed only by the potential for interference inside them. Fortunately, our EMI/RFI filters are superb peace-keepers. We offer the widest selection of EMI/RFI filters in the industry, in unsurpassed ranges of inductance and capacitance values, temperature ratings, frequencies and current ratings. Products like our unique high-frequency L-Chip Inductor, with its precision tolerance of

±2%, are made possible by our exclusive thin-film technology. And our ability to combine high current ratings with lower DC resistance means you don't have to compromise one for the other in your designs. So as you're designing the newest weapon for the corporate wars, let us be a small part in your success and help you avoid internal strife. For more information and our EMI Filter catalog, call **1-800-831-9172, ext. 151.**




**A small part
in your success**

16-BIT DAC EXTENDS AC PERFORMANCE

The Analog Devices current-output AD768 combines the speed characteristics of 12-bit DACs with the precision of 16-bit devices and includes full dc and ac performance specifications. The guaranteed minimum update rate is 30M samples/sec; 40M samples/sec is typical. Other key typical specifications include 1/2-LSB differential nonlinearity at 14 bits, 83-dBc spurious-free dynamic range at 1.002 MHz, 35 pV-s glitch impulse, 465-mW power dissipation, and full-scale settling time of 25 nsec to 0.025%. Price is also a key feature of this DAC; at \$19.95 (1000), it costs less than some of the company's 12-bit devices in the same speed range.

The manufacturer has also provided a glimpse into the DAC's performance for video-on-demand applications, such as an asymmetrical digital subscriber line (ADSL)—

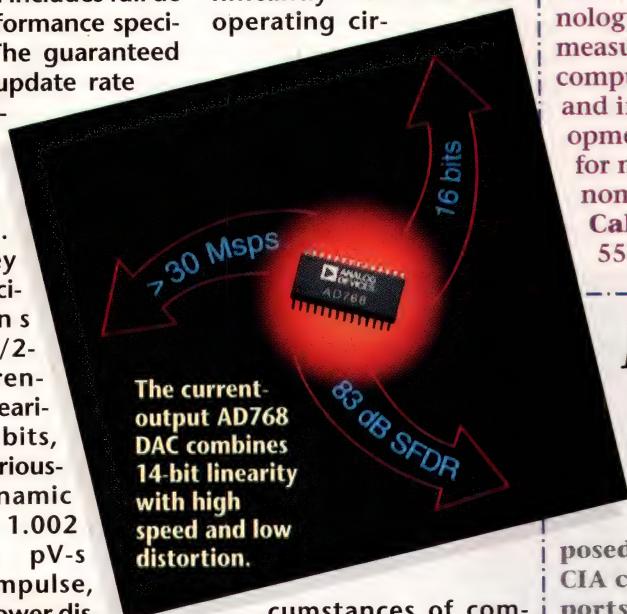one of the standards ANSI is evaluating. Most DAC ac specifications are the result of tests with single-tone signals that differ significantly from the real operating cir-



cumstances of communications applications, which use spread-spectrum and frequency-division-multiplexed signals. The AD768's data sheet shows the following test result of a typical ADSL transmit chain: S/N ratio of 63.5 dB at 151 kHz and THD of -60 dBc at 160 kHz.

—by Anne Watson Swager
Analog Devices, Wilmington, MA, (617) 937-1428. Circle No. 482

VIEWLOGIC ANNOUNCES EDA BRIDGE. Viewlogic System and TEAM Corp have announced an EDA-bridge tool bar. The product presents Windows-style graphical icons for point-and-click control of frequently used commands and functions. According to the companies, the bridge makes Viewlogic's Pro Series CAE tools easier to learn and use.

TEAM Corp, Oakville, ON, Canada,
(905) 842-1303. Circle No. 483
Viewlogic Systems Inc, Marlborough, MA,
(508) 480-0881. Circle No. 484

Awards recognize outstanding engineers and products

EDN's annual Innovation and Innovator of the Year Competition honors outstanding engineering professionals who are committed to quality and creativity in electronics. The magazine presents innovation awards in the following eight major product/technology areas: ICs and semiconductors; µPs; test and measurement; electronic-design-automation tools; computers and peripherals; components, hardware, and interconnection technology; embedded development software; and power sources. Applications for nomination are due by Nov 15. Call EDN for a nomination package.—by Fran Granville
Cahners Publishing Co, Newton, MA, (617) 558-4681. Circle No. 485

Interface IC allows multiple functions on PCMCIA card

National Semiconductor's InfoMover PCM16C00 is the first communications interface circuit that implements the proposed PCMCIA multifunction standard for PCMCIA card designs. The InfoMover PCM16C00 supports any two I/O functions and memory that operate concurrently on a single PCMCIA card. The interface circuit seamlessly supports National's ST-NIC Ethernet controller device or any other LAN controller. The other function on the card could be a fax/modem chip set.

The challenge of implementing multifunctions on a PCMCIA card is that the host interface has only one interrupt-request (IREQ) line. Each function must use this line to get the attention of the µP in the main computer. Sharing the line can cause problems when more than one device driver attempts to use this line simultaneously.

In cooperation with the PCMCIA committee, National came up with an arbitration method for using the IREQ. The method employs priority or round-robin protocols, whichever the user prefers, informs the host system which function actually requires service, and arbitrates among them.

The multifunction circuit also offers power-management features that conserve battery life in portable or handheld computers. The PCM16C00 operates at 3.3 or 5V, and you can turn off or put into a sleep mode one or two functions on the card. In addition, the interface device supports hot-swapping so that you don't have to reboot the system when changing cards. The device comes in a 144-pin TQFP and costs \$15 (1000).

—by John Gallant
National Semiconductor Corp, Santa Clara, CA, (800) 272-9959. Circle No. 486

ADC fits 14-bit, 10-MHz performance in small package

Datel's ADS-945 achieves its high-resolution, high-speed performance not in a power-hungry board-level design but in a 2×4-in. DIP with a package height of 0.29 in. At 4.5W, the 945's typical power consumption is less than 40% of the nearest small-package competitor. Key technical specifications include no missing codes to the 14-bit level over the industrial temperature range (-25 to +85°C), minimum S/N ratio of 78 dB, and maximum THD of -80 dB for dc to 1-MHz signals. The ADC, which includes a T/H amplifier, a reference, timing/control logic, and error-correction circuitry, costs \$866 (100) for a commercial-temperature version. The industrial-temperature version costs \$1079.

—by Anne Watson Swager
Datel Inc, Mansfield, MA,
(508) 339-3000, ext 227.

Circle No. 487

Data-acquisition system streams 1M samples/sec to disk

BY COMBINING A PENTIUM PC containing a fast 1.7-Gbyte, SCSI hard drive with a 1M-sample/sec, 12-bit ADC board and some clever software, United Electronic Industries (UEI) has produced a system that can acquire nearly one-half hour of data nonstop at the ADC's top sampling rate. The hard drive is one of the "AV" types, which, unlike standard high-capacity drives, does not pause periodically for thermal recalibration of its read/write head. It's also removable; you can substitute a 3.02-Gbyte unit if you need to record even more data nonstop.

The \$9750 system comes with a 17-in., high-resolution color monitor; selecting a 15-in. unit saves \$250. You can also substitute other data-acquisition boards for the base system's Win-30D, or you can add a second board. The software runs under DOS. Part of its speed is attributable to its ability to pack four 12-bit conversion results into three 16-bit data transfers. If your acquired data set does not use too much of the room on the hard disk, the software rewrites the file onto the drive in a format that matches the requirements of the package you will use to postprocess the data. Moreover, UEI's software, which is available separately for \$295 (source code, \$695) lets you omit portions of the initial record from the final data file.

—by Dan Strassberg
United Electronic Industries, Watertown, MA, (617) 924-1155.

Circle No. 488

PCMCIA card connects PC to MIL-STD-1553 bus

With a new PCMCIA card from ILC Data Device Corp (DDC), you can bring the power and convenience of portable computing to the MIL-STD-1553 data bus. The BU-65550 card provides an intelligent interface between a Type II PCMCIA slot and the dual-redundant 1553 bus, making the card useful for testing and system-integration tasks.

The card incorporates DDC's BU-61586 Advanced Communications Engine (ACE). The ACE includes dual transceivers and encoder/decoders, complete 1553 protocol, 12k words of shared RAM, and memory-management logic for the bus-controller, remote-terminal, and bus-monitor modes. Each card costs \$3995.—by Gary Legg
ILC Data Device Corp, Bohemia, NY, (516) 567-5600, ext 7381.

Circle No. 490

DILBERT® by Scott Adams



The Fluke 79: More Of A Good Thing

More high-performance features.
More advanced measurement capabilities. More of the vital information you need to troubleshoot even the toughest problems — with both analog and digital displays.

Meet the latest, greatest member of our best selling 70 Series II family — the new Fluke 79 digital multimeter.

It picks up where the original family left off. In fact, it's a quantum leap forward — in performance, value and affordability.

It's got the features you'd expect from Fluke. Including high resolution. Fast autoranging. Patented, automatic Touch Hold®. A quick continuity beeper. Diode test. Automatic self-test. Battery-conserving sleep mode. And it's just as rugged and reliable as the rest of the 70 Series II family. Easy to operate, too — with one hand.

And thanks to the Fluke 79's proprietary new integrated circuit technology, that's only the beginning. When it comes to zeroing in on tough electrical problems, the Fluke 79 leaves the competition behind:

Hz

Frequency: The Fluke 79's built-in frequency counter lets you measure from below 1 Hz to over 20 kHz. And while you view frequency on the digital display, the analog bar graph shows you AC voltage. So you can see if potentially hazardous voltage is present.



Fast 63-segment analog bar graph: The Fluke 79's bargraph moves as fast as the eye can see, updating at a rate of 40 times per second to simulate the functionality of an analog needle. You get the high speed and high resolution you need to detect peaking, nulling and trending.

←

Capacitance: No need to carry a separate dedicated capacitance tester; the Fluke 79 measures capacitance from 10 pF to 9999 μ F.



Actual Size

40Ω


Lo-Ohms range: Our proprietary Lo-Ohms function lets you measure resistance as low as 0.01 ohms. High noise rejection and a test lead Zero Calibration function make the Fluke 79 ideal for detecting small resistance changes.

SMOOTHING

Smoothing™: Our exclusive new Smoothing mode gives you a stable digital readout for unstable signals — by displaying the running average of eight readings. No more jitter or "digit rattle" due to noisy signals.

Get a good thing going: To put more meter to work for you — at a price that works for you, too — head for your nearest Fluke distributor. For the name of your nearest distributor, or for more product information, call **1-800-87-FLUKE**.

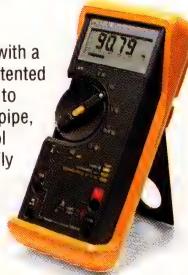The Fluke 79 comes with a yellow holster and patented Flex-Stand™ — easy to hang from a door or pipe, clip onto a belt or tool kit, or stand at virtually any viewing angle. There's even storage space for test leads.



Fluke 79 Series II

\$199*
4000 Count Digital Display (9999 in Hz, capacitance, and Lo-Ohms)
63-segment Analog Bar Graph
0.3% Basic DC Voltage Accuracy
Automatic Touch Hold
Diode Test, Audible Continuity Beeper
Autoranging, Manual Ranging
Holster with Flex-Stand
Frequency Counter to over 20 kHz
Capacitance, 10 pF to 9999 μ F
Lo-Ohms Range with Zero Calibration
Smoothing
700 Hours Battery Life (alkaline)
3-Year Warranty

* Suggested U.S. list price


Fluke Corporation P.O. Box 9090, M/S 250E Everett,
WA 98206. ©Copyright 1993. Prices and specifications
subject to change without notice. Ad No. 00512

FLUKE®

Chips lower cost of video playback

New ICs from Cirrus Logic allow low-cost implementations of video playback on both desktop and portable computers. For desktop designs, the CL-GD5440 provides video control and acceleration, and an optional CL-PX4072 multistandard TV decoder accepts NTSC, PAL, or SECAM inputs. For portable systems, the CL-GD7542 provides video control and acceleration with an optional video-overlay port. The cost to implement a video subsystem with the chips, excluding memory and depending on options, ranges from about \$30 to \$70 in OEM quantities. The ICs work on either the PCI or the VL bus.

Video subsystems designed with the new chips and $256k \times 16$ -bit DRAMs can display full-screen, full-motion (30-frame/sec) video. The two video-controller chips provide horizontal and vertical interpolation between incoming video pixels to scale a video image to screen size or smaller. The CL-GD5440 for desktops provides one- to four-times scaling; the CL-GD7542 for portables has two-times scaling. The number of available colors in desktop imple-

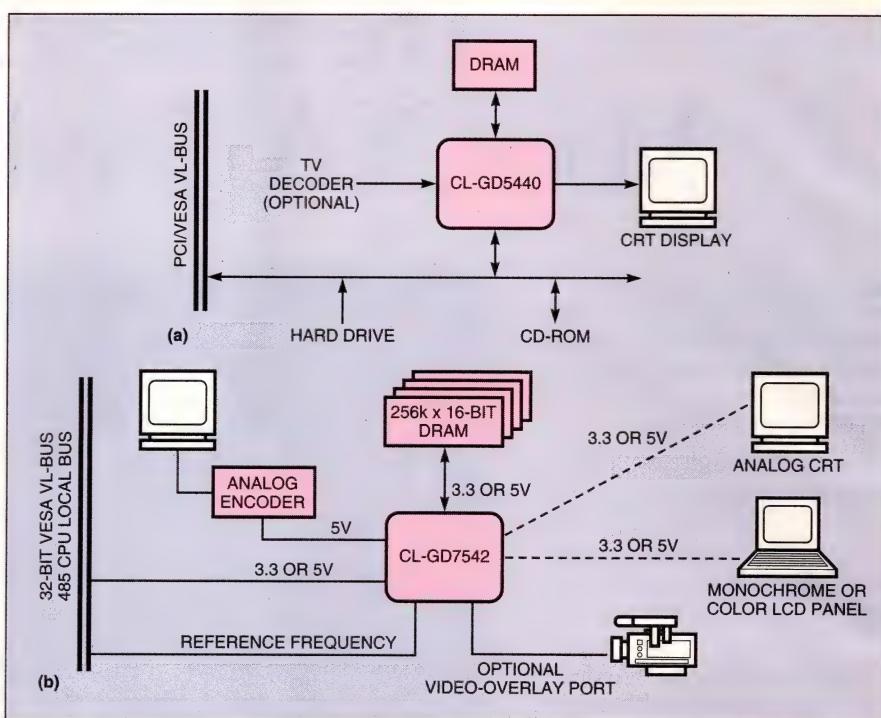

New ICs from Cirrus Logic implement video playback on desktop systems (a) and on portables (b).

mentations ranges from 16 for 1280×1024 -pixel displays to 64,000 for 800×600 -pixel displays. For portable implementations, the color range is from 16 million for 640×480 -pixel displays to 256 for

larger displays. The CL-GD7542 for portables supports the new 800×600 -pixel SVGA format and other formats. —by Gary Legg

Cirrus Logic, Fremont, CA, (510) 623-8300.

Circle No. 491

Clamped amplifiers jump in accuracy and add a surprise

The AD8036 and AD8037 from Analog Devices offer high linearity and clamp accuracy—an order of magnitude improvement over existing clamped amplifiers. In addition, an engineer at the company found another benefit of the devices: You can easily configure them as full-wave rectifiers, in one case by connecting the noninverting input to the high or low clamp inputs. You can even put a modulating signal into the high and low clamp inputs, which each have a bandwidth of at least 100 MHz.

A proprietary design that implements the clamping at the amplifier input as opposed to the output provides the very high clamp accuracy that makes additional applications possible. Maximum and typical output deviations from the clamp voltage setting are ± 25 and ± 15 mV, respectively. The design also minimizes signal distortion near the clamp voltages and allows for a maximum useful amplifier range. You can set the clamp voltage, for example, to any value in the $\pm 3.9V$ output range.

In the unclamped region, these 250- and 275-MHz amplifiers also have very low distortion; they are cousins of the recently introduced wide-bandwidth, ultra-low-distortion 320-MHz AD9631 and 250-MHz AD9632, which boast a spurious-free dynamic range of -72 dBc typical at 20 MHz. The AD8036 is unity-gain stable, and the AD8037 is stable for gains of +2; you must use both in noninverting configurations. Settling time to 0.01% accuracy is 16 nsec. All of these low-distortion amplifiers cost \$4.12 (1000). One main application for all these devices is driving high-speed, high-resolution ADCs (see "Drive amplifiers for ADCs" in this issue). —by Anne Watson Swager

Analog Devices Inc, Wilmington, MA, (617) 937-1428. **Circle No. 492**


Current-feedback amps increase in accuracy

"Precision" and "accuracy" are two words not usually associated with current-mode feedback amplifiers. These amplifiers' claim to fame is high bandwidth without the familiar gain-bandwidth roll-off of voltage-feedback amplifiers. However, Elantec Corp is combining precision and current feedback in the form of the EL2165C and the EL2175C. These amplifiers provide designers of high-speed-instrumentation, video, imaging, and communications systems with much better dc characteristics than are available in conventional current-mode feedback amplifiers. With -3-dB bandwidth for gains of +2 at 30 and 120 MHz, input offset voltage is

(Continued on pg 16)

STEP UP To PSPICE®

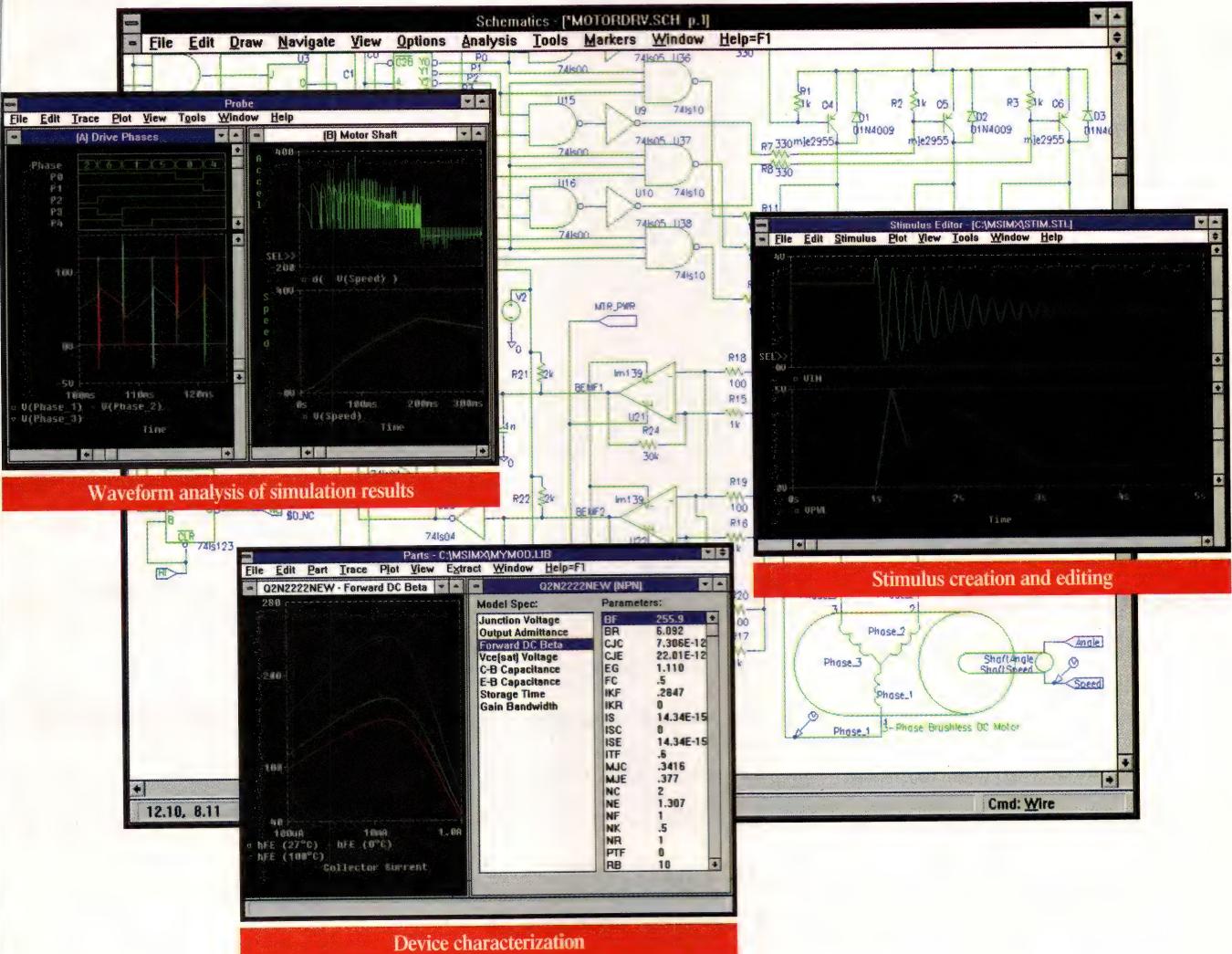TRADE IN YOUR COMPETITIVE SPICE-BASED SIMULATOR
FOR MICROSIM PSPICE AT A 50% DISCOUNT



Now you can save 50% off the regular price of MicroSim PSpice, the industry standard for quality in SPICE-based simulation. You'll find the versatile modeling capabilities of PSpice are far superior — and you can even run it on the same platform you're now using, whether your current simulator runs on the IBM-PC (Microsoft® Windows™ or DOS), HP, Sun, or even within the Cadence or Mentor framework.

MicroSim PSpice delivers the most advanced analog simulation capabilities today. Features like proprietary algorithms with exceptional accuracy over a wide range of analyses and device models. Aurora-certified BSIM3 models. And the most comprehensive libraries providing over 7,400 analog parts. What's more, you're guaranteed unrivaled

service including free expert technical support, an informative BBS, flexible upgrade policies, quarterly technical newsletters and more.

Plus, when you use PSpice, the door is open to a wide range of options to help you produce more reliable designs. That's because PSpice is only one part of the **MicroSim Design Center®** family of analog and digital products.

Join more than 20,000 satisfied PSpice customers worldwide. All you have to do is send us your competitive SPICE-based simulator to save 50% on analog PSpice. But hurry, because this discount is available for a limited time only — offer ends December 23, 1994. Don't miss out. Call today for more information.



MicroSim Corporation

The Desktop EDA Company

20 FAIRBANKS • IRVINE, CA 92718 • USA • (714) 770-3022
(800) 245-3044 • FAX: (714) 455-0554 • BBS: (714) 830-1550

Design Center and PSpice are registered trademarks of MicroSim Corporation. All other trademarks are the property of their respective owners.

• Circle No. 150 for PC • Circle No. 152 for Workstation

EDN September 29, 1994 • 15

500 µV, and negative input-bias current is 500 nA. Respective peak-output currents are 50 and 80 mA. The 2165C consumes 4 mA, and the 2175V consumes 8.5 mA. The 2165C settles to 0.1 and 0.01% in 110 and 185 nsec. Both operate on supplies ranging from ±3 to ±16V and provide input/output compliance to within 2V of the supplies. Respective settling times to 0.1 and 0.01% are 110 and 185 nsec for the 2165C and 55 and 85 nsec for the 2175C. The devices come in 8-pin DIPs and SOICs, and prices start at \$2.67 (1000). Samples will be available this month. (All listed specifications are for typical performance.)

—by Anne Watson Swager

Elantec Corp, Milpitas, CA, (408) 945-1323. Circle No. 493

Wider tape boosts minicartridge capacity

New QIC-Wide products from Conner and Sony enable a QIC tape minicartridge to store 420 Mbytes of compressed data, conveniently keeping pace with storage capacities of the disk drives in many new high-end PCs. Sony's QIC-Wide media is responsible for the high capacity, providing a 68% increase over typical 250-Mbyte QIC-80 minicartridges. Conner's 11250M tape drive, which uses the new media, is also compatible with standard QIC media.

QIC-Wide tape is 0.315 in. wide, compared with 0.25 in. for QIC tape. Because the extra width provides additional strength, Sony can make the tape thinner and thus pack more of it into a minicartridge—400 ft vs the usual 307 ft. A redesigned Conner tape-drive head accommodates the wider media, and modified tape-drive firmware ensures QIC and QIC-Wide compatibility. An internal-mount version of the new Conner drive sells for \$114 (OEM); an external, parallel-port model costs \$244. A Sony minicartridge two-pack will sell for under \$50. —by Gary Legg

Conner Tape Products Group, Costa Mesa, CA, (714) 641-1230. Circle No. 494

IC ATE systems economize on pin electronics

Today's digital ICs often have pin counts in the hundreds but operate at maximum speed only on a fraction of their pins. Integrated Measurement Systems (IMS) has found a way to save sizable sums for purchasers of testers for these devices. Instead of following the industry custom of providing the same performance on all pins, for its ATS Blazer! system, IMS has designed a 100-MHz pin-electronics card that is mechanically and electrically interchangeable with the system's 200-MHz card. The 200-MHz card uses a mixture of silicon and GaAs ICs to achieve its performance; the 100-MHz card uses silicon devices exclusively and is, therefore, substantially less expensive. A 320-pin system one-third of whose pins operate at 200 MHz costs less than half of the \$1.6-million cost of competitive systems that have the same number of pins, all capable of running at 200 MHz.

At the same time (that is, at next week's International Test Conference in Washington, DC), IMS parent, Cadence Design Systems Inc, in conjunction with the Industrial/Consumer Division of automatic-test-equipment vendor Teradyne Inc, will announce a pair of enhanced packages for development of programs for testing mixed-signal ICs. Version 2.0 of Cadence's Dantes virtual-test software, integrated with Teradyne's Image ExChange test-event simulator, enables test engineers to verify device-test programs without waiting for first silicon and without taking time on a tester. (See this issue's cover story on pg 24.)

—by Dan Strassberg

Cadence Design Systems, Beaverton, OR, (503) 626-7117. Circle No. 495

Integrated Measurement Systems Inc, Beaverton, OR, (503) 626-7117. Circle No. 496

Teradyne Inc, Boston, MA, (617) 422-2567. Circle No. 497

MOS-controlled thyristors get some backup



Harris Semiconductor is extending support for its MOS-controlled thyristor (MCT) with the HIP2030 gate driver, which also simplifies designing with high-power insulated-gate bipolar-transistor (IGBT) modules. To drive an MCT previously required one dual FET driver, two FETs, two diodes, two capacitors, and 11 resistors. Designed by Harris and available since 1992, MCTs are power-switching devices that provide a two-times current-rating increase over IGBTs along with a lower forward voltage drop in the same die size. MCTs are useful in power-switching applications at rates up to around 100 kHz whenever high current and low conduction loss are prime requirements.

MCTs may seem more complicated to use because they require a dual-polarity control signal, but many IGBT manufacturers now recommend using similar control signals for IGBTs because of their large gate capacitances. By switching the polarity of its output and adjusting two resistors to obtain the desired voltage levels, the HIP2030 can drive IGBT modules. The HIP2030 (\$5.50 (1000)) can drive 60 nF of MOS capacitance with 30V p-p in less than 200 nsec and 15 to 20 nF in less than 100 nsec. The IC also includes a charge pump so that it can operate from a single low-voltage supply as well as from the single or dual high-voltage supplies that provide the MCT gate-drive voltages. A latch/reset circuit can inhibit drive to the MCT gate in the event of excessive load current or overheating.

—by Anne Watson Swager

Harris Semiconductor, Melbourne, FL, (800) 442-7747, ext 7267. Circle No. 498

They see how video works wonders.

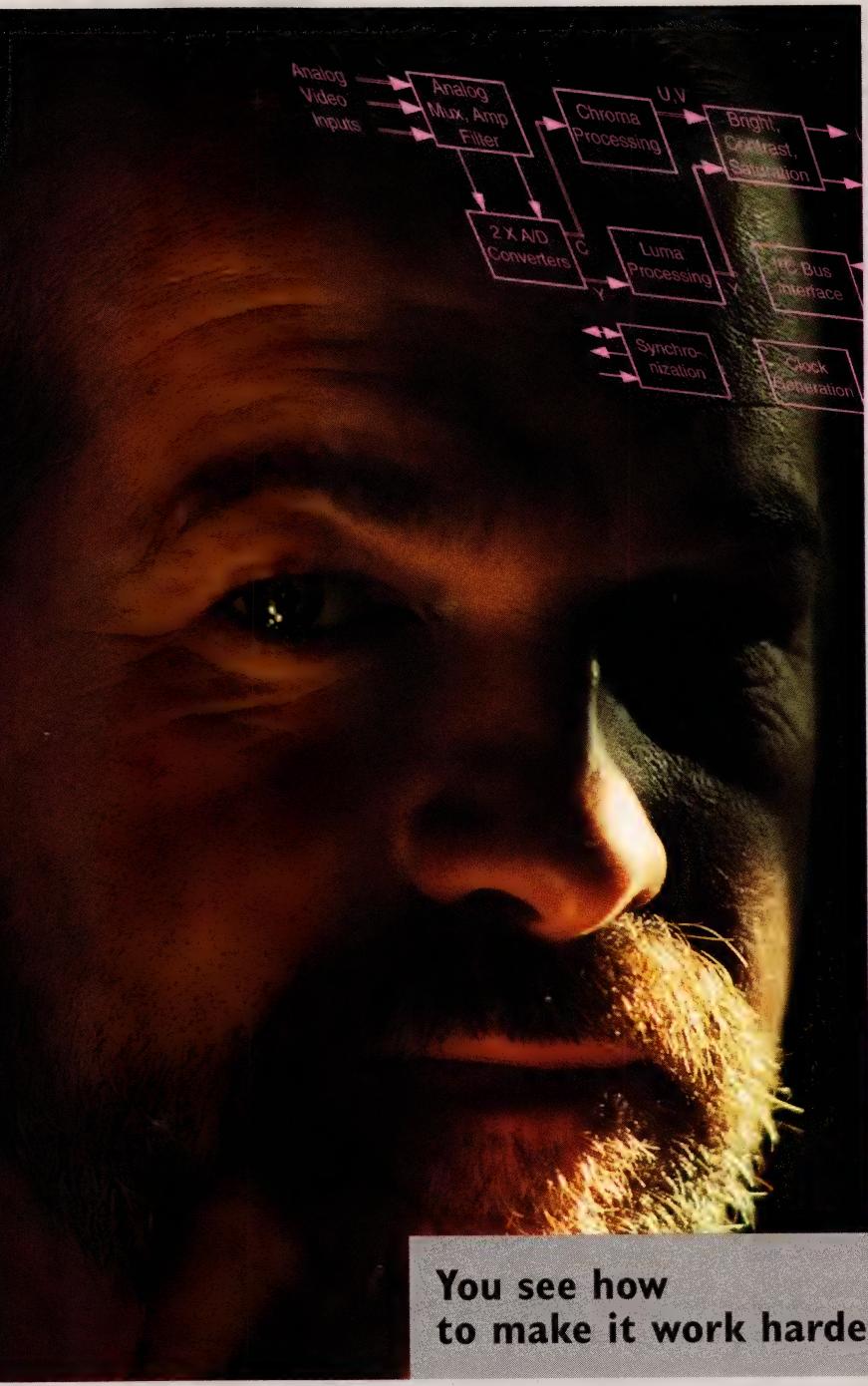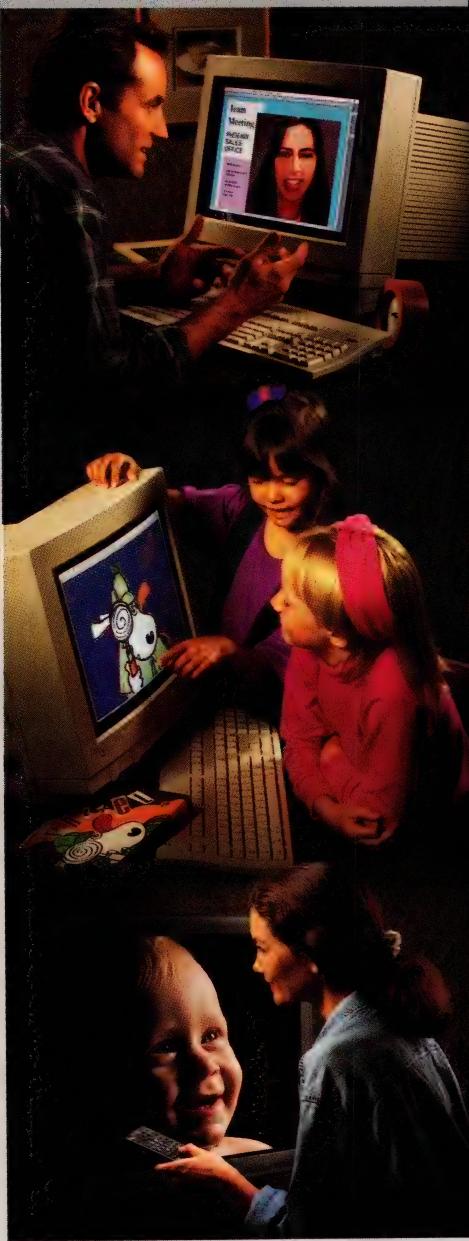

**You see how
to make it work harder.**

Which is where Philips enters the picture.

SAA7116
By applying the experience and innovation that made us the leader in video digital encoders and decoders, Philips is expanding into new areas that can turn up the volume on your video ideas.

Our new SAA7116 PCI bus interface is a perfect example. It lets you stream full-bandwidth video onto a PC motherboard. Just think of the possibilities.

Another example is our new SAA7140 high-performance scaler with two-dimensional phase-correct interpolation and double-programming settings. And the list goes on.

So call Philips today and get the full story. We'll help you translate your personal vision into video wonder.

I-800-447-1500, ext. 1141



**Philips
Semiconductors**

© Philips Electronics North America Corporation, 1994



PHILIPS

DESIGN SUPERCON'95

The Conference about Putting Technology to Work
"Design Expertise for Designers"

February 28 to March 2, 1995

Santa Clara, CA

LAST CALL!

Call for Papers

Co-developed by EDN and Hewlett-Packard Co

HIGH-PERFORMANCE SYSTEM DESIGN CONFERENCE

Authors are invited to submit abstracts, biographies, and/or completed papers on recent advances, practical design techniques, and case studies in the design of advanced digital systems. Areas of interest include, but are not limited to:

■ HIGH-PERFORMANCE COMPUTING ARCHITECTURES

- Multiprocessing
- Reconfigurable hardware
- 100+MHz microprocessors
- ESDA (practical aspects)
- Packaging effects on architecture design
- Memory/cache design

■ REAL-WORLD EFFECTS ON DIGITAL SYSTEMS

- Signal integrity
- Practical pc-board layout techniques
- Electromagnetic interference (EMI)
- Clock distribution
- High-speed packaging effects
- Metastability

■ HIGH-SPEED DATA MOVEMENT

- High-performance bus design (PCI bus, EISA, VL)
- Using high-speed serial links
- I/O-system design
- Driver/interconnect effects on high-speed data movement
- Timing analysis and verification
- Optimizing mass-storage communication

■ HIGH-PERFORMANCE EMBEDDED DESIGN

- DSP supplanting traditional CPU
- Graphic-system design
- Image processing
- Debugging high-performance embedded systems
- Embedded hardware/software integration
- CASE for embedded system design

Note: Existing papers in the areas of interest should be sent along with the abstracts/biographies.

SUBMISSION INSTRUCTIONS

Send six copies of your abstract, biography, and double-spaced, double-sided existing papers to:

Markus Levy**EDN Magazine**

1936 Sheffield Drive

El Dorado Hills, CA 95762

EMAIL: EDNLEVY@MCIMAIL.COM

Phone: (916) 939-1642


Fax: (916) 939-1650

(Please do not submit papers by fax)

EDN**HEWLETT
PACKARD**

Beat The Board Hogs

With the First SMT 128K x 32Bit SRAM

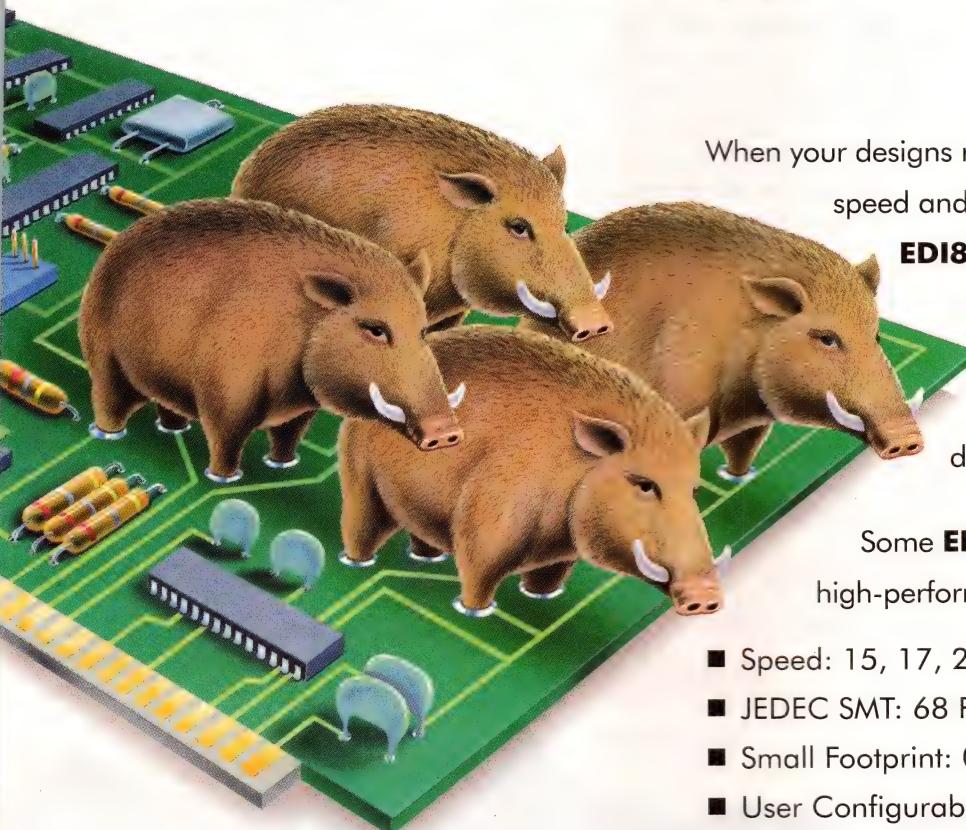

When your designs require more memory,

speed and board space, the new

EDI8L32128C-AC is the answer.

Our high density memory
array solution doubles the
efficiency of your board
design - in *half* the space.

Some **EDI8L32128C-AC**

high-performance advantages:

- Speed: 15, 17, 20 and 25ns
- JEDEC SMT: 68 Pin PLCC
- Small Footprint: 0.990 sq. inches
- User Configurable Organization
- High Density 4 Mbyte CMOS SRAM

Achieve the greatest memory efficiency
without hogging your valuable board design.
Give us a call today for samples and
application information.



Better performance than four
128K x 8 PSOs in half the space

New Memory Databook now available.

508-366-5151 ext. 214

EDI is ISO9001 Certified



Electronic Designs, Inc.

One Research Drive • Westborough, MA 01581 USA Tel: 508-366-5151 • Fax: 508-836-4850

Electronic Designs Europe, Ltd.

Shelley House, The Avenue • Lightwater, Surrey GU18 5RF United Kingdom • 0276 472637 • Fax: 0276 473748

CIRCLE NO. 32

EDN September 29, 1994 • 19

FAST Track to FAST SCSI

90's Challenges. The 90's demand higher levels of performance and faster delivery than ever. Time-to-market, technological demands, and changing user needs make fast, simple SCSI seem as elusive as the horizon. To stay ahead in these challenging times, you need products you can count on, with proven ability to deliver the quality and reliability your customers require.

90's Products. After over a decade of industry leadership, NCR is still working hard to meet your needs and the challenges of the 90's. The NCR 53C90 family of SCSI Controllers is constantly evolving, implementing and offering state-of-the-art products. For example, the NCR 53C90 family supports multiple bus architectures, advanced SCSI-2 commands, fast SCSI data transfers and provides our exclusive TolerANT® SCSI driver and receiver technology, for reliable data transfers in every SCSI system.

90's Solutions. The SCSI challenges of the 90's can't be solved with silicon alone. Quality and service provide you with the competitive edge that can make your industry leading designs a reality. Whether you require SCSI-1 or fast SCSI-2, in any system architecture, NCR has the products to meet your needs today. You can count on us to keep you on the fast track with the right technology, at the right price, at the right time for all your SCSI requirements.

The NCR 53C90 Family

*Proven Performance
for the 90's and
Beyond*

CIRCLE NO. 88



NCR SCSI: Real Products, Real Solutions, Real Fast!

SCSI	FAST SCSI*	
53C90A	53CF90A	Single-bus architecture; SCSI sequences controlled by hardware state machine to minimize host intervention
53C90B	53CF90B	Adds pass-through parity for increased system reliability
53C94	53CF94	Adds split-bus architecture for more flexibility
53C96	53CF96	Adds support for differential transfers

*NCR Fast SCSI devices transfer SCSI data at 10 MB/s synchronous or 7 MB/s asynchronous

For more information about NCR SCSI products and a free poster, call 1-800-334-5454.





What users want is assurance that, by adopting VXI, they are placing their bets on a leading-edge technology that has staying power.



Jesse H. Neal
Editorial Achievement Award
1990 Certificate, Best Editorial
1990 Certificate, Best Series
1987, 1981 (2), 1978 (2),
1977, 1976, 1975

American Society of
Business Press Editors Award
1994, 1991, 1990, 1988, 1983,
1981

VXI: One big, happy family at last?

"We must all hang together, or assuredly, we shall all hang separately," said Benjamin Franklin more than two centuries ago. In a similar spirit, the VXI Plug-and-Play Systems Alliance welcomed its newest members at a meeting in Austin, TX, in mid-July. Among the seven companies joining the alliance is the group's largest and, arguably, most influential member—Hewlett-Packard. Market researchers claim that HP has captured 38% of the revenues for VXI instrumentation, the largest share of any vendor. HP owes its lead to many factors, not the least of which is its broad line of VXI hardware.

Notwithstanding a strong VXI software entry, the VEE graphical programming system (available both for Unix workstations and Windows PCs), HP's share of VXI software sales is not the largest. Software market-share honors go to National Instruments. NI's VXI products include LabWindows for MS-DOS, LabWindows/CVI for Windows PCs and Sun Workstations, and the LabView graphical programming system for the Macintosh, Windows PCs, and Unix workstations.

About a year ago, several companies formed the VXI Plug-and-Play Alliance. Alliance founders realized that for VXI to make good on its early promise, VXI systems integrators had to be able to put together systems using components from any VXI vendor and be assured that the hardware and software would play together. If problems developed, users would not tolerate a group of vendors who pointed fingers at each other. By spring of this year, the Alliance membership had grown to nearly 20 VXI vendors.

Whether or not the perception was correct, the formation of the Alliance created an impression that the VXI community was polarizing into two camps. One camp, comprising Alliance members, was headed by National Instruments with its lead in VXI software. The other camp, headed by HP, offered a broad line of high-quality hardware and credible software. Within either camp, the level of compatibility was high, although not as high as necessary. Between camps, even if outright animosity

didn't exist, the level of compatibility was unacceptable.

The problem with this state of affairs was that the VXI community could ill afford to rend itself asunder. Despite some attractive competing technologies, a united VXI community can succeed. But VXI would mortally wound itself if vendors tried to gain the upper hand by labeling certain VXI products inferior because of incompatibilities with their own products. Such an approach would not only dissipate the energies of VXI vendors; it would send precisely the wrong message to potential users. What users want is assurance that by adopting VXI, they are placing their bets on a leading-edge technology that has staying power. Users want to know that their investment will be preserved by the continued availability of products and support services from a wide variety of vendors. To achieve a lower cost of ownership over the life of their systems, these users will pay a premium for initial purchases.

Now that the VXI Plug-and-Play Alliance has set the stage for cooperation among all VXI vendors, the vendors must deliver on that promise. HP, the company with the most resources, faces the biggest challenge: producing C-language versions of several hundred instrument drivers. The new drivers, which will be just as compatible with VEE as HP's current drivers, will also be compatible with LabWindows/CVI. Indeed, HP may get help in this effort from National Instruments, because NI already has LabWindows/CVI drivers for many HP VXI modules. The result will be that users of HP hardware will be able to use NI software—if they choose to, and vice-versa.

What transpired in mid-July in Austin was surely a watershed event for VXI. But its significance for the rest of the industry is even greater. VXI began in 1987 with a spirit of cooperation among competitors who realized that their own interests would be served if they placed customers' interests first. Just when it looked as if that spirit of cooperation was unraveling, the VXI Plug-and-Play Alliance resurrected it with a vengeance.

How much time must pass before other electronics market segments realize that this type of customer-focused cooperation can also pay big dividends to vendors?

DAN STRASSBERG, SENIOR TECHNICAL EDITOR

Send me your comments via fax at (617) 558-4470, or on the EDN Bulletin Board System at (617) 558-4241, 300/1200/2400 8,N,1. From the Main System Menu, enter ss/soapbox and select W to write us a letter.


7.5ns

Nanoseconds Ago How AMD Has Improved

The New MACH® Family Gives You 7.5ns Speeds,
Plus The Design Tools You Need To Get To Market Faster.

You can never be too fast.
Or too well equipped, for that matter.
And the new MACH CPLDs give you both:
The speed you need for the critical path
— up to 7.5ns. Plus a whole new set of
design tools you'll need along the way.

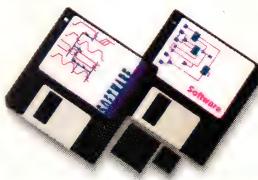There's nothing faster than the new
members of our MACH family. Our 1800-



The new MACH family members feature speeds up to 7.5ns, while our new software tools include schematic design entry and timing simulation capabilities.

gate MACH 210A-7 clocks-in at 7.5ns, while
our 3600-gate MACH 230-10 reaches 10ns.
Now that's fast.

And you'll bring your product to market
in record time with AMD's new software
offerings. Now you can get your favorite
design tools — including MicroSim, Data
I/O® and Viewlogic™ — directly from AMD.



You Can't Measure Speed. You've Seen The MACH Family.

You get the right tools, right away.

If you need additional design support, you can always rely on our FusionPLD™ partners, a team of vendors ready and waiting to give you the support you need when speed is of the essence.

What's more, AMD delivers both JTAG testing and 5-Volt in-circuit programming. So you have the flexibility to test, program, and reconfigure your designs right on the board. And both capabilities are an integral part of our free in-circuit programming kit.

So call AMD today for more information on the

entire high-speed MACH family, design tools, and our free 5-Volt in-circuit programming kit. Because with AMD behind you, you'll finish faster every time.

800-222-9323



Ask for our free
programming
kit 19Q.




Advanced Micro Devices

ASIC TEST IT'S A NEW BALL GAME

DAN STRASSBERG, SENIOR TECHNICAL EDITOR

Testing ASICs means more than just designing for test. Although today's sophisticated DFT tools are a big step forward from earlier ones, intelligently tackling test requires a partnership between design and test—and designers' full appreciation of what test is all about.

Even if you think you know all you need to about ASIC test, don't turn the page quite yet. Sure, you know that, thanks to structured design methods, you can create chips of incredible complexity in less time than it took to develop devices only one-tenth as complex just a few years ago. And you probably also know that, in some cases, structured design-for-test (DFT) techniques can reduce creating test patterns to a pushbutton operation that takes less than a day on a workstation. A few years ago, pattern generation, performed manually, was a tedious, error-prone ritual that could consume months.

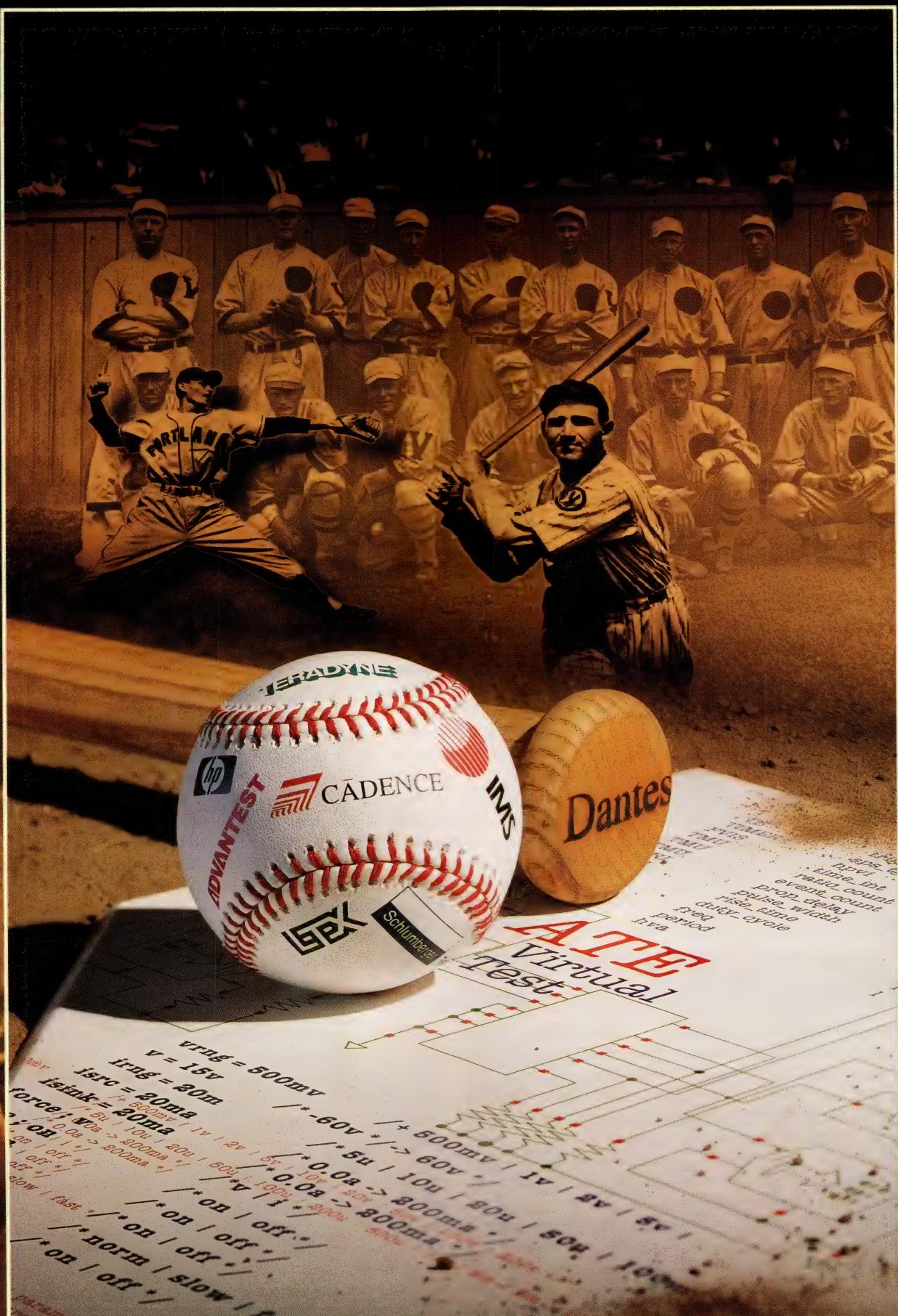


PHOTOGRAPHY COURTESY CADENCE / IMS

ASIC TEST

That's the good news about ASIC test. But there is a dirty little secret too—a part that too many design engineers have tried to pretend doesn't exist: Making sure before you have silicon that the devices will be testable when silicon finally arrives requires much more than turning an automatic-test-pattern-generation (ATPG) package loose on the design. Test-development can still take months and, in the case of mixed-signal ICs, sometimes stretches to over a year. But there's more good news: Suppliers of electronic-design-automation (EDA) tools and automatic test equipment (ATE) are introducing a host of products to automate dozens of tasks that are essential for developing adequate tests. Designers previously performed these tasks by hand.

These tools fit into a category called "virtual-test" (VT) tools. Cadence Design Systems was among the first to use the term in connection with IC test but has not applied for a trademark and has no plans to apply for one. Indeed, the company would be happy if other vendors began using the phrase. Marv Wolfson, vice president of Cadence's test-software business, thinks that such acceptance would enhance the concept's credibility. Nevertheless, because there is no universally agreed-upon scheme for categorizing EDA tools, Wolfson is concerned that other companies could confuse users by attempting to alter Cadence's meaning.

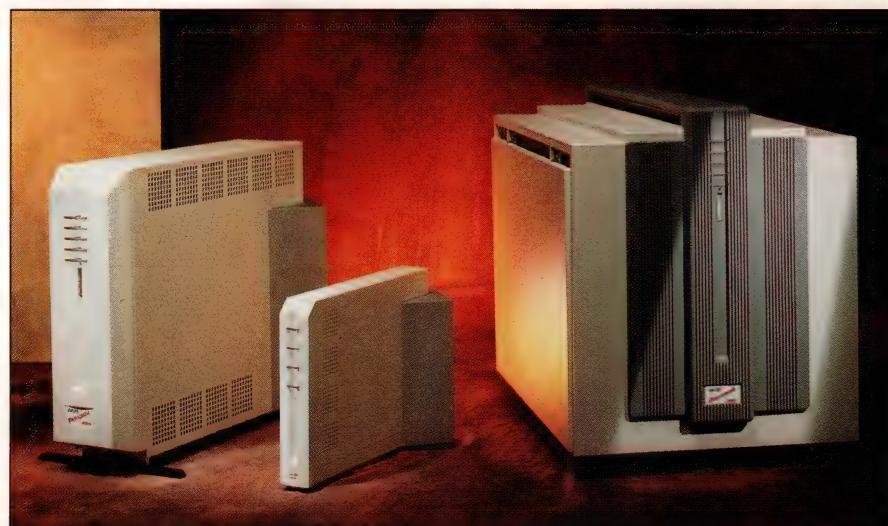That meaning is specific: VT tools allow test engineers to create, optimize, simulate, and debug test fixtures and device-test programs that can run on ATE systems. VT tools' main goal is to



Classical gate-level stuck-at fault simulation for circuits not designed with the use of DFT methodologies is inherently computation-intensive; the operation can take weeks, even on a powerful workstation. Specialized hardware accelerators, like these Paradigm XP units from Zycad Corp, can cut fault simulation times by as much as two orders of magnitude.

shorten product-development cycles through more efficient use of test-engineering resources. The tools, which begin by taking input from the device's design database, allow users to complete most test development *before* silicon becomes available *without* tying up scarce and expensive ATE.

An added benefit is the tools' ability to reveal device-design problems that affect testability. Through VT, users can demonstrate that devices are testable *before* transmitting the designs to a foundry. Designers who learn about test problems soon enough can modify their designs to eliminate the need for costly work-arounds or even costlier mask redesigns. VT recognizes

that the roles of design and test engineers are complementary and that test engineers are designers, albeit not of products—but of the fixtures, test programs, and procedures that make possible economical production of high-quality products.

Don't be confused by the seeming similarity between VT tools and a more familiar type of EDA tool, the design-rule checker. To be sure, both types of packages help to ensure testability, but design-rule checks occur earlier in the design cycle—before the insertion of the chip features that provide testability. Design-rule checking aims to verify that automatic test-structure insertion packages can, in fact, add features that

THE TORTUOUS PATH TO IC QUALITY

"Tortuous:" the dictionary defines it as "winding, twisted...complex." Electronic-design-automation (EDA) tool vendors have spent countless person-years developing tools that make the path to IC quality less tortuous. Although these efforts have achieved considerable success, the path is still not straight or smooth. Part of the reason is that most of the efforts focus on the first two categories in the test-development-automation tool list on the next page: design-for-testability (DFT) and pattern-development tools.

DFT tools in particular are used early in the design process. In most companies, the users are design engineers—the traditional audience for EDA products. Users of pattern-development tools are more varied. In some companies, test-pattern development is a design function. In other companies, the job

falls to test. In a few cases, netlist files go off to a foundry, and the foundry generates the test patterns.

Test engineers working in IC-fab facilities are most likely to use virtual-test (VT) tools. Although design verification and manufacturing test have different objectives, putting responsibility for VT too far from design can result in test programs that fail to find critical device defects. Despite the capabilities of the design-rule-checking packages used earlier in the design process, projects that wait too long to use VT tools miss a golden opportunity to correct design flaws while they can still be corrected at moderate cost. Undoubtedly, the probability that both the first silicon and the first iteration of the test program will work as desired improves dramatically as cooperation between design and test goes up.

provide high fault coverage. As part of creating test packages, VT tools can complement design-rule checking by proving that rule checking has achieved its goals.

The most appropriate term for the universe of tools involved in ASIC test is "test-development automation" (TDA) tools. (Some vendors use the term "test-automation," but the tools, most of which are software, don't automate testing; ATE does that. The tools automate various aspects of test development.) The **box**, "The tortuous path to IC quality," and the **table**, "Test-development-automation tools," indicate the types of tools and their significance in test development. The listings should shed light on the roles of classes of tools. In the manufacturers' **box**, you'll find names of EDA suppliers that offer TDA tools as well as names of vendors of semiconductor ATE systems.

According to Ben Bennetts, senior test consultant at Synopsys, achieving a testable design for a digital IC involves the following five primary steps, which Bennetts attributes to Robert Aitken of Hewlett-Packard:

- Design-rule checking to make sure that the design conforms to the rules for the chosen DFT methodology or methodologies—full or partial scan, built-in self test (BIST), boundary scan, or IDDOQ (a technique for CMOS ICs that finds faults by measuring a chip's quiescent supply current, I_{DDQ}). The rule-check preconditions the circuit for the insertion of test structures that implement the chosen methodologies.
- Test-structure insertion—for example, conversion of D flip-flops into scannable latches. Test-structure insertion is often called "test synthesis"—another somewhat misleading term. Test synthesis doesn't synthesize tests; it synthesizes silicon structures that make it convenient to design tests.

- Global reoptimization to assure that the design that now includes test structures meets the original constraints on such factors as timing, area, output-drive capability, and power dissipation.
- Test-pattern generation, or the gen-

Although modern test-pattern generators include fault simulators, free-standing fault simulators can still be useful. Such simulators start with functional vectors (developed for design verification). These vectors provide structural-defect coverage without additional effort. Functional vectors usually provide 40 to 50% fault coverage and often catch timing-related faults. Whereas fault coverage of 40 to 50% is usually not adequate for production test, it can be a good starting point. Moreover, timing-fault coverage is something that scan-test vectors don't normally provide.

Even though these five steps go a long way toward assuring testability with a specified degree of fault coverage, they do not, in general, complete the job of producing a testable design. That job involves steps such as design and debugging of test fixtures and test programs. Although the test vectors that ATPG tools create are the most important elements of a test program, they aren't the program. Moreover, until you debug the test fixture and test program, design problems that affect testability may remain hidden. This is especially true when devices are complex or have appreciable analog or mixed-signal content or when the specifications push process limits or tax test-equipment capabilities.

An objective of virtual-test tools is to minimize the likelihood that the test fixture, test program, or ATE idiosyncrasies can interfere with valid and adequate testing. To be useful for this purpose, the tools must not add appreciable delays to the design cycle. Design engineers and program managers cannot tolerate a process that delays the transmission of a design to a

TEST-DEVELOPMENT-AUTOMATION TOOLS

Design-for-testability (DFT) tools (test-synthesis tools)

Testability-analysis tools
 Design-rule checkers
 PLD testability-analysis tools
 Stuck-at fault-simulation and vector-grading tools
 Hardware accelerators for fault simulation
 Delay-fault simulators

Test-structure insertion tools
 Boundary-scan-structure insertion tools
 Internal-scan-structure insertion tools
 Partial-scan tools
 BIST-structure insertion tools
 Regular-structure BIST insertion
 Random-logic BIST insertion
 Tools for inserting IDDQ-initialization structures

Pattern-development tools

ATPG
 Full-scan ATPG
 Partial-scan ATPG
 Sequential ATPG (Ed note: such as it is)
 Boundary-scan vector generators
 IDDQ vector-generation tools
 Tools for predicting IDDQ and setting test limits
 Vector-compaction tools

Virtual-test tools

EDA-related
 (Tools that support ATE from more than one supplier)
 Test-rule-checking tools
 Test-schematic-capture tools
 Test-documentation tools
 Tools for automating test-fixture design and layout
 Test-fixture-simulation tools
 Tester-resource-simulation tools
 Signal-analysis tools
 Format-conversion tools (also see tester-specific VT tools)

Tester-specific
 (Tools specific to particular ATE systems or systems from one supplier)
 Format-conversion tools (also see EDA-related VT tools)
 ATE system software
 Test-sequencing tools
 Test-optimization tools
 Test-debugging tools
 Test emulators (also called test-event simulators)
 Tools for off-line test-program development

eration of test patterns that, when applied to the circuit, make faults observable.

- Fault simulation and fault-coverage grading of test-vector sets. Fault-coverage grading, is commonly referred to as "fault grading," doesn't grade faults; it grades vector sets' ability to detect faults.

ASIC TEST

foundry by more than a few days.

However, the need to rush products to market is no greater than the need to turn over every stone when looking for device faults. Semiconductor test and process engineers often use the following equation to determine how high a test process' fault coverage must be. Although some of the assumptions underlying the equation are open to question (uniform density of defects across the wafer, for example), nobody

has come up with a technique for calculating required fault coverage that is easier to apply or in which reliability experts have more faith.

$$DL = 1 - (Y^{1-FC})$$

where DL=defect level (the portion of devices that pass the test but are, in fact, defective), Y=yield (the portion of all devices tested that are good), and FC=fault coverage (the fraction of all

possible faults that the test can find).

$$\begin{aligned} \text{If } DL = 1000 \text{ ppm} &= 0.1\% = 10^{-3} \text{ and} \\ FC &= 0.9, \\ 10^{-3} &= 1 - (Y^{0.1}) \\ Y &= 0.991. \end{aligned}$$

Thus, if the fault coverage is 90% and you can't tolerate more than 0.1% bad devices' getting through your test process, you must be confident that the manufacturing process (before testing)

MANUFACTURERS OF TEST-DEVELOPMENT-AUTOMATION TOOLS

For free information on test-development-automation tools such as those discussed in this article, circle the appropriate numbers on the postage-paid Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you read about them in EDN.

Accugen Software Inc
Nashua, NH
(603) 881-8821.
Circle No. 301

Advantest America Inc
Fort Lee, NJ
(201) 886-0300
Circle No. 302

Altium, an IBM Co
San Jose, CA
(408) 534-4100
Circle No. 303

Ando Corp
Sunnyvale, CA
(408) 991-6700
Circle No. 304

Arkos Design Inc
Scotts Valley, CA
(408) 461-8100
Circle No. 305

AT&T Design Automation
Murray Hill, NJ
(908) 582-4083
Circle No. 306

Attest Software Inc
Santa Clara, CA
(408) 982-0246
Circle No. 307

Cadence Design Systems Inc
Beaverton, OR
(503) 626-7117
Circle No. 308

Chrysalis Symbolic Design Inc
Andover, MA
(508) 475-7700
Circle No. 309

Compass Design Automation
San Jose, CA
(408) 434-7852
Circle No. 310

Corelis Inc
Cerritos, CA
(310) 926-6727
Circle No. 311

Credence Systems Corp
Fremont, CA
(510) 657-7400
Circle No. 312

CrossCheck Technology Inc
San Jose, CA
(408) 432-9200
Circle No. 313

Eagle Test Systems Inc
Mundelein, IL
(708) 367-8282
Circle No. 314

Flynn Systems Corp
Nashua, NH
(603) 891-1111
Circle No. 315

Hewlett-Packard Co
Santa Clara, CA
(800) 452-4844
Circle No. 316

Ikos Systems Inc
Cupertino, CA
(408) 255-4567
Circle No. 317

Integrated Measurement Systems Inc
Beaverton, OR
(503) 626-7117
Circle No. 318

JEH Consulting Inc
Monument, CO
(719) 488-3454
Circle No. 319

JTAG Technologies BV
Eindhoven, The Netherlands
31-40-782-584
Circle No. 320

Logical Solutions Technology Inc
Campbell, CA
(408) 374-3650
Circle No. 321

LSI Logic Corp
Milpitas, CA
(408) 433-8000
Circle No. 322

LTX Corp
Westwood, MA
(617) 461-1000
Circle No. 323

Megatest Corp
San Jose, CA
(408) 437-9700
Circle No. 324

Mentor Graphics Corp
Wilsonville, OR
(503) 685-7000
Circle No. 325

Micro Component Technology Inc
San Jose, CA
(408) 432-3200
Circle No. 326

MOSAid Systems Inc
Santa Clara, CA
(408) 727-7199
Circle No. 327

Motorola Inc
Phoenix, AZ
(602) 994-6561
Circle No. 328

Schlumberger Technologies
San Jose, CA
(408) 437-5129
Circle No. 329

Simutest Inc
Sunnyvale, CA 94086
(408) 720-9427
Circle No. 330

Summit Design Inc (formerly TSSI)
Beaverton, OR
(503) 643-9281
Circle No. 331

Sunrise Test Systems Inc
Santa Clara, CA
(408) 980-7600
Circle No. 332

Synopsys Inc
Mountain View, CA
(415) 962-5000
Circle No. 333

S-Z Testsystems
Sunnyvale, CA
(408) 749-8797
Circle No. 334

Teradyne Inc
Boston, MA
(617) 422-2567
Circle No. 335

Teradyne Inc
Agoura Hills, CA
(818) 991-2900
Circle No. 336

Texas Instruments Inc
Dallas, TX
(214) 575-6396
Circle No. 337

Viewlogic Systems Inc
Marlborough, MA
(508) 480-0881
Circle No. 338

Zycad Corp
Fremont, CA
(510) 623-4551
Circle No. 339

VOTE . . .
Please also use the Information Retrieval Service card to rate this article (circle one):

High Interest 598
Medium Interest 599
Low Interest 600



Super Circle Number

For more information on test-development automation tools available from all of the vendors listed in this box, you need circle only one number on the postage-paid reader service card.

Circle No. 340

SHRINK YOUR WIRELESS DESIGN AND YOUR COSTS WITH HARRIS SILICON RF ICs.

Squeeze ounces and inches out of your next wireless project – and dollars out of your cost budget – with new RF front end ICs from Harris. Our HFA3600 LNA/Mixer gives you low-power, low-noise 900 MHz performance in 40% less space than discretes. Yet they cost just \$1.82 each in 5000 piece quantities. And it's part of a whole family of high-performance, low-cost Harris silicon RF ICs, including our HFA3102 Dual Long-Tailed Pair Transistor Array and HFA3101 Gilbert Cell. They all pack a lot of product into a package that's compact – with a price to match.

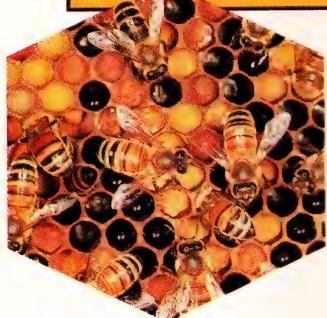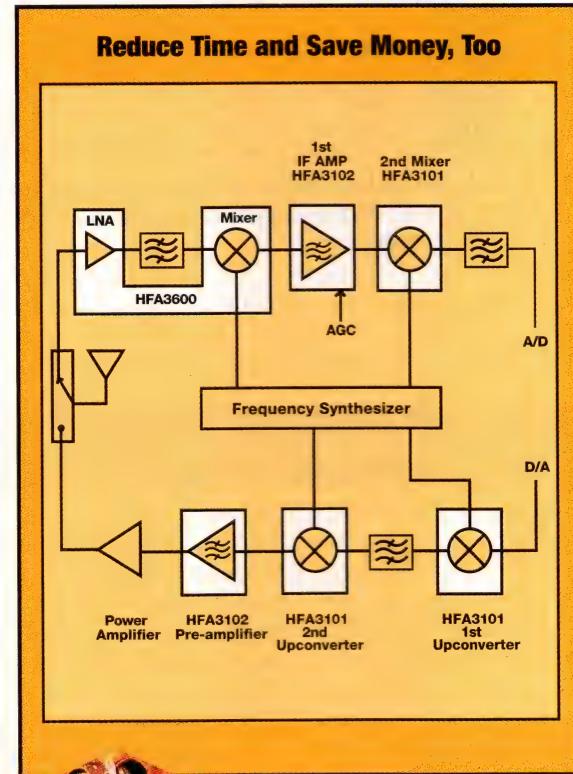

As with the HFA3600, the honeybee packs a lot of potential in a small package and the rewards are inexpensively sweet.

Features

HFA3600 LNA/Mixer

- Power consumption: 11mA @ 5V, 1.2 mW (sleep mode)
- LNA noise figure: 2.3dB
- Mixer OIP: +3.2dBm
- Integrated 50Ω matching
- Integrated power down function
- Just \$1.82 (5000s)

HFA3102 Dual Long-Tailed Pair Transistor Array and HFA3101 Gilbert Cell

- Power Gain Bandwidth: 5 GHz
- Current gain: 70
- Excellent hfe and Vbe matching
- Just \$1.80 (5000s)



Call 407-724-3818 and request documents:
3655(HFA3600), 3635(HFA3101), 3663(HFA3102).
Or call 1-800-4-HARRIS and ask for extension 7266.


ASIC TEST

yields at least 99.1% good devices.

If $Y=0.8$ and $FC=0.9$, $DL=0.022$.

In other words, if the fault coverage is 90%, and 80% of the devices you send to test are good, 2.2% of the devices that test tells you are good, are, in fact, defective.

In today's market, few applications can tolerate defect levels as high as 1000 ppm, let alone 2.2%. Most applications, even commercial ones, require defect levels no higher than 200 ppm. The message is clear: 90% fault coverage is rarely adequate. Adding to the problem of achieving adequate fault coverage is the assertion that devices that purportedly can be tested with 100% fault coverage using scan-test vectors actually achieve fault coverages no higher than the low 90% range when tested with functional vectors. If this assertion is correct and if the faults detected in functional testing are not delay faults—which scan does not claim to catch—the allegation that scan-test vectors provide less than 100% coverage raises doubts about the

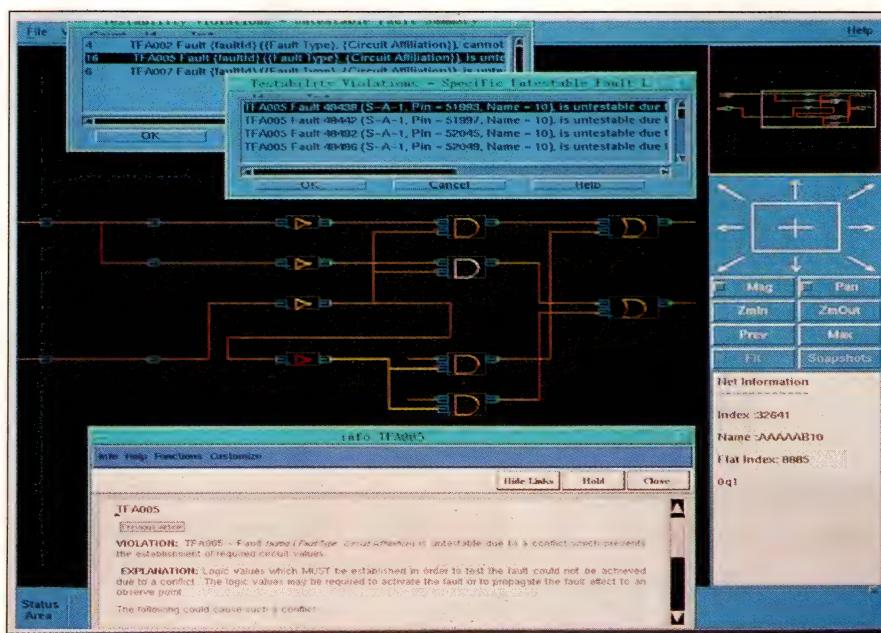

Packages such as TestBench from Altium perform design-rule checks. In this screen, the graphic display indicates a conflict that prevents a fault from being activated or propagated.

effectiveness of scan methodologies.

Because no single test method reveals every fault, if you need a low rate

of test escapes (defective devices that escape detection in test), you need to use a combination of test methodolo-

LOOKING AHEAD

In IC test, as in so many other areas of electronics, a wonderful synergy is developing. That synergy—between structured design and test-development automation (TDA)—will make test development faster and easier and will make testing more effective. Alas, though, like nearly everything else the electronic-design-automation (EDA) industry touches, new, improved, TDA tools are unlikely—at least at first—to live up to vendor promises. (Users would have walked away long ago from most industries with the EDA industry's sorry record of overpromising. EDA users have little choice, however; they can't do their jobs without EDA tools. Fortunately, EDA vendors usually deliver promised tools to those who can wait long enough.)

The most important incentive to implement TDA is the continuing march toward greater IC complexity. That march is possible only because of the use of top-down design methodologies. From a test viewpoint, top-down design can remove the designer too far from the gate level. But, since you really have to think at the gate level (and maybe even at the transistor level) to achieve good fault coverage, you have to look to new technologies to make sure that complex devices are tested adequately. The new technologies are automatic test-structure insertion (test synthesis) and automatic test-pattern generation (ATPG).

Test synthesis and ATPG aren't panaceas, however. For exam-

ple, many informed industry observers doubt that ATPG will ever become a reality for sequential circuits. And, except when used on designs for relatively simple devices of moderate performance, ATPG doesn't come close to doing the whole test-engineering job. Thus, virtual-test tools should become important components of test engineers' arsenals. Marketing those tools effectively poses a challenge to the EDA industry, however.

With the exception of a few companies, EDA companies do not have close ties to test engineers. (Summit Design—formerly TSSI—is probably the most notable exception. Cadence, thanks to its ownership of ATE vendor Integrated Measurement Systems—IMS—is another.) The challenge for EDA companies is to develop the ties with test engineers that they already enjoy with design engineers. Clearly, EDA vendors have been courting the test community; for several years, many EDA companies have been highly visible at the International Test Conference. (The 1994 edition of the conference will take place on Oct 3, 4, and 5 in Washington, DC.)

Nevertheless, any EDA vendor that seriously intends to do business with the test community must do more than appear at industry events. A word of advice to the vendors seems appropriate here: If you think design engineers are cynics, get to know a few test engineers! The way to test engineers' hearts definitely is *not* through excessively optimistic product-performance and delivery claims.



**Finally, a 3-volt PLD
fast enough to work
right alongside
today's CPUs.**

With a propagation delay of just 7.5ns, the new LVT22V10 is far and away the world's fastest 3-volt PLD.

Its blazing speed is the only thing that keeps pace with today's high-performance 3-volt CPUs. And it's also loaded with critical functionality. Like low ground bounce (<0.8V_{OLP}). Live insertion for on-line systems. Flexible 3/5V mixed system support. And a variety of packages and temperature ranges.

LVT22V10

One key to this performance breakthrough is Philips' unique QUBiC BiCMOS process. It allows us to create a true 3-volt PLD, not a retrofitted 5-volt IC. But we're not stopping here. Keep an eye in the sky for a full squadron of 3-volt PLDs.

And don't wait. Our 3-volt PLD lets you fly with today's CPUs right now. Get more information and an LVT22V10 sample kit with one call.

I-800-447-1500 ext. 1139

**Philips
Semiconductors**



PHILIPS

ASIC TEST


gies: full scan on portions of the chip that are amenable to full scan, partial scan elsewhere, boundary scan on the I/O lines, BIST on structures such as RAM, IDDQ to detect faults that elude the other methodologies, and possibly some delay-fault testing. Although such a mixed approach may sound too complex to be practical, industry experts are nearly unanimous on its validity. Moreover, with the right suite of test-development tools, you can achieve high fault coverage more easily by mixing methodologies than by doggedly applying a single, sometimes inappropriate, approach.

IDDQ is a promising technique. Thanks in part to a well-documented study that has become an industry classic (Ref 1), the approach is starting to see broad application. IDDQ has several advantages: It imposes minimal constraints on chip designers. Although it may be advisable to add structures to the silicon that initialize the chip for IDDQ tests, such structures aren't mandatory. Creation of IDDQ vectors requires minimal knowledge of a chip's operation. You need no more than a few hundred IDDQ vectors to provide high fault coverage—even for chips with half a million gates. And, although definitive studies are still lacking, several people familiar with the technology expect to see a high correlation between I_{DDQ} and delay faults.

That's the good news about IDDQ testing. The bad news is that, today, the tests are so time-consuming that few foundries apply more than a small fraction of the IDDQ vectors needed to achieve high fault coverage. (The number of vectors applied usually is under 20. Such limited IDDQ tests act as an adjunct to functional and scan tests.) IDDQ tests are slow because you must measure tiny currents—microamps at most—and, on ATE systems, only the slow pin-measurement units can perform the task. Help is on the way, though. An industry group called QTAG (the name was adapted from JTAG, the Joint Test-Action Group that ultimately became the IEEE-1149 Boundary-Scan Committee) will shortly announce a design for a bipolar current-to-voltage-converter IC housed in an eight-pin SOIC package that test engineers can mount on device-under-

test (DUT) boards. The IC significantly speeds IDDQ testing by supplying a voltage proportional to I_{DDQ} that ATE systems' high-speed hardware can measure.

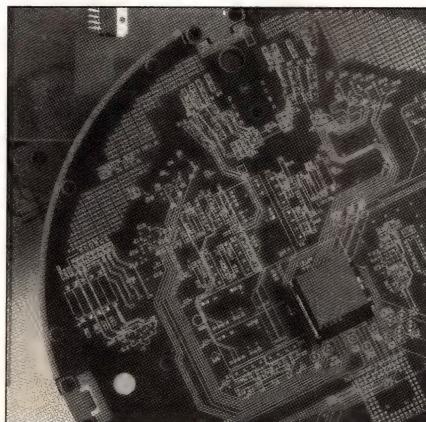A second problem with IDDQ is that setting test limits often involves a trial-and-error process, which, in turn, requires actual devices. However, soft-



With high-performance and mixed-signal ICs, designing for test involves more than developing a set of test vectors. A critical component is the board that connects the device under test (DUT) to the automatic test system. Teradyne's A500 series test systems for analog VLSI ICs use boards like these.

ware to predict the levels of I_{DDQ} in good devices should arrive soon, allowing designers to set test limits accurately before the arrival of first silicon.

Still only a few VT products

Whereas nearly half of the types of TDA tools fall into the VT category, less than half of the available TDA products are VT tools. VT tools complement—but do not replace—the more classical DFT and ATPG tools. To be sure, designs of certain types—mixed signal, for example—need VT more than do other types of designs. The most ambitious EDA-related VT tool is probably Cadence's Dantes (an acronym derived from design and test engineering system) for analog and mixed-signal designs.

Version 2.0 of the two-year-old tool will debut at the 1994 International Test Conference in October. Among its capabilities is test-rule checking to make sure that proposed tests do not ask the test equipment to do things it can't do. This capability assures, for example, that you

don't ask a voltage source to slew faster than its specified maximum rate. Dantes also provides several features to aid in documenting test setups and parameters; it can accept input in the form of test schematics. Moreover, it automates the layout of test fixtures such as DUT boards.

Dantes lets you simulate these boards, including their parasitic inductances and capacitances. Thanks to the cooperation of ATE vendors, Dantes also permits simulation of the resources of mixed-signal test systems. These resources include such components as voltage/current sources, measurement subsystems, and switch matrices. Coupled with design data on the device to be tested, this simulation capability lets you accurately predict how a device will behave on a real tester.


Even after you simulate individual tests, you don't have a complete test program; you have a collection of tests. Although you might think that a test program is nothing more than such a collection, that isn't the case. Transforming the tests into a working program involves a bit of science and a bit of art. This is where tester-specific VT tools enter the picture.

Test-sequencing tools (one type of tester-specific tool) attempt to minimize test time by looking at the tester and device states at the end of each test to make sure that a minimum number of things must happen before the next test can run. Here, "things" means vectors that must be applied to the DUT or commands that must be executed to make various tester resources ready for the next test.

Even when test sequences are determined in the manner described above, throughput is not necessarily maximized. Tests that devices are most likely to fail should run first. This minimizes the time spent testing devices that will ultimately be rejected. Test-program-optimization tools attempt to strike a balance between tester- and device-state considerations and the likelihood that devices will fail individual tests.

Another part of test-program optimization is binning of devices. Binning is more of a concern with standard analog and mixed-signal parts than with most ASICs. Vendors often sort analog ICs into multiple performance grades,

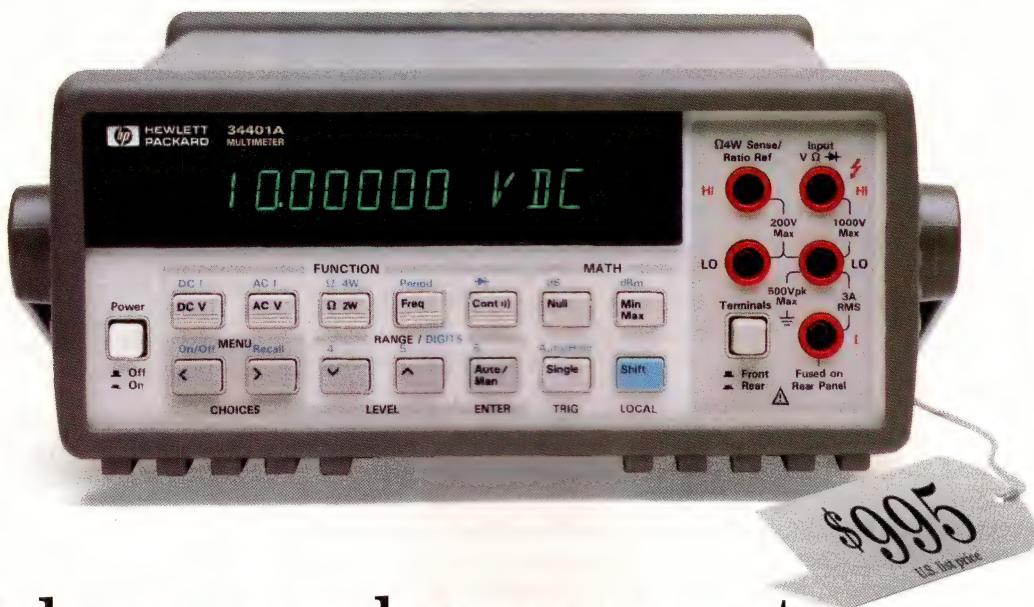There are a number of reasons this HP DMM outperforms a Fluke.



Pick any number you want.

Price & Performance	HP 34401A	Fluke 8842A/059
Digits	6 1/2	5 1/2
Price	\$995*	\$1570**
Speed (readings/second)	1,000	100
dc 1 Year Accuracy	0.0035%	0.0030%
ac 1 Year Accuracy	0.06%	0.08%
ac Bandwidth	3 Hz to 300 kHz	20 Hz to 100 kHz

Features & Functions	HP 34401A	Fluke 8842A/059
Measurement Functions	12	5
Programming Languages	Fluke 8840A/42A, SCPI, HP 3478A	Fluke 8840A/42A
Internal Storage	512 readings	none
Interfaces	HP-IB, RS-232	GP-IB
Warranty	3 Years	2 Years

The numbers are clear: you get performance within budget, without compromise.

For less than the cost of 5½ digits from Fluke, you can have the 6½ digit HP 34401A. And with more than twice as many measurement functions, you'll have more ways to tackle your test challenges.

Looking for speed? Technology leveraged from our 8½ digit DMM and custom ICs deliver up to 1,000 readings every second. That's up to 10 times faster than the Fluke.

Add up the numbers... lower price, higher performance, more capability, plus a longer warranty.

Now the only other number you need is the one on our telephone.

Call HP DIRECT and discuss your application with an experienced engineer who understands the measurements you need to make. We have hands-on experience with HP instruments, and we can help with everything from comparing specs to solving specific test needs. And ask about HP 34812A BenchLink/Meter software, a \$150* solution that makes it easy to transfer data from your HP 34401A DMM to a PC.

"Call me at HP DIRECT to discuss the best DMM for your application.

**1-800-452-4844,
Ext. 8632."**



* U.S. list price as of 7/94.

** Price includes GP-IB and ac options.

All Fluke prices and specifications are as of 6/94.

There is a better way.

**hp HEWLETT®
PACKARD**

CIRCLE NO. 86

ASIC TEST

but binning can also affect digital ICs—an example is µPs that are sorted into several speed grades. Binning strategies can influence test sequencing and throughput: You can save time when devices placed in lower performance categories need not undergo all tests.

A device can fail a test because the device is bad or because of problems with the test or the test program. Test-debugging tools provide visibility of the state of the tester, its individual resources, and, sometimes, the DUT itself to aid in determining what has gone wrong when the test results do not agree with the expected results.

Some observers of the IC-design scene comment that the role of the test engineer is becoming superfluous or that modern EDA tools are reducing the role of the test engineer to that of a technician. That is not the case. In reality, test engineers are design engineers. Instead of designing products, they design the fixtures, test programs, and processes that make possible the eco-



Motorola's PowerPC 603 µP has approximately 300,000 gates. Thanks to structured DFT methodologies, developing test vectors for the chip was not the big job you might think. Using tools from Mentor Graphics, Motorola engineers did the job in only a few days.

nomical, high-quality manufacture of products thought up by design engineers. New TDA tools offer test engineers power similar to the power that EDA tools place in the hands of design engineers. But for companies to derive the full benefit of TDA, design engi-

neers must develop more understanding of the evolving role of test engineering. And, most important, partnering between design and test must begin very early in the life of each project.

EDN

Reference

1. Maxwell, Peter C, R Aitken, V Johansen, and I Chiang, "The effectiveness of IDDQ, functional, and scan tests: How much fault coverage do we need?" *Proceedings of the International Test Conference 1992*, pg 168.

You can reach Senior Technical Editor Dan Strassberg at (617) 558-4205, fax (617) 558-4470, EDN BBS: EDNSTRAS. Internet: ednstrassberg@mcimail.com

VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest
598

Medium Interest
599

Low Interest
600

Sun Spark 5 workstations, AutoCad release 12,

**THERE ARE
SOME PRETTY
BIG NAMES
ON OUR BOARD.**


Cadence schematic capture, circuit simulation and
PCB design software, Internet Connectivity,
Altera Max + Plus II Development Systems,
PPG Electro Image Photoresist, Genrad.

compunetics, inc.

Engineering Systems Division

700 Seco Road, Monroeville, PA 15146 • (412) 373-8110
internet: jschmitt@well.sfc.ca.us

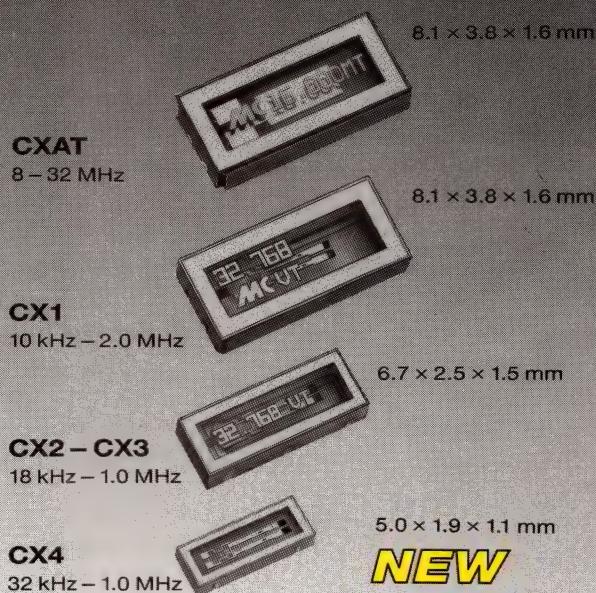THE EUROPEAN SOURCE OF MINIATURE SMD CRYSTALS



Micro Crystal
Div. of ETA SA
CH-2540 Grenchen
Switzerland
Tel. (065) 51 82 82 Fax (065) 51 82 83 A company of SMH

CIRCLE NO. 82

NEW DIMENSIONS IN DATA PRODUCTIVITY



**INTELLIGENT
INSTRUMENTATION™**

A Burr-Brown Company




WHAT'S INSIDE:

- PC-Based Data Acquisition
 - Software Page 1 - 4
 - Hardware Page 5 - 7
- Digital I/O Page 8
- Digital Signal Processing Page 9
- Multibus Page 9
- Operator Interfaces Page 10
- Bar Code Computers Page 10

FEATURES/BENEFITS

- Graphical, block-diagram development environment; requires no programming
- Context-sensitive, on-line help
- Analog and digital input up to 10MHz
- High-speed data streaming to disk
- Real-time data displays and controls
- Dynamic Data Exchange (DDE) with other Windows® programs
- Supports serial RS232, RS422, and RS485 communications
- Optional Visual Designer Custom Block ToolKit enables Windows programmers to add new block functions and support custom hardware
- Significantly reduces application development time

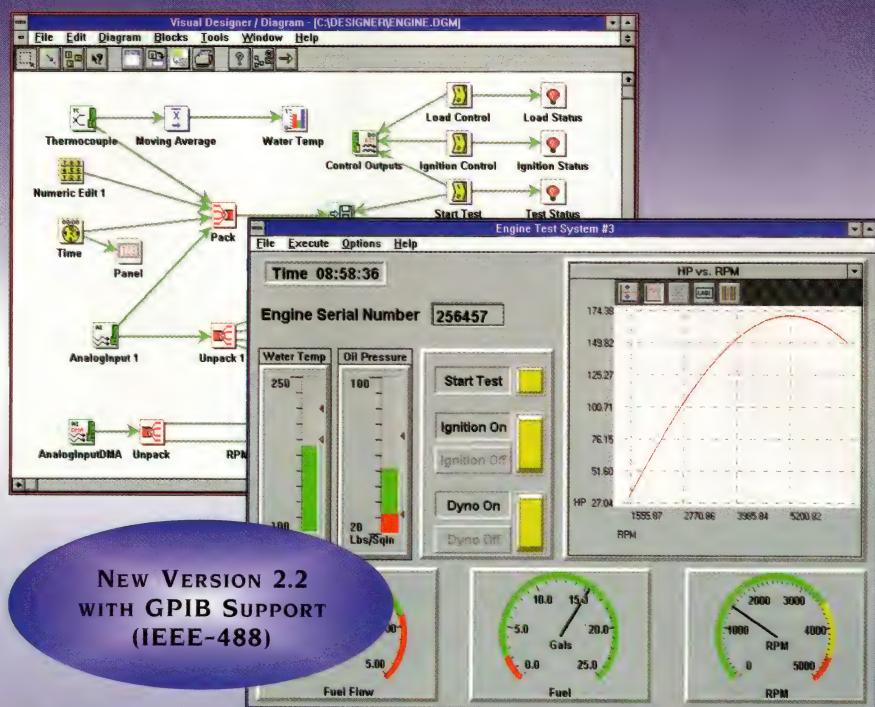VISUAL
DESIGNER

Visual Designer™ for Windows is a powerful, easy-to-use application generator for PC-based data acquisition, test, measurement and control. Designer takes you beyond programming to quickly create application software customized for your own requirements.

What sets Visual Designer apart from both traditional and graphical programming languages is its ease of use. With Designer, you simply build a block diagram of your application. Time-consuming programming is not required.

Visual Designer lets you capture, record, manipulate, analyze, display, and output data; control processes and devices; and create custom instruments with chart recorders, panel meters, oscilloscopes, spectrum analyzers, and more. You can use Designer over and over to generate any number of applications. And, any application that you develop with Designer for use with Intelligent Instrumentation's data acquisition boards can be distributed with a royalty-free license.

IDEAL APPLICATIONS

Visual Designer has hundreds of applications in the factory, field and laboratory. A few of the most popular are:

- Test Equipment – oscilloscopes, spectrum and waveform analyzers, power meters, chart recorders, specialized instruments
- Automotive – engine analyzers, emissions analyzers, specialized performance testers, test-track data logging
- Medical – EKG, EEG, biomedical research, patient monitoring
- Machine Monitoring – vibration analysis, quality control, temperature/pressure/stress/condition monitoring
- Environmental Monitoring – chemical analysis, air and water monitoring, environmental control
- Manufacturing – process monitoring & control, product testing, machine control
- Research and Development – data logging, experiment analysis, laboratory automation
- Power Utility Monitoring – power quality monitoring, event analysis, efficiency analysis

DESIGNER

AQUISITION APPLICATIONS



CIRCLE NO. 190

SELECT FROM VISUAL DESIGNER'S WIDE RANGE OF BLOCK LIBRARIES:

COMPARISON

Compare
Threshold Alarm
Window Alarm

DATA CONVERSION

Accumulate
Concatenate
Cut
Decimate
Delay
Modify Units
Multiplex
Pack
Type Conversion
Unpack

DDE

DDEClient
DDEServer

DISPLAY

Analog Meter
Annunciator
Bargraph
Chart
Panel
Plot (oscilloscope)
X/Y-Plot

DSP

Power Spectrum
Digital Filters
FFT

FILE I/O

FileName
Read ASCII File
Read Binary File
Write ASCII File
Write Binary File

GPIB COMMUNICATIONS

IEEE-488

INPUT/OUTPUT,

Analog Input
Analog Output
Burst Generator
Digital Input
Digital Input Port
Digital Input ZPB6064
Digital Output
Digital Output Port
Counter
8254 Counter
Period Measurement
Rate Generator
Thermocouple Input

INPUT/OUTPUT UNDER DMA

Analog Input DMA
Analog Output DMA
Counter DMA
Digital Input DMA
Digital Output DMA

LOGIC

AND
NAND
NOR
NOT
One Shot
OR
SR Flip-Flop
XOR

MATH

Absolute Value
Add
Clip
Derivative
Divide
Integral
Inverse (1/x)
Log10
Ln
Moving Average
Multiply

mX + b

Square
Square Root
Subtract
10^x
Xy

MEASUREMENT

Maximum
Mean/Sum
Minimum
Peak
RMS

MISCELLANEOUS

Extract
Feedback
Latch
Load
PID
Run Controller
Time
Timer
Wait

SERIAL COMMUNICATIONS

Serial

USER INTERFACE

Alphanumeric Entry
Audio Announcer
Message Beep
Slider
Switchbar
User Prompt

WAVEFORM GENERATION

Constant
Pulse
Random
Sine Wave

ORDERING INFORMATION

DESCRIPTION	PART NUMBER	PRICE
Visual Designer Custom Application Generator for Data Acquisition	PCI-20901S	\$995
Visual Designer Custom Block ToolKit	PCI-20904S	\$795

NOTE: VISUAL DESIGNER SUPPORTS THE PCI-20087W, PCI-20098C, PCI-20377W-1, PCI-20378W, PCI-20428W, PCI-20501C AND ZPB6064


BUY VISUAL
DESIGNER BY DEC. 30TH '94
FOR ONLY \$695
(SAVE \$300)

SIGNALYZER

CAPTURE, ANALYZE AND DISPLAY YOUR DATA UNDER WINDOWS

FEATURES/BENEFITS

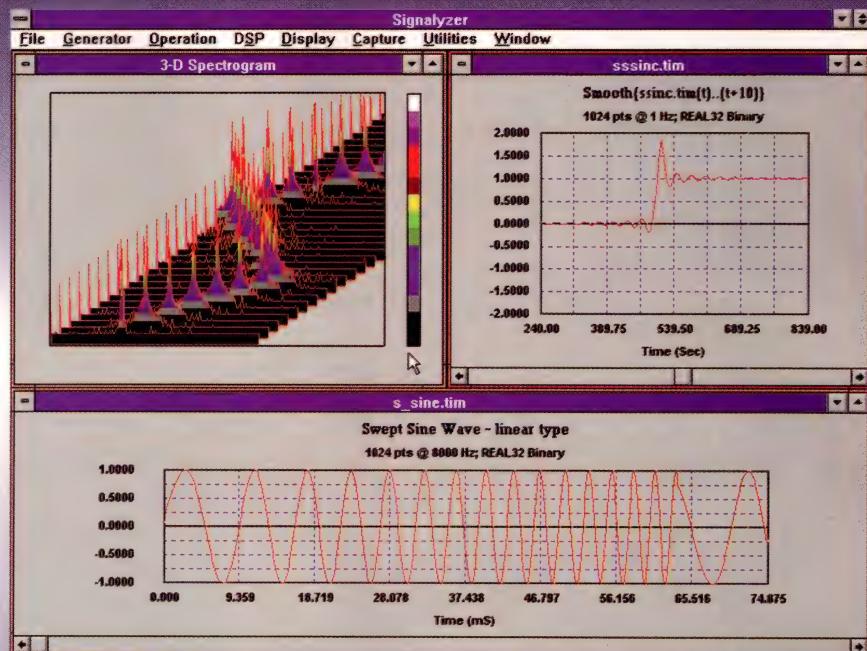- 1 to 32 Channels of Data Acquisition
- Wide Range of Data Analysis and Manipulation Functions
- Oscilloscope and Spectrum Analyzer
- Supports Wide Range of PCI Hardware
- High-Speed Processing
- Sample Rates up to 10MHz
- Data Acquisition at Full Hardware Speeds
- Real-Time Streaming to Disk



CIRCLE NO. 191



Signalizer, a Windows-based software package, provides a powerful tool for analyzing signals. Data acquisition can be as simple as selecting the Capture menu and specifying the setup in a dialog box. You can select channel(s), gain, sample frequency, and the amount of data to be captured. Simple menu selections allow you to manipulate, analyze, display, and/or export captured data.

Signalizer's rich set of signal analysis functions supports both time- and frequency-domain signal analysis. Display capabilities include static displays of captured data as well as real-time oscilloscope and spectrum displays.

When used with the optional Digital Filter Design software, Signalizer filters data files with FIR and IIR digital filters. This option generates the necessary filter coefficient files for low-pass, high-pass, band-pass and band-rejection filters.

FUNCTIONS

DISPLAYS	Cos(x)
Waveform	Atan(x)
Oscilloscope	Exponential
Spectral (1D, 2D, & 3D)	Extract
Cursor Readouts	Smooth
Zoom	Sample & Hold
Pan	Quantize
Autoscale	Statistics
Color Selection	

WAVEFORM GENERATORS
Sinusoidal
Swept Sine
Square
Triangular
Exponential
Windowing Functions
Unit Step
Sinc
Ramp
Unit Sample
Noise

DATA MANIPULATION
Add
Subtract
Multiply
1/X
Square
Square Root
Shift
Flip
Join
Sin(x)


ORDERING INFORMATION

DESCRIPTION	PART NUMBER	PRICE
Signalizer Data Acquisition, Analysis and Display Software	PCI-20395S-1	\$495
Digital Filter Design Software Option	PCI-20396S-1	\$295

NOTE: SIGNALIZER SUPPORTS THE PCI-20098C, PCI-20377W, PCI-20428W-1&-2, PCI-20501C AND ZPB34A BOARDS.

CHARTSTREAM

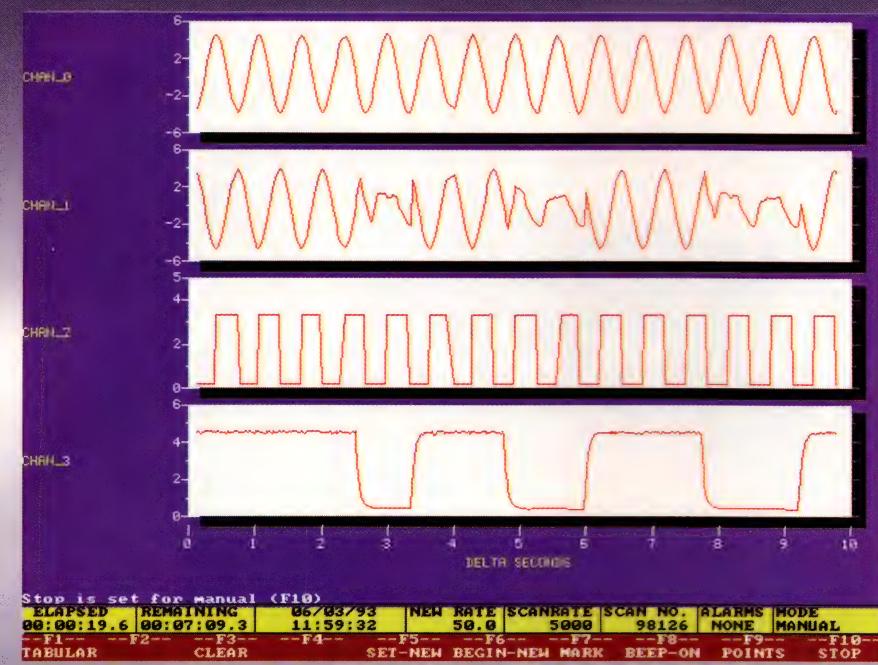STREAM MULTICHANNEL DATA TO DISK WITH ANALYSIS AND DISPLAY



CIRCLE NO. 192

ChartStream allows your PC to acquire, display, and analyze analog data from multiple channels without writing custom software. It is modeled along the lines of the familiar standalone chart recorder. ChartStream's two software components, the data recorder and the post-process data analyzer, operate together seamlessly.

The ChartStream Recorder streams up to 80 channels of analog data to disk at a total rate of up to 100,000 samples/second. As data is streamed continuously to disk, it is also immediately displayed on the screen in strip-chart or x-y plots or in tabular form.

ChartStream Analyzer is a powerful, yet easy-to-use, graphical data analysis package for data manipulation and display. Available graph types include strip-chart, X-Y plot, and multi-plot graphs. ChartStream also supports integrals, derivatives and three levels of smoothing.

ORDERING INFORMATION

DESCRIPTION	PART NUMBER	PRICE
ChartStream Recorder/Analyzer	PCI-20379S-1	\$595

NOTE: CHARTSTREAM SUPPORTS THE PCI-20098C, PCI-20377W-1 AND PCI-20501C BOARDS.

FEATURES/BENEFITS

- Records up to 80 analog channels with real-time display
- Streams to disk at up to 100kHz; to memory at up to 1MHz
- Mathematical operations on waveforms, including integration, differentiation, and inter-channel arithmetic
- Graphical post-process analysis and display
- Graphical user interface; menu-driven operation
- Real-time engineering unit conversion
- Multiple real-time display pages
- Pre- and post-triggered operation



FUNCTIONS

CHARTSTREAM RECORDER

ACQUISITION

Up to 80 Analog Inputs
100kHz Stream to Disk
1MHz Stream to Memory
Variable Scan Rate

TRIGGERING

Analog Channel
Digital Channel
Pre- and Post-Triggered Operation

REAL-TIME CALCULATIONS

Add, Subtract, Multiply, Divide
Sin()
Cos()
Tan()
ASin()
ACos()
Atan()
Abs()
Ln()
Log()
Engineering Units
Calculated Channels

DISPLAY

Strip-Chart Plots
Real-Time Display
10 Display Pages
X-Y Plots
Tabular Display

CHARTSTREAM ANALYZER

Pan
Zoom
Playback
 d/dt
 $\int dt$
Smoothing
Titles
Labels
Text
Print

LOW-COST DATA ACQUISITION BOARDS

PCI-20428W SERIES

FEATURES/BENEFITS

- Premium Functionality at Low Cost
- 100kHz Multichannel Analog I/O Throughput
- 16SE/8Diff Analog Inputs (-3, 16SE)
- 12-Bit Resolution
- DMA Data Transfer to Host Memory (External Triggering)
- Two 12-Bit Analog Outputs (-1 and -2 only)
- Dual DMA for simultaneous analog input/output
- 8 Digital Inputs, 8 Digital Outputs
- 1 Counter/Timer, 2 Rate Generators
- Includes Master Link, C Language, DOS Drivers and Windows DLL
- **Lifetime Warranty**



**BUY ANY
PCI-20428K & VISUAL
DESIGNER BY DEC. 30TH '94
FOR ONLY \$995
(SAVE \$455)**

CIRCLE NO. 193

SOFTWARE SUPPORTED:



VISUAL
DESIGNER



SIGNALYZER



MASTER
LINK
DRIVERS

PARAMETER	CONDITIONS	SPECIFICATION
ANALOG INPUTS Number of Channels, Resolution A/D Voltage Ranges Over Voltage Common Mode Rejection Linearity Error Throughput, Multichannel	Single-ended/Differential Power On/Off 60Hz, 100 Ohm Unbalance, Gain 100 DMA, Triggered DMA	16/8, 12 bit 0-5V, 0-10V, ±5V, ±10V ±35V/±20V -92dB (0.05lsb/V) ±0.024%FS 100kHz
ANALOG OUTPUTS (-1 & -2 only) Channels, Resolution Voltage Ranges Throughput	Using DMA	2, 12 bits (1 part in 4096) 0-10V, ±5V, ±10V 100kHz
DIGITAL I/O Number of Ports, Levels		2 (1 input, 1 output), TTL
COUNTER Number of Channels, Clock Speed		1 (16 bit), 8MHz
POWER REQUIREMENTS	+5V	1A

ORDERING INFORMATION

DESCRIPTION	PART NUMBER	PRICE
Low-cost I/O Board (Gain 1, 10, 100)	PCI-20428W-1	\$395
Low-cost I/O Board (Gain 1, 2, 4, 8)	PCI-20428W-2	\$395
Low-cost I/O Board (Gain 1, without Analog Outputs)	PCI-20428W-3	\$295
Low-Cost I/O Board (Gain 1, 10, 100) with Termination Panel	PCI-20428K-1	\$455
Low-Cost I/O Board (Gain 1, 2, 4, 8) with Termination Panel	PCI-20428K-2	\$455
Low-Cost I/O Board (Gain 1, without Analog Outputs) with Termination Panel	PCI-20428K-3	\$355

EXPANDABLE DATA ACQUISITION BOARDS

PCI-20098C SERIES



CIRCLE NO. 194

BUY ANY
PCI-20098C & VISUAL
DESIGNER BY DEC. 30TH '94
AND SAVE \$400

FEATURES / BENEFITS

- Completely Software Programmable
- Up to 100kHz Multichannel Gap-Free Sampling
- 16SE/8Diff 12-bit Analog Inputs
- Random Channel/Gain Sequencing
- DMA, Interrupt and Polled Modes
- Burst-Mode Sampling, Triggering
- 16 Buffered Digital I/O Channels
- Two 16-Bit Counters
- Accepts up to Two Option Modules
- Includes Master Link Software Drivers for DOS and Windows
- **Lifetime Warranty**

SOFTWARE SUPPORTED:



VISUAL
DESIGNER



SIGNALIZER



CHARTSTREAM



MASTER
LINK
DRIVERS

PARAMETER	CONDITIONS	SPECIFICATION
ANALOG INPUTS		
Number of Channels, Resolution	Single-ended/Differential	16/8, 12 bit (1 part in 4096)
Channel Expansion	Using Option Modules	to 80 SE, to 40 Diff
A/D Voltage Ranges		0-10V, ±5V, ±10V
Software Programmable Gains		1, 10, 100, 200
Over Voltage	Power On/Off	=±35V, ±20V
Common Mode Rejection	60Hz, 100 Ohm Unbalance, Gain 200	90dB (0.05lsb/V)
Linearity Error		±0.012%FS
Throughput, Multichannel w/ DMA	PCI-20098C-1, -2 Gain 1,10	45KHz, 100KHz
DIGITAL I/O		
Number of Ports, Levels	Programmable	2 (expandable to 8), TTL
COUNTERS		
Channels, Clock Speed, Levels	Maximum	2, 16MHz, TTL
BURST GENERATOR		
Range, Resolution, Level		0.002Hz to 2MHz, 125ns, TTL
POWER REQUIREMENTS	+5V	1.7A Max

EXPANSION MODULES			
PCI-20031M-1	32SE, 16 Diff Analog Expander	PCI-20003M-2	2 Ch., 12-bit Analog Output
PCI-20363M-2	8 Chan., Simultaneous Sample/Hold, Expander	PCI-20006M-2	2 Ch., 16-bit Analog Output
PCI-20020M-1	Analog Trigger/Alarm	PCI-20021M-1B	8 Ch., 12-bit Analog Output
		PCI-20004M-1	32 Ch., Digital I/O

ORDERING INFORMATION

DESCRIPTION	PART NUMBER	PRICE	PRICE WITH VISUAL DESIGNER
Expandable 1/0 Board; 45kHz	PCI-20098C-1	\$795	\$1390
Expandable 1/0 Board; 100kHz	PCI-20098C-2	\$895	\$1490
Expandable 1/0 Board; 45kHz with Termination Panel & Cables	PCI-20098K-1	\$1150	\$1745
Expandable 1/0 Board; 100kHz with Termination Panel & Cables	PCI-20098K-2	\$1250	\$1845

LOW-POWER DATA ACQUISITION BOARDS

PCI-20377W SERIES

1 MHZ EXPAN

PCI-205

FEATURES/BENEFITS

- 45kHz and 100kHz Models, 12-Bit Resolution
- 16 SE/8 Diff Analog Inputs with DMA Data Transfer to Host Memory
- Rate Generator with 8MHz Crystal Timebase
- DMA Data Transfer to Host
- 8 Digital Input, 8 Digital Output Channels
- Two 16-Bit Counters
- Includes Master Link Software Drivers for DOS and Windows
- **Lifetime Warranty**



CIRCLE NO. 195

SOFTWARE SUPPORTED:



VISUAL DESIGNER CHARTSTREAM SIGNALIZER MASTER LINK DRIVERS

FEATURES/BENEFITS

- Completely Software Programmable
- 1MHz Gap-Free Throughput To Host Memory
- 8SE, 12-Bit Analog Inputs
- Two DMA Channels
- Random Channel Sequencing
- Burst-Mode Sampling, Triggering
- 16 Digital I/O Channels
- Two 16-Bit Counters
- Accepts up to Two Option Modules
- Includes Master Link Software Drivers for DOS and Windows
- **Lifetime Warranty**

PARAMETER	CONDITIONS	SPECIFICATION
ANALOG INPUT Number of Channels, Resolution A/D Voltage Ranges Software Programmable Gains	Single-ended/Differential	16/8, 12-bit (1part in 4096) 0-10V, ±5V 1, 10, 100, 200
OverVoltage Common Mode Rejection Linearity Error Throughput, Multichannel w/ DMA	Power On/Off 60Hz, 100 Ohm Unbalance, Gain 200 PCI-20377W, -2 Gain 1, 10	±35V, ±20V 90db, (0.05lsb/V) ±0.012%FS 45KHz, 100KHz
DIGITAL I/O Number of Ports, Levels	Programmable	2 (1 input, 1 output), TTL
COUNTERS Channels, Clock Speed, Levels		2, 8MHz, TTL
RATE GENERATOR Range, Resolution, Level		0.002Hz to 2MHz, 125ns, TTL
POWER REQUIREMENTS	+5V	300mA, 1.5W

PARAMETER	CONDITION
ANALOG INPUTS Number of Channels, Resolution Channel Expansion A/D Voltage Ranges OverVoltage Linearity Error Throughput, Multichannel w/ DMA	Single-ended (PCI-20501C-1 Using Option Modules)
DIGITAL I/O Number of Ports, Levels Throughput w/ DMA	Power On/Off
COUNTERS Channels, Clock Speed, Levels	Programmable
BURST GENERATOR Range, Resolution, Level	
POWER REQUIREMENTS	PCI-20501C-1

EXPANSION MODULES (EISA)

PCI-20368M-1	16 Ch. Analog Expander
PCI-20363M-2	8 Ch. Simultaneous Sample/Hold Exp
PCI-20020M-1	Analog Trigger/Alarm

ORDERING INFORMATION

DESCRIPTION	PART NUMBER	PRICE
Low-Power I/O Board; 45kHz	PCI-20377W-1	\$495
Low-Power I/O Board; 100kHz	PCI-20377W-2	\$545
Low-Power I/O Board; 45kHz, with Termination Panel & Cables	PCI-20377K-1	\$815
Low-Power I/O Board; 100kHz, with Termination Panel & Cables	PCI-20377K-2	\$865

ORDERING INFORMATION

DESCRIPTION
1MHz 1/O Board for EISA computers
1MHz 1/O Board for EISA computers with Termination Panel & Cables

BLE BOARD C SERIES



CIRCLE NO. 196

SOFTWARE SUPPORTED:



VISUAL
DESIGNER



CHARTSTREAM SIGNALIZER




SIGNALIZER
MASTER
LINK
DRIVERS



FEATURES / BENEFITS

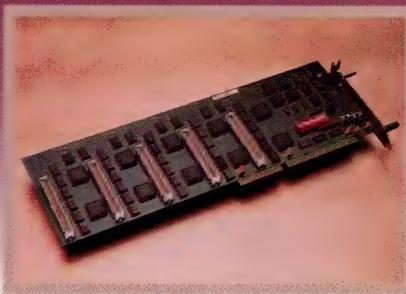- 40, 120 or 240 Digital I/O Channels
- Programmable as Inputs or Outputs in 8-Bit Ports
- Software Programmable; No Jumpers
- High Current-Sink (24mA) and Source (15mA) Capability
- Includes Master Link Software Libraries for DOS and Windows
- Lifetime Warranty



CIRCLE NO. 197

SOFTWARE SUPPORTED:



VISUAL
DESIGNER



MASTER
LINK
DRIVERS

The PCI-20378W Series and PCI-20087W-1 Digital I/O Boards interface with the expansion bus on an ISA (PC/AT or EISA) computer. The PCI-20378W-1 has 30 eight-bit-wide ports and provides 240 channels of buffered TTL I/O. The PCI-20378W-3 has 15 ports and provides 120 channels of buffered TTL I/O. And the

PCI-20087W has 5 eight-bit-wide ports and provides 32 channels of buffered and 8 channels of unbuffered TTL I/O. You can program each port individually for either input or output. The buffers provide a source capability of 15mA and a sink capability of 24mA.

SPECIFICATION	
PCI only)	8, 12 bit (1 part in 4096) to 40 SE 0-10V, ±5V ±35V, ±20V ±0.036% FS 1MHz
	2 (expandable to 6), TTL 1 Mbyte/sec
	2, 16MHz, TTL
	0.002Hz to 2MHz, 125ns, TTL
	3.7A Max
PCI-20003M-2	2 Ch., 12-bit Analog Output
PCI-20006M-2	2 Ch., 16-bit Analog Output
PCI-20021M-1B	8 Ch., 12-bit Analog Output
PCI-20004M-1	32 Ch. Digital I/O

PARAMETER	PART NUMBER	SPECIFICATION
DIGITAL I/O Number of Ports	PCI-20378W-1 PCI-20378W-3 PCI-20087W	30 15 5 (4 full buffered) TTL compatible Source Current Vout = high 15mA Sink Current Vout = low 24mA
Input Levels Output Current	All All	
INTERRUPTS Sources	PCI-20378W-1 PCI-20378W-3 PCI-20087W	Up to 6 Up to 4 Up to 3
PC Levels	All	[2 through 7]
POWER REQUIREMENTS	PCI-20378W-1 PCI-20378W-3 PCI-20087W	+5V, 3.65A maximum +5V, 2.14A maximum +5V, 425mA

ORDERING INFORMATION

PART NUMBER	PRICE
PCI-20501C-1	\$2470
PCI-20501K-1	\$2810

DESCRIPTION	PART NUMBER	PRICE
240 Channel Digital I/O	PCI-20378W-1	\$495
120 Channel Digital I/O	PCI-20378W-3	\$349
40 Channel Digital I/O	PCI-20087W-1	\$179

DSP PROCESSOR BOARDS

ZPB34A SERIES

Our DSP product line offers both fixed and floating point solutions. Our DSP boards are supported by a wide range of analog input and output options.

**FOR
MORE INFORMATION ON
OUR DSP PRODUCT LINE
(800) 685-9911**

CIRCLE NO. 198

FLOATING POINT DSP BOARDS

PART NUMBER	DESCRIPTION	PRICE
ZPB34A	AT&T DSP32C, 50MHz, 64K to 2.25M RAM	from \$995
ANALOG I/O OPTIONS:		
ZPB100	1ch, 16-bit, 8kHz input/output	\$395
ZPD1002	2ch, 12-bit, 10MHz input	\$3495
ZPD1003	1ch, 16-bit, 500kHz input	\$2295
ZPD1007	2ch, 16-bit, 200kHz input/output	\$1495
ZPB1008	8ch, 12-bit, 100kHz input	\$1195

FIXED POINT DSP BOARDS

PART NUMBER	DESCRIPTION	PRICE
PCI-20202C	TI TMS320C25, 50 MHz, 64K RAM	from \$995
EXPANSION MODULES:		
PCI-20019M-1A	8 Channel, 89kHz, 12-bit Analog Input	\$560
PCI-20023M-1	8 Channel, 200kHz, 12-bit Analog Input	\$895
PCI-20341M-1A	4 Channel, 85kHz, 16-bit Analog Input	\$695
PCI-20003M-2	2 Channel, 12-bit Analog Output	\$195
PCI-20006M-2	2 Channel, 16-bit Analog Output	\$545
PCI-20021M-1B	8 Channel, 12-bit Analog Output	\$570

MULTIBUS DATA ACQUISITION PRODUCTS

Our Multibus product line offers a wide range of industrial I/O including: analog input, analog output, digital I/O and counter/timer boards.

**FOR
MORE INFORMATION ON
OUR MULTIBUS LINE
(800) 685-9911**

CIRCLE NO. 199

DIGITAL I/O AND COUNTER BOARDS

PART NUMBER	DESCRIPTION	PRICE
MP802B	32 Channel Relay Output Board (0.5A, 10W per channel)	\$765
MP810NS	24 Channel Isolated Digital Input (0 to 84VDC, 0 to 168VAC)	\$875
MP830-72	72 Channel Digital Input/Output	\$655
MP821B-15	15 Channel Counter/Timer	\$1645

ANALOG INPUT BOARDS

PART NUMBER	CHANNELS	INPUT RANGES	RESOLUTION	PGA	RATE	ANALOG OUTPUT	PRICE
MP8418B	31SE/15Diff	±2.5, 0-5, ±5 0-10, ±10 Volts	12-bits	None	26 kHz	2 ch, 12-bit	\$1,315
MP8418B-PGA	31SE/15Diff	±2.5, 0-5, ±5, 0-10, ±10 Volts	12-bits	1 to 1000	2.8 kHz	2 ch, 12-bit	\$2,085
MP8418B-EXP	96SE/48Diff	±2.5, 0-5, ±5, 0-10, ±10 Volts					\$865

ANALOG OUTPUT BOARDS

PART NUMBER	CHANNELS	OUTPUT RANGES	RESOLUTION	CONVERSION TIME	PRICE
MP8316-V	16	±2.5, 0-5, ±5, 0-10, ±10 Volts	12-bit	3.5 msec	\$1,095
MP8316-I	16	0-24.5 mA	12-bit	8.5 msec	\$1,265

MICROTERMINALS

FOR OPERATOR INTERFACE & DATA COLLECTION

Our broad line of microterminals allows you to select a model with just the features you need—from a basic operator interface to a multifunction unit for bar code data collection. We offer a selection of cases, functions, keyboards, displays and much more.

You'll find our products in use worldwide as operator interface/control panels or as data collection terminals. Ideal applications include:

OPERATOR INTERFACE/ CONTROL PANELS

- Instrumentation
- Communications Products
- Machine Set-Up & Control
- Test and Measurement
- Process Controllers
- Inventory Control

**PRICED
FROM \$195**
FOR CATALOG
(800) 685-9911



CIRCLE NO. 200

DATA COLLECTION TERMINALS

- Shop Floor Control
- Material Tracking
- Time & Attendance
- Inventory Control
- Quality Control
- Machine Monitoring

PARAMETER	SPECIFICATIONS
Communications Display Keypad Physical Functions	RS232, RS422 1 x 16 LCD, LED or 2 x 40 Backlit LCD Numeric, Alphanumeric NEMA 4 (IP66) Extended Temperature Available 6 to 18 Programmable

LANPOINT COMPUTERS

LAN-READY BAR CODE PCS

LANpoint Computers® are a family of compact, rugged DOS PCs designed to add bar code capabilities to a LAN. Both bar code decoding and an Ethernet™ interface are built-in. And a standard PC COM1 port can be used to attach serial or RS232 devices.

- LANpoint® is the smallest unit, measuring just 9.0" W x 5.0" H x 15" D and weighing only 17lb. It includes a full keyboard.
- TIMEpoint®, designed for time & attendance, features a cast-metal case and a built-in bar code or magnetic stripe reader.
- FACTORYpoint®, our NEMA 4 (IP66) industrial model, withstands the harshest environments.

Companies worldwide count on our LANpoint Computers for applications such as:


- Material & Document Tracking
- Shipping & Receiving
- Time & Attendance
- Job Costing
- Labor Data Collection



FOR COMPLETE
LANPOINT INFORMATION
(800) 685-9911



CIRCLE NO. 201

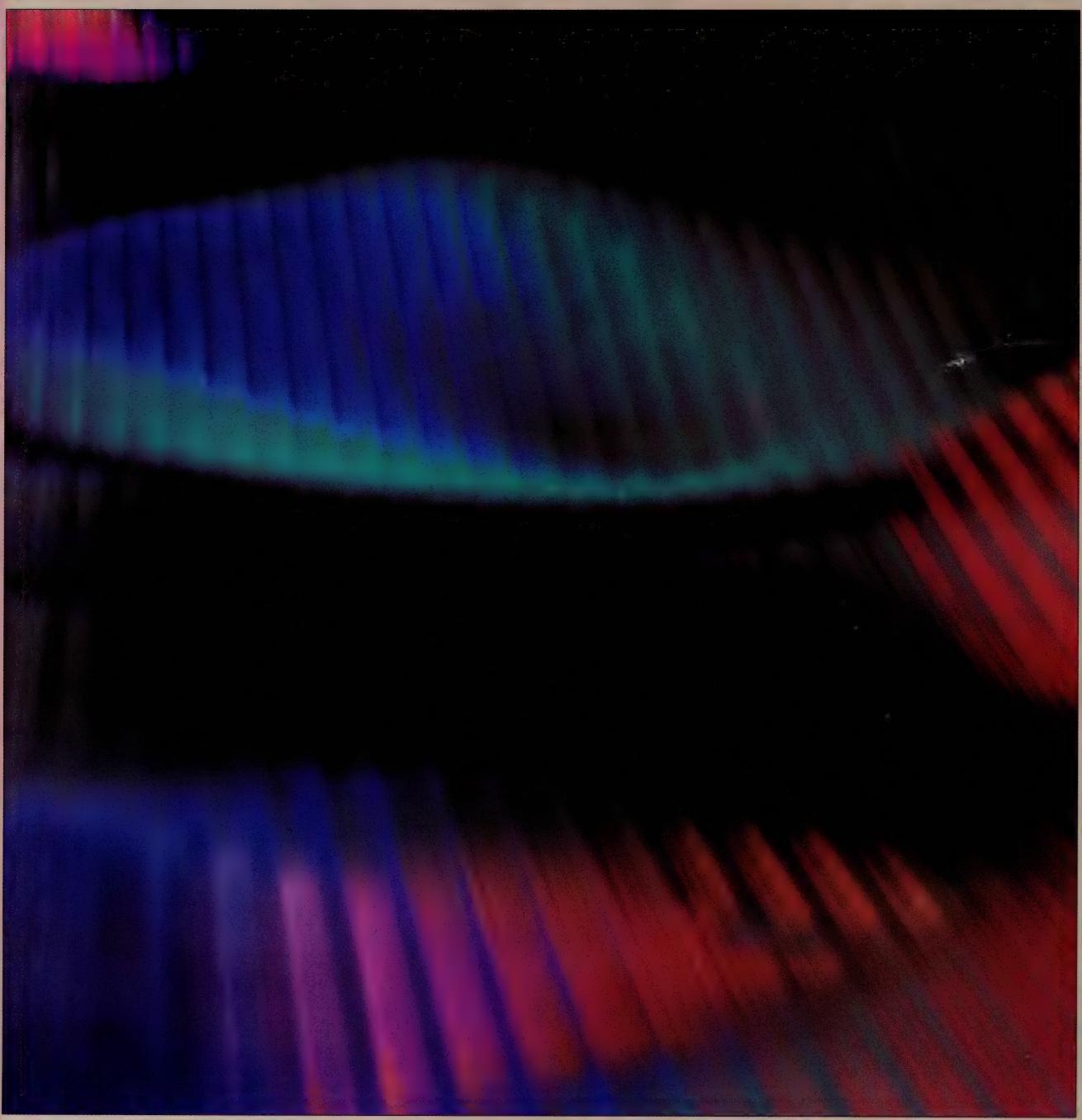

**INTELLIGENT
INSTRUMENTATION™**
A Burr-Brown Company 

6550 S. BAY COLONY DR., MS130 • TUCSON, ARIZONA 85706 • (800) 685-9911 • FAX (602) 573-0522

Visual Designer™, LANPOINT COMPUTERS®, LANPOINT®, TIMEPOINT®, FACTORYPOINT®, Intelligent Instrumentation, Inc.; Windows®, MS-DOS®, Microsoft Corporation; Ethernet™, Xerox Corp; The Yes logo and the NetWare logotype (shark teeth) are trademarks of Novell, Inc.

Lifetime warranty covers products from the date of purchase until five years after the date that INTELLIGENT INSTRUMENTATION discontinues manufacturing the product. The information provided herein is believed to be reliable; however, INTELLIGENT INSTRUMENTATION assumes no responsibility for inaccuracies or omissions. INTELLIGENT INSTRUMENTATION assumes no responsibility for the use of this information, and all use of such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. INTELLIGENT INSTRUMENTATION does not authorize or warrant any INTELLIGENT INSTRUMENTATION products for use in life support or aircraft control applications.

How to Get a Benchful of Signals Without a Bench Full of Generators.



Gone are the days of scouring the lab for function-specific generators.

At a price that's less than many single-purpose generators, Wavetek's new Model 395 does the job of seven different signal sources and does every job extremely well.

In an instant you can choose from a host of signals, from clean sine

waves up to 40 MHz to complex pulse trains and arbitrary waveforms. When you use

Model 395 as a pulse generator, for example, you can individually control the amplitudes, widths, and rise and fall times for up to ten pulses in a train. On-screen help makes

signal selection easier than ever.

You can create many signals that might otherwise require hooking


together two, three or more generators. With gating, looping, linking,

**Take your choice:
function generator,
sweep generator,
pulse generator,
modulator,
trigger generator,
noise generator,
arb, and all of
the above.**

signal summing, and complete arbitrary waveform capability, our universal signal source can produce just about any waveform you can conceive. You can even store any setup for later use — for recall at the

touch of a button!

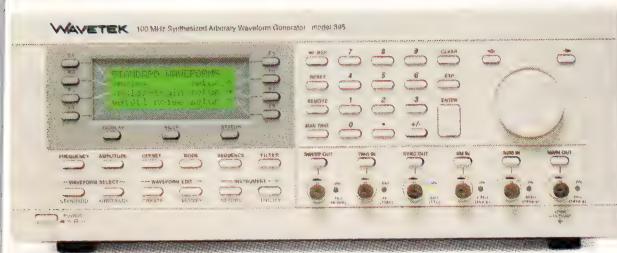So come to the source for all your signal needs. Call Wavetek today at **1-800-223-9885**, and get all the details on the new Model 395 universal signal source.




The Universal Signal Source.

U.S.A.: (619) 279-2200 / U.K.: (603) 404824 / Germany: (089) 96 09 49-0 / Hong Kong: (852) 865-1903

CIRCLE NO. 97




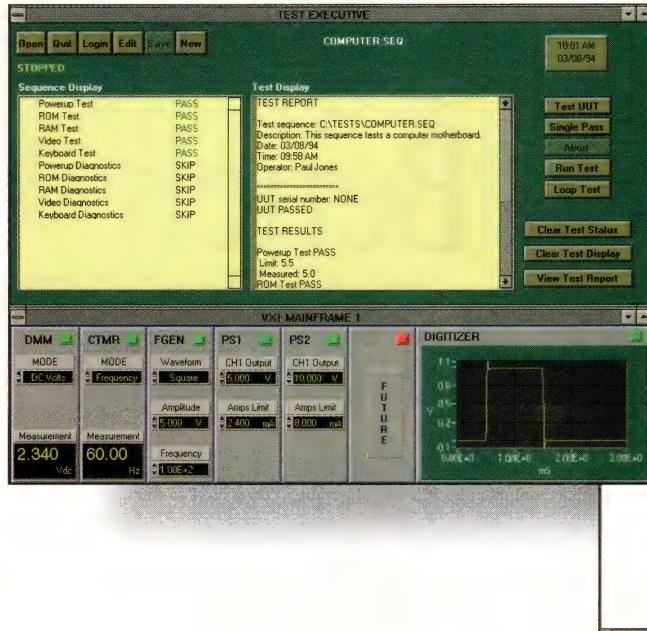What's Revolutionizing the Test Industry?



LabVIEW®

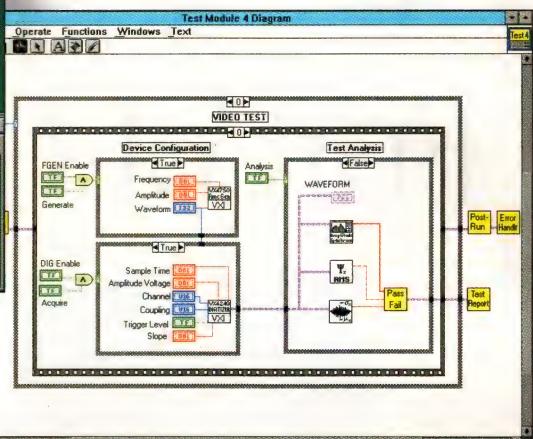Graphical Programming for
Virtual Instrumentation



Virtual Instru

A True Breakthrough in Instrumentation

Virtual Instrumentation is revolutionizing the test industry. How? By empowering you to build your test systems better than ever before. Reusing both hardware and software from one system to the next. Easily enhancing existing systems to meet future needs. Using your existing instruments and even leveraging your existing code. Most importantly, doing all this in less time and for

less money using industry-standard computers and object-oriented software.

A True Breakthrough in Productivity

Virtual instrumentation is much more than a graphical user interface or a layer of icons in the name of "ease of use" – it's a new philosophy. A philosophy that delivers a true breakthrough in efficiency and productivity. Where software is optimized for you and by you.

Where both hardware and software are open, modular, reusable, and interchangeable. Where vendor-defined becomes user-defined through flexible software combined with general-purpose instruments.

A True Breakthrough in Software

At National Instruments we understand the importance of software for virtual instrumentation. That's why we've pioneered this revolution with the test industry's two leading software products.




Branch Offices: Australia 03 879 9422 • Austria 0662 435986 • Belgium 02 757 00 20 • Canada 519 622 9310 • Denmark 45 76 26 00 • Finland 90 527 2322
France 1 48 14 24 24 • Germany 089 741 31 30 • Italy 02 48301892 • Japan 03 3788 1921 • Mexico 95 800 010 0793 • Netherlands 03480 33466
Norway 32 848400 • Singapore 6359015 • Spain 91 640 0085 • Sweden 08 730 49 70 • Switzerland 056 20 51 51 • U.K. 0635 523545



LabWindows®/CVI

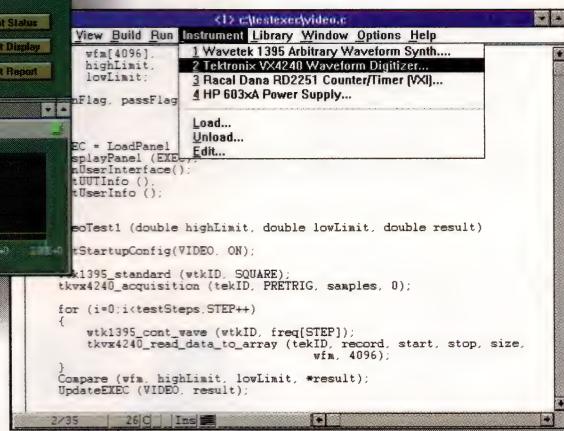C Programming for
Virtual Instrumentation



mentation.

If you like graphical programming, choose LabVIEW, **the** graphical language that others are judged by. If you like conventional programming, choose LabWindows/CVI, **the** only interactive C environment designed for building virtual instruments.

A True Breakthrough in Functionality

Both LabVIEW and LabWindows/CVI feature extensive GPIB and VXI instrument drivers in source code –

for instruments from more than just one vendor – drivers for plug-in DAQ boards, powerful test executives, industry-standard connectivity, and links to your existing code. And with compiled speed and a single, consistent programming paradigm from top to bottom, you don't need to struggle with a hodgepodge of different tools to build your system.

A True Breakthrough in Test

If you think there's a lot at stake here,

you're right. Virtual instrumentation redefines the test industry, shifting the balance of power from vendors to you – so you define the future.

**Join the Virtual Instrument Revolution and discover why...
The Software is the Instrument.**



For your FREE LabVIEW or LabWindows/CVI demonstration package call
(800) 433-3488 (U.S. and Canada)

Corporate Headquarters • 6504 Bridge Point Parkway • Austin, TX 78730-5039 USA • Tel: (512) 794-0100 • Fax: (512) 794-8411
© Copyright 1994 National Instruments Corporation. All rights reserved. Product and company names listed are trademarks or trade names of their respective companies.

For more information on LabVIEW Circle No. 204

For more information on LabWindows/CVI Circle No. 205

EDN September 29, 1994 • 49

NATIONAL INSTRUMENTS®
The Software is the Instrument™



NOT THE SAME OLD WAVE

The Fastest
12-Bit
Single-Chip
Data Acquisition System
(140 ksps)


The LM12434 / 8 ~ A 12-bit monolithic serial I/O system-on-a-chip with fast, zero-glue-logic serial interface to all the popular microprocessors ~ Analog front end includes 4- or 8-channel mux and 12-bit+sign ADC with sample-and-hold ~ Digital features include user-program-

mable conversion sequencer with 8-word RAM for instruction storage, 16-bit delay timer, and 32-word conversion FIFO ~ Specified for high speed (140ksps with 45mW [max.] power consumption @ 5V) or low power (105ksps, consuming 20mW [max.] @ 3.3V) ~ For ordering information and a product information kit with free evaluation software, call **1-800-NAT-SEMI, Extension 319.**




National Semiconductor

Control Rough Waves with Soft Switching

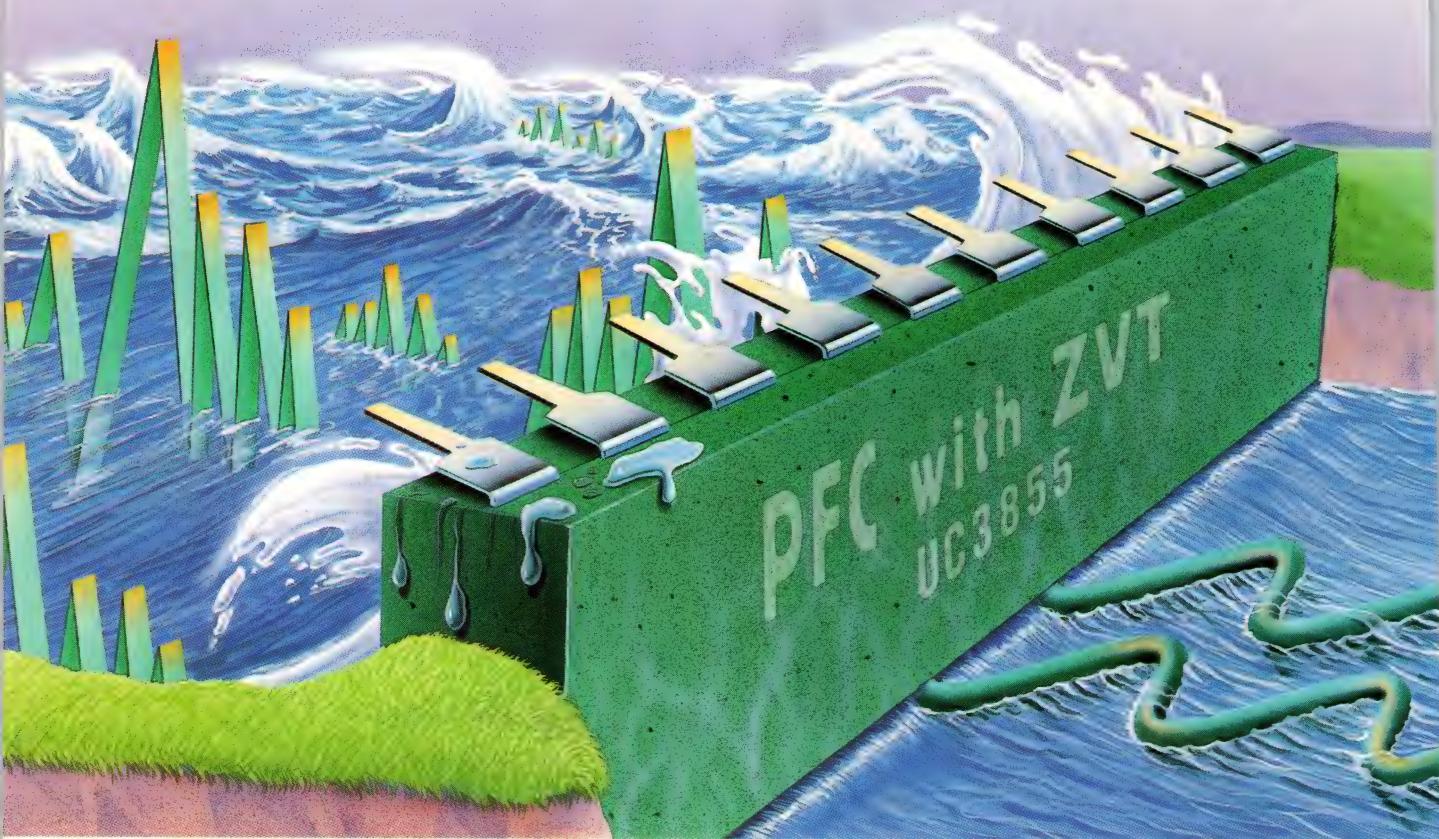

Reach new heights in power factor correction performance. The UC3855's unique "soft switching" technique dramatically reduces diode recovery and MOSFET turn-on losses. The result is super-high efficiency which enables higher frequency switching and more compact preregulator designs.

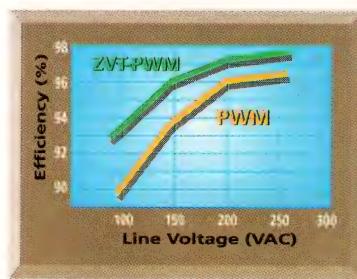Call, FAX or write us today for free samples and application information.



The UC3855 Advantages

- ◆ Provides all control functions for Zero Voltage Transition (ZVT) boost PFC
- ◆ Soft switching reduces EMI and increases efficiency
- ◆ Inductor current synthesizer allows single current sense transformer
- ◆ Fixed frequency average current mode control minimizes line current distortion
- ◆ Overvoltage and overcurrent protection
- ◆ UVLO threshold options
- ◆ SOIC and PLCC packages available

 INTEGRATED CIRCUITS
UNITRODE

TEL: (603) 429-8610

FAX: (603) 424-3460

7 Continental Boulevard, Merrimack, NH 03054

CIRCLE NO. 46

Evolving ADCs DEMAND MORE from drive amplifiers

ANNE WATSON SWAGER, TECHNICAL EDITOR

FINDING AN AMPLIFIER THAT DOESN'T TARNISH AN ADC'S PERFORMANCE IS HARD ENOUGH. BUT NOW YOU ALSO HAVE TO DEAL WITH SINGLE-SUPPLY VOLTAGES AND THE QUIRKY SWITCHED-CAPACITOR INPUT STRUCTURE.

OP-AMP DESIGNERS ARE scrambling to keep pace with changes in ADCs, changes that often make driving these converters more difficult. Ever-increasing speed and resolution, more ADCs with single-supply voltages, and more ADCs with switched-capacitor input structures are forcing system designers to carefully evaluate the drive amplifier's performance.

Depending on the input signal and source, many sampling A/D converters—particularly the switched-capacitor types—require an input-drive amplifier to amplify extremely low-level signals, to provide a low-impedance source for the ADC inputs, or to provide the necessary drive current for the ADC.

You might ask why manufacturers of monolithic, hybrid, and modular products don't routinely include op amps or buffers in front of their ADCs. In the case of an IC, ADC manufacturers use processes that may not be compatible with drive-amplifier requirements. For example, using a CMOS process makes it difficult to meet the low-drift and -noise requirements of high-performance analog functions. In the case of hybrid and modular ADCs that combine high resolution and speed, manufacturers don't include amplifiers

because applications often require different amplifiers, such as one optimized for low noise or another optimized for low distortion.

ADC manufacturers, particularly those that also produce op amps, often


make specific drive-amplifier suggestions. However, the drive amp you ultimately choose needs to closely match your system requirements. Choosing the optimum drive amplifier requires looking at the problem from two perspectives. The first is sheer overall performance. The second is the specific ADC input structure and how it can affect the performance of the op amp.

To provide the best overall performance, the op amp ideally should contribute no additional error to that of the ADC. One way to ensure this is to use an amplifier whose noise, as measured in S/N ratio, is much better than the ADC's theoretical, best-case dynamic range. The familiar equation for this range is:

$$6.02 \times N + 1.76 \text{ dB}$$

where N equals the number of bits. For a 12-bit system, then, an amplifier should have an S/N ratio of 74 dB.

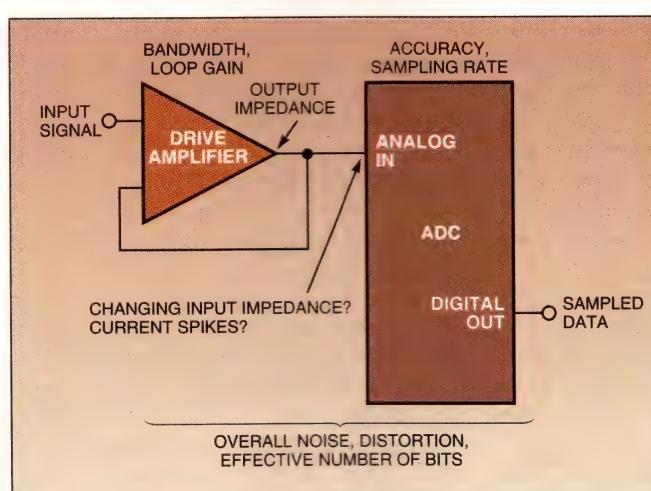Willie Rempfer, design manager of ADCs at Linear Technology, recommends that you also keep in mind the results of adding the noise power of two sources—in this case, the op amp and the ADC. A simple calculation tells you what the combined S/N ratio is. First, transform the



Choosing the best amplifier for driving an ADC requires that you evaluate the amplifier from two perspectives. First, you must ensure overall op-amp and ADC performance. Second, you must examine your ADC's input structure and take steps to minimize its effect on the amplifier.

DRIVE AMPLIFIERS FOR ADCs

S/N ratios in dB to voltages, that is, divide by 20, then calculate 10^x . Next, calculate the square root of the sum of the squares and then convert the result back to dB by multiplying the log by 20.

The results from a series of these calculations demonstrates how an op amp can affect the overall performance. For two components with equal S/N ratios, say 93 dB, the joint S/N ratio is 3 dB less at 90 dB. If you choose an op amp with an S/N ratio 3 dB higher than that of the ADC, you knock the overall S/N ratio down by only 1.8 to 91.2 dB. With a 6-dB difference, an ADC of 93 dB and an op amp of 99 dB produce an overall result 1 dB down, or at 92 dB. A difference of 10 dB produces an almost-negligible difference—0.4 dB.

The point of these theoretical calculations is that the op amp has to be much have a higher S/N ratio than the ADC to have no detrimental effect on the ADC's performance.

Another way to evaluate op amps, suggest Texas Instruments engineers Al Miller and Paul Nossaman, is to compare an op amp's performance to the weight of an ADC's LSB in volts. For example, the LSB weight of a 10-bit converter with a 4V input range is 3.9 mV ($4V/1024$). Compare this number to amplifier specifications, such as input-offset voltage, drift, and noise, all multiplied by the closed-loop gain, to get an idea of the errors the amplifier introduces. For example, an amplifier with a gain of 10 multiplied by an offset of 0.5 mV produces 5 mV, or 1.28 LSBs, of error.

Bandwidth, settling time

To determine the speed requirements of a drive amplifier, you need to match the amplifier's settling time to the ADC's acquisition time. Also, bandwidth requirements can be much more than you expect. Burr-Brown Applications Manager Bonnie Baker says that

many customers drastically underestimate the bandwidth necessary to sustain gain accuracy. Without substantial amounts of gain over the input signal bandwidth, you can easily introduce

After defining your requirements, you hope to find an amplifier that meets those specifications. Unfortunately, this may not be easy. Engineers at Analogic and Datel know all too well

that the choice of ADCs to drive the companies' high-resolution and high-speed ADCs (Ref 1) is limited. Although numerous suitable op amps are available for 12-bit ADCs, only a handful of parts is suitable for driving the 14- and 16-bit, above-500-kHz, hybrid and modular ADCs that these companies produce. According to Don Travers, Analogic's product marketing manager, engineers at Analogic can spend as much time working on the front end as on the ADC itself.

When recommending op amps to their customers, both of these companies choose from a select group.

Depending on the applications, the choice requires a tradeoff between distortion, noise, and settling time. Settling time is particularly difficult because few manufacturers test to a settling time of 0.001% that's approximately equivalent to 16-bit performance.

For example, Analogic recommends Analog Devices' AD843 (\$3.70) (all prices quoted are for 1000-piece quantities) for applications requiring the fastest settling, but this choice doesn't result in the lowest noise performance. For lowest distortion, they recommend the AD845 (\$2.76). Datel engineers also recommend the AD845, which, according to the company's tests, settles to 14-bit accuracy in 400 to 500 nsec. The AD811 (\$2.85) has even faster settling to 14 bits, or 200 nsec. Even faster is Comlinear's CLC402 (\$5.25), which for 2V signals settles to 14-bit accuracy in 50 nsec. Burr-Brown's OPA627 (\$7.35), which is somewhat slower but accurate to 14 bits, also makes Datel's recommended list.

Some of these recommendations may be about to change. Analog Devices has just introduced a new generation of extremely low-distortion



Figure 1

This plot for a theoretical, single-pole system provides an idea of the relationship between the input signal's frequency and a dominant, single-pole frequency to produce a given level of accuracy. For 12-bit single-pole systems, the single-pole frequency F_p must be 100 times the signal frequency F to introduce no gain errors. (Courtesy Burr-Brown Corp)

errors that exceed 1 LSB.


Fig 1, which applies only for single-pole systems and for accuracy of 0.25 LSB, provides a general idea of how high a single-pole frequency must be to produce a particular level of accuracy. For example, consider a unity-gain amplifier with a single closed-loop pole at 10 MHz ($F_p=10$ MHz). According to the plot, the highest signal frequency (F) you can amplify to 12-bit accuracy is 100 kHz because F_p/F is approximately equal to ~ 100 at 12 bits. Worse yet, for 16-bit accuracy, the plot indicates that you would need almost 400 times greater amplifier closed-loop bandwidth than signal bandwidth. (Remember, amplifiers can have more than one pole, the pole of the amplifier may not be the dominant pole, and the plot applies to 0.25 LSB accuracy. The graphs for 0.5 and 1 LSB accuracy would be flatter.)

Certain applications require amplifiers with higher performance levels than those that the ADC typically dictates. Undersampling, for example, requires that an amplifier's bandwidth be compatible with the high-frequency input signal, not the slower sampling rate of the ADC.

There may be only one power source more reliable than our switchers.



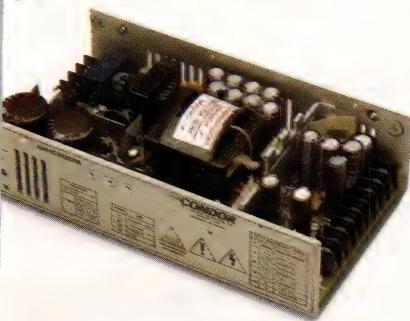Condor's Global Performance® power supplies offer continuous range input, full agency approvals and more.



Our Global Performance switchers give you reliability, performance and full agency approvals, including UL1950 without D3 deviation, CSA22.2 No. 234 Level 3, IEC950, EN60950, VDE0805 Class B EMI and VDE0871 Level B EMI. Medical versions are approved to UL544, IEC601-1, CSA234 Level 3 and VDE0750.

Features include:

- 71 models (single- and multi-output)
- Industry-standard packages
- Custom designs available
- 8 power levels (40 to 225W)
- Continuous-input voltage (85-264VAC)
- OVP on all 5V outputs and single-output units

- MTBF 100,000+ hours per Mil Hndbk 217E
- 8-hour burn-in with cycling (24 hours on medical versions)
- Computerized testing (data sheets furnished)
- 2-year warranty
- 30-day FREE evaluation (call for samples)

If you want top performance and reliability with quick turnaround and competitive pricing, try Condor's Global Performance switchers. The only approval they're missing is yours!

WORLD CLASS RELIABILITY
CONDOR

Condor D.C. Power Supplies, Inc. • 2311 Statham Parkway, Oxnard, CA 93033 • (805) 486-4565 • 1-800-235-5929 (outside CA)
FAX (805) 487-8911 • Send for our catalog, or see us in EEM.

CIRCLE NO. 64

EDN September 29, 1994 • 55

DRIVE AMPLIFIERS FOR ADCS

amplifiers, the AD9631 and AD9632 (both \$4.12). At 1 and 5 MHz, respectively, these amplifiers exhibit typical distortion of -113 and -95 dBc. Spectral noise density is 7 nV $\sqrt{\text{Hz}}$. Settling time to 0.01% is typically 16 nsec.

Lower input ranges

The group of high-accuracy and high-speed amplifiers starts to dwindle as power-supply voltages decrease. The current crop of 14- and 16-bit ADCs with sampling rates of 1 MHz and above typically have wide input ranges of ± 5 or ± 10 V and work from high supply voltages of ± 15 V and sometimes an additional +5 or -5V supply. However, these companies are considering designing lower voltage parts that might present a problem in accuracy rather than speed. For example, Analog designer Tony Dicuccio knows of no amplifier that settles to 16-bit level without a thermal tail in the ± 5 V amplifier supply range.

Supply voltage has a decided impact on amplifier performance. Numerous amplifiers can meet 12-bit accuracy and distortion specs at 1 MHz, but few can do this while operating from a single 5V supply. Although many companies have already announced numerous single-supply amplifiers—at the latest count, Analog Devices has 11 families and 25 products—most are still designing op amps that can drive the higher performance, single-supply ADCs.

Designing an amplifier with wide input and output ranges and other characteristics, such as low distortion, wide bandwidth, fast settling, and capacitive drive, is no easy task. According to Walt Kester, staff applications engineer with Analog Devices, an op amp doesn't have to be rail-to-rail on both the inputs and outputs. In general, it's more important for an op amp to have an input that can go to ground than one whose input can go to the positive rail. Another important asset of

an amplifier is that its output swing within $V_{CE(SAT)}$ of either supply rail, which implies common-emitter or totem-pole outputs instead of the traditional emitter-follower outputs.

output amps drive capacitive loads. Maxim recommends the 500-kH MAX492 family for driving ADCs, such as the company's 12-bit, 75k sample/sec MAX187.

Still, single-supply op amps have a long way to go before they can adequately drive 16-bit ADCs or those faster than 1 MHz. For example, the current crop of single-supply amplifiers cannot meet the noise or open-loop gain requirements for driving 16-bit delta-sigma ADCs.

On the high-speed side, National Semiconductor is working to design a better amplifier to drive its 12-bit, 1-MHz ADC12062 ADC. Finding an amplifier that swings 5V rail-to-rail at this speed is difficult. Until the last few months, the company recommended its LM6361 (\$1.75) amplifier, which requires bipolar supplies. However, the company recently announced the rail-to-rail LM6142 (\$2.10). Compared with driving the 12062 with a perfect source, driving the ADC with the 6142 reduces S/N ratio plus

distortion by just 1 dB, from 70 to 69 dB. Still, the company isn't satisfied and is working on a higher speed amplifier, the LM7131 (from \$1.55 to \$1.85), for release next month.

The basic problem with rail-to-rail amplifiers, says National Application Engineer Bill McDonald, is that there isn't much gain in the amplifier's feedback when the op amp is operating near the rails. This lack of gain causes settling problems, particularly if the ADC

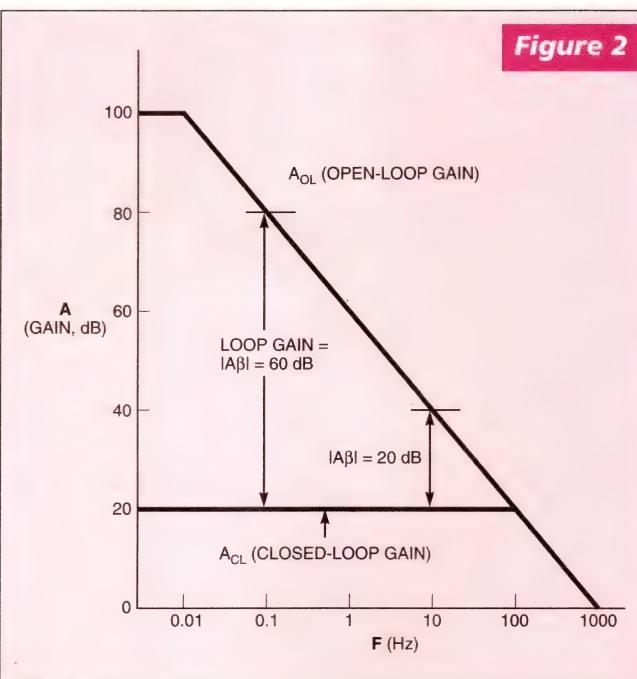


Figure 2

The classic open- and closed-loop curves show that loop-gain—which is inversely proportional to output impedance—decreases as you approach the unity-gain crossover frequency. The higher the output impedance, the more difficulty an amplifier has handling current spikes from the ADC.

To achieve higher ac performance for their single-supply amplifiers, companies are designing new input and output stages. For the new OP279 (\$1.31), designers at Analog Devices altered the usual input biasing to reduce distortion. The amplifier can typically supply ± 80 mA and has a THD specification of 0.01%. A patent-pending output stage in Maxim Integrated Products' MAX492 (\$2.25) and MAX493 (from \$1.45) family helps these rail-to-rail

LOOKING AHEAD

Current and future challenges for op-amp designers include achieving lower noise and distortion for high-resolution and high-speed ADCs. However, you won't see a flurry of activity in this area because of these ADCs' lower volumes compared with other ADC types.

For single-supply systems, op-amp designers will have to continue to design innovative circuit structures to improve drive capability, settling time, and distortion at high bandwidths. You will see more single-supply amplifiers with improved ac specifications.

D/As for Every Application


16-Bit D/A Ideal for Industrial Applications

DAC712 is a 16-bit D/A designed and specified for industrial applications—it's ideal for ATE equipment, analog I/O boards, robotics, process controllers, and similar designs. A full-function device, it's complete with a precision $\pm 10V$ temperature-compensated voltage reference, $\pm 10V$ output amplifier, and 16-bit port bus interface. Featuring a fast, 16-bit parallel, double-buffered interface for direct connection to industrial buses, DAC712 beats the competition in price, power, and size. It is packaged in a 28-pin, "skinny" 0.3in DIP—half the size of our competition! Power dissipation is a low 600mW, and prices have been cut, too! It's also available in a 28-lead SOIC package and priced from \$13.00 in 100s.

Circle No. 26



Multiplying

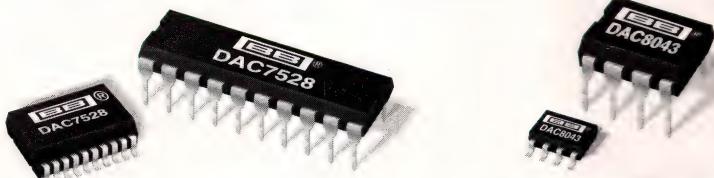

Dual, CMOS, 8-Bit D/A Delivers Competitive Performance and Price

DAC7528 is a dual, 8-bit, CMOS multiplying D/A converter—it's a pin for pin replacement for the industry standard "DAC7528". Use it for digitally controlled filters, disk drives, motor control systems, X-Y graphics, programmable gain/attenuation, and auto calibration applications. Key specs are: double buffered data latches, single 5V supply operation, $\pm 1/2$ LSB linearity, four-quadrant multiplication and TTL compatibility. DAC7528 is available in a 20-pin DIP, SOIC, and die. Priced from \$4.14 in 100s, delivery is immediate and off-the-shelf.

Circle No. 28

12-Bit Serial Input D/A in 8-Pin Mini-DIP & SOIC

DAC8043 is a 12-bit, CMOS multiplying D/A converter that's a pin for pin replacement for the industry standard "DAC8043". Its small size, low cost, and high performance make it perfect for auto calibration, motion control, programmable amplifiers/attenuators, and digitally controlled filters. Key specs are: 12-bit accuracy, 3-wire serial interface, $\pm 1/2$ LSB INL/DNL, ± 1 LSB gain accuracy, 5ppm/ $^{\circ}$ C gain tempco, and TTL/CMOS compatibility. Operating from a +5V supply, DAC8043 is available in an 8-pin Mini-DIP, SOIC, and die. Priced from \$7.47 in 100s, delivery is immediate and off-the-shelf.

Circle No. 29

New Data Conversion Products IC Data Book

The *Data Conversion Products IC Data Book* contains detailed product descriptions, complete specifications, applications tips, and ordering information for our broad line of high performance, data conversion products. Over 950 pages, it offers more than 25 new data conversion solutions. New products profiled include: A/D and D/A converters, data acquisition components, sample/hold amplifiers, V/F converters, and multiplexers. The *Data Conversion Products Data Book* is **FREE** from any Burr-Brown sales office or representative. Or, call the Literature Hot Line at (800) 548-6132 to get your copy.

Circle No. 27



Low Cost, High Accuracy 16-Bit D/A

DAC56 is a complete 16-bit, monolithic D/A—at \$5.83 in 1000s, it's the most cost-effective, highest accuracy D/A available for the industrial market today! It's self-contained with a stable, low noise, internal zener voltage reference; high speed current switches; a resistor ladder network; and a low noise output op amp—all on a single chip. Key specs are: 0.012% linearity error (max), 12-bit guaranteed monotonicity, 1.5 μ s voltage out settling time, 350ns current out settling time, $\pm 3V$ voltage out, and $\pm 1mA$ current output. Use it for process control, ATE equipment, and multiple channel applications. Specified over the 0°/70°C temperature range, DAC56 is available in 16-pin DIP and SOIC packages.

Circle No. 30



Burr-Brown Corporation • P.O. Box 11400 • Tucson, AZ • 85734-1400 • Call (800) 548-6132 or FAX (602) 741-3895.



DRIVE AMPLIFIERS FOR ADCS

input kicks back any unusual current or charge spikes. Thus, at peaks of a sine wave, settling becomes more difficult and can potentially lead to increased second-harmonic distortion. The LM7131's design provides adequate gain bandwidth even for signals close to the supply rail. The unity-gain crossover frequency is around 70 MHz.

Performance is not the only reason that lower supply voltages complicate your choice of a drive amplifier. The input-voltage range of new high-speed, single-supply ADCs is not ground-referenced but is centered around some common-mode voltage between ground and the positive supply. For instance, the input-voltage range can be 2V p-p centered around 3V. Thus, if you start with a ground-referenced input signal, you need to either

ac-couple or level-shift the input with a single-supply op amp that also has the necessary distortion specifications and drive capability.

Level-shifting is important not only because of changing supply voltages but also because of changing ADC input ranges. Gone are the days of wide input ranges for most ADCs. Many input ranges are now 1 to 2V, which you may need to shift before the ADC input. You can level-shift using an op amp and resistors or using difference amplifiers, such as Analog Devices' AD830 (\$2.42) and Linear Technology's LT1187 (\$2.85).

You don't necessarily have to drive a 5V ADC with a 5V op amp. As long as you pay attention to the ADC's input and common-mode range, you can use a ±5 or ±15V amplifier. You may need to take steps to protect the ADC. For example, each member of the Burr-Brown's ADS family includes a front-

end resistor that provides inherent input-overvoltage protection. However, all ADCs do not offer such protection. For such cases, clamped amplifiers can prevent the amplifier from driving the ADC with an out-of-range signal. Most clamped amplifiers and those with output limits need to recover from saturation quickly to keep the ADC from going into saturation.

Comlinear, Harris, and Analog Devices produce amplifiers with output limits. Harris' 350-MHz HFA1135 (around \$3) runs on ±5V supplies and has a maximum saturation recovery time of 1.5 nsec. Analog Devices has also just released two clamped amplifiers, the AD8036 and AD8037 (both \$4.12), which feature high-speed and second-harmonic distortion around 72 dB at 20 MHz. Thus, these devices are suitable for 10-bit systems and implement the clamping at the amplifier's input, which the company says pro-

FOR FREE INFORMATION...

For free information on op amps and ADCs, circle the appropriate numbers on the postage-paid Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you read about their products in EDN.

Analog Devices Inc
Wilmington, MA
(617) 937-1428
Op amps and ADCs
Circle No. 357

Analogic Corp
Wakefield, MA
(508) 977-3000
ADCs
Circle No. 358

Burr-Brown Corp
Tucson, AZ
(602) 746-1111
Op amps and ADCs
Circle No. 359

Comlinear Corp
Fort Collins, CO
(303) 226-0500
Op amps and ADCs
Circle No. 360

Crystal Semiconductor
Austin, TX
(512) 445-7222
ADCs
Circle No. 361

Datel Inc
Mansfield, MA
(508) 339-3000
ADCs
Circle No. 362

Elantec Corp
Milpitas, CA
(408) 945-1323
Op amps
Circle No. 363

Harris Semiconductor Corp
Melbourne, FL
(800) 442-7747
Op amps and ADCs
Circle No. 364

Linear Technology Corp
Milpitas, CA
(408) 432-1900
Op amps and ADCs
Circle No. 365

Maxim Integrated Products
Sunnyvale, CA
(408) 737-7600
220Op amps and ADCs
Circle No. 366

Micro Linear Corp San Jose, CA
(408) 433-5200
ADCs
Circle No. 367

Micro Power Systems
Santa Clara, CA
(408) 727-5350
ADCs
Circle No. 368

National Semiconductor
Santa Clara, CA
(408) 721-2885
Op amps and ADCs
Circle No. 369

Philips Semiconductors
Sunnyvale, CA
(800) 447-1500
Op amps and ADCs
Circle No. 370

Signal Processing Technologies
Colorado Springs, CO
(719) 528-2314
ADCs
Circle No. 371

Sipex Corp
Billerica, MA
(2508) 671-1940
ADCs
Circle No. 372


Texas Instruments
Denver, CO
(800) 477-8924, ext 4500, #SLY50
Op amps and ADCs
Circle No. 373

VOTE . . .
Please also use the Information Retrieval Service card to rate this article (circle one):
High Interest 592
Medium Interest 593
Low Interest 594

Super Circle Number

For more information on op amps and ADCs available from all of the vendors listed in this box, you need only circle one number on the postage-paid reader service card.

Circle No. 374

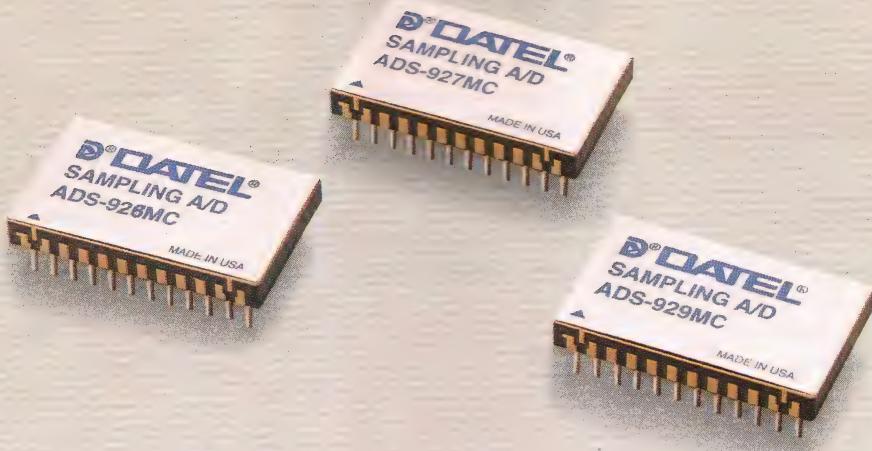

500kHz-10MHz 14-bit Sampling A/D's

Secure your design's future ... Today!

Take control of your next design with a 14-bit A/D from DATTEL. Each device is the proven performance, power, size and price leader in its class. Ideal for imaging, communications and radar/sonar applications, these versatile A/D's operate in commercial, industrial or military environments.

Secure your design's future today by selecting a sampling A/D that's ahead of its time.

- Lowest prices
- Smallest packages
- Lowest power consumptions
- Low noise and distortion
- Ideal for demanding time or frequency-domain applications
- No missing codes over temperature
- MIL-STD-883 screening optional

Model	Resolution (Bits)	Sampling Rate (MHz)	DNL (LSB)	No Missing Codes*	SNR (dB)	THD (-dB)	Power (Watts)	MIL-STD-883 Screening Optional	Price OEM (USA)
ADS-926	14	0.5	±0.5	Yes	80	87	1.6	24-Pin DDIP	Yes \$205
ADS-927	14	1	±0.5	Yes	78	80	1.7	24-Pin DDIP	Yes \$237
ADS-929	14	2	±0.5	Yes	77	78	1.8	24-Pin DDIP	Yes \$271
ADS-944	14	5	±0.5	Yes	76	77	2.95	32-Pin TDIP	Yes \$479
ADS-945	14	10	±0.5	Yes	78	80	4.5	Custom DIP	No \$831

* 0 to +70°C or -55 to +125°C (-25 to +85°C for ADS-945)

DATTEL, Inc., 11 Cabot Boulevard, Mansfield, MA 02048 Tel: (508) 339-3000
FAX: (508) 339-6356. For immediate assistance 800-233-2765.

DATTEL
INNOVATION and EXCELLENCE

DRIVE AMPLIFIERS FOR ADCS

duces better clamp accuracy and linearity than do competing products.

Focus on ADC inputs

In addition to picking the right amplifier from strictly a performance point of view, a second major factor governing the amplifier choice is the ADC's input structure. Flash converters, with their notoriously nonlinear and high input capacitances, were formerly the most difficult ADCs to drive. Now switched-capacitor input structures are usurping that reputation.

In general, all ADCs fit into one of three groups, depending on whether they have benign, flash, or switched-capacitor inputs.

Benign ADCs have reasonably high and mostly constant input impedances and cause no unusual perturbations at the output of the op amp during sampling intervals. Many of Analog Devices' bipolar ADCs, such as the 1671, 871, 872, 9022, and 9023, fit into this category.

Although flash converters used to routinely require high current at high speed to drive their high input capacitances, manufacturers such as Signal Processing Technology have reduced the problem in new flash converters. Five years ago, a 150-MHz part from the company had a 45-pF input capacitance. Now, newer architectures and processes make possible a 150-MHz ADC with 10-pF capacitance.

Converters with switched-capacitor sampling inputs are the newest genre of ADCs. Many types of ADCs, including almost all CMOS types and high-resolution delta-sigma and audio ADCs, now feature these inputs. An ADC with this switching structure doesn't automatically have high input impedance, and the input impedance can change during the sampling cycle. These inputs also cause transient currents that shock and disturb the op amp's output. The op amp then must settle back to its orig-

inal buffered or amplified version of the input signal before the next conversion.

Unfortunately, it's virtually impossible to tell from op-amp settling-time specifications what the settling performance will be under these circumstances. Settling time after a transient

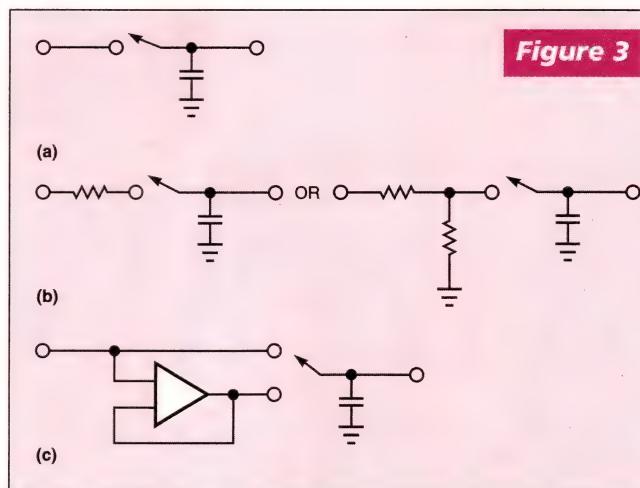


Figure 3

Switched-capacitor input structures are not all the same. To reduce the transient currents produced by the basic unbuffered-capacitive-sampler structure in (a), some manufacturers have added series resistors, as in the resistive-input sampler (b), and others implement a front-end coarse-charge buffer (c). (Courtesy Jerome Johnston of Crystal Semiconductor)

event at the output is not the same as the settling time a company specifies on op-amp data sheets. Normal settling time refers to how long an amplifier's output takes to settle based on a step change at the amplifier's input. In driving switched-capacitor ADCs, the output is at the desired level, but the ADC perturbs this output. No op amp data sheet directly addresses this type of output settling time.

However, it is possible to get some idea of how an amplifier will react to transients by looking at phase-vs-frequency curves. If the phase response rolls off in a smooth linear fashion, the op amp will likely settle fairly effectively after an output glitch. Without a smooth roll-off, especially near the crossover frequency, peaking in the response of the amplifier will occur. Too much peaking implies that the amplifier lacks a well-behaved transient response and will have difficulty driving the ADC's transient load.

You can also take steps to minimize the effects of the output transient. The

most important step is to ensure that the amplifier maintains a low output impedance over all input frequencies of interest. Op amps with high output impedances can't quickly respond to changes in an ADC's input capacitance or handle the transient currents the ADC kicks back. If the op amp doesn't settle in time for the next conversion, nonlinearities can result.

By looking at single data-sheet numbers, you might assume that most op amps have a fairly low and constant output impedance. However, most data-sheet numbers apply only when the amplifier has sufficient loop gain. Also, output-impedance-vs-frequency curves often stop short of revealing what happens at high frequencies. If the dynamic load placed on the amplifier is beyond the amplifier's unity-gain crossover frequency, the output impedance can be quite high.

Remember that high loop gain is necessary for low output impedance, according to the following equation:

$$R_{\text{OUT}} \approx R_o / 1 + A\beta$$


where R_o is the open-loop output impedance and $A\beta$ is the loop gain. As you get closer to the unity-gain crossover frequency of the op amp, $A\beta$ decreases, leading to increased output impedance (Fig 2).

This impedance requirement then translates directly to a bandwidth requirement. A higher bandwidth op amp has higher loop gain and thus lower output impedance at higher frequencies. According to Harris Semiconductor linear-product-marketing engineer Chris Henningsen, this is one reason to use an 800-MHz amplifier in front of a 20-MHz ADC, which is sampling a 5-MHz video-input signal. The high-bandwidth op amp more effectively swamps out the ADC's kickback signals than does a lower bandwidth amplifier.

According to Linear Technology's Rempfer, op amps with emitter-follower outputs running with lots of current

"I'm FlatPAC..."

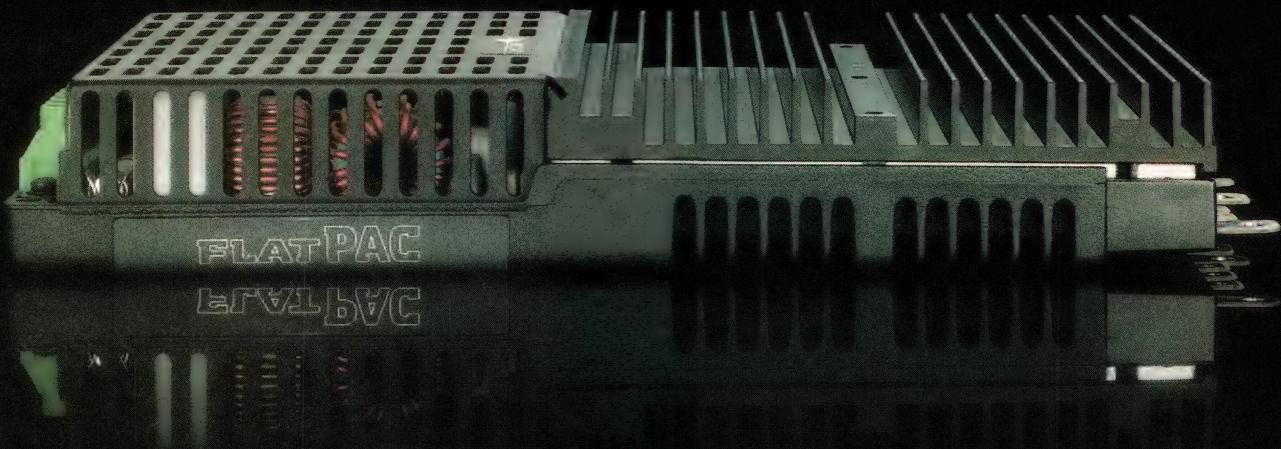...I'll respond
to any line you feed me!"



Vicor's Autoranging FlatPAC • Up to 600 Watts

Low Profile, 1.37"H • Configurable • Agency Approved

- Inputs: 115/230 VAC Autoranging
- Up to 3 Outputs: 1 to 95 VDC
- VDE/FCC Class "A" and/or "B"
- 30 mS Holdup
- UL, CSA, TÜV, VDE 0805,
EN 60950, IEC 950
- Meets IEC 801-5, Level 3
- 80-90% Efficiency
- BUS OK and AC OK
- Output Disable
- ZCS Power Architecture
- Low Noise FM Control

Component Solutions For Your Power System


Vicor Corporation 23 Frontage Road • Andover, MA. 01810 USA • Tel: (508) 470-2900 • Fax: (508) 475-6715

Vicor Europe Carl-von-Linde Strasse 15 D-85748 Garching-Hochbruck, Germany • Tel: +49-89-329-2763 • Fax: +49-89-329-2767

Vicor Asia-Pacific 10F, No. 7, Ho Ping E. Road, Sec. 3, Taipei, Taiwan • Tel: +886-2-708-8020 • Fax: +886-2-755-5578



SURFACE MOUNT DC-DC Converters

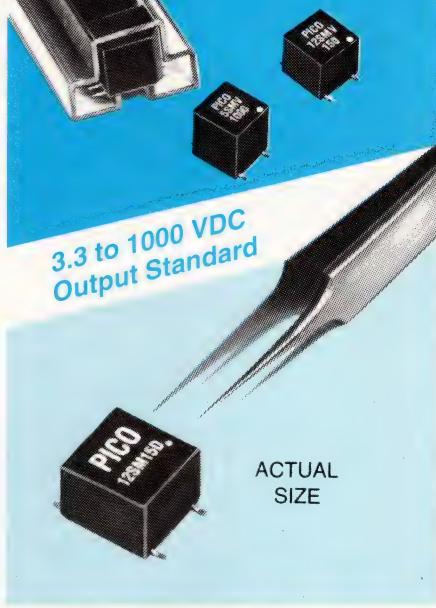

PICO's SM and SMV Series

- 1.25 watt output at 70° ambient
- 140 standard models
- Ultra-miniature size .34 ht., 3.5 grams weight
- 5 input voltage ranges 5, 12, 24, 28 and 48 VDC
- Up to 1500 volts input/output isolation
- No heat sink or electrical derating required
- Up to 1000 volts DC output
- MIL-STD 883 options available
 - Expanded operating temp (-55°C to +85°C)
 - Stabilization Bake (125°C ambient)
 - Temperature Cycle (-55°C to +125°C)
 - Hi Temp, burn in
- Over 1400 standard DC-DC and AC-DC models up to 200 watts

Delivery—
stock to one week

See EEM
or send direct
for Free PICO Catalog.
Call toll free **800-431-1064**
in NY call **914-699-5514**
FAX **914-699-5565**

PICO Electronics, Inc.
453 N. MacQuesten Pkwy., Mt. Vernon, N.Y. 10552
CIRCLE NO. 89

DRIVE AMPLIFIERS FOR ADCs

usually have the necessary low output impedance. One thing to watch out for, however, is amplifiers with inherently higher output impedances, such as those with collectors driving the output—specifically, amplifiers with rail-to-rail outputs.

Inputs have their differences

Manufacturers are also doing their part to minimize the effects of the ADC's transient glitch by modifying the switched-capacitor input. You now find ADCs with the following three types of inputs: (Fig 3):

- input directly connected to sampling switch,
- input series resistor before switch,
- coarse-charge buffer.

Burr-Brown's ADS family of pin-compatible 12- and 16-bit ADCs are an example of the input-series-resistor-before-switch structure. The designers put a series resistor on the input so that charge doesn't go straight into the op amp. The ADC designers also reduced the switching current by 10. The result, according to Burr-Brown, is that any amplifier can drive members of the ADS family.

Crystal Semiconductor uses the coarse-charge buffer approach in its CS5101A ADC and all its dc-accurate delta-sigma parts (CS5504 through CS5509). The input switch connects either to a CMOS unity-gain buffer amplifier or to the input signal. The coarse-charge buffer charges the hold capacitor to a signal near the input. When the switch connects to the input, the driving circuit has only to provide charge to compensate for the buffer's offset voltage. The result is that the ADC produces low transient current.

These improvements don't mean you can ignore the amplifier, however. Crystal Semiconductor Applications Engineer Jerome Johnston still fields calls from customers who complain about missing codes, presumably caused by a poor-performing ADC. Johnston says the problem isn't usually the ADC, but a poorly selected amplifier that has difficulty settling properly, particularly around bipolar zero. The company recommends placing an RC network between the op amp and ADC to buffer the dynamic transient current from the ADC. Choose the RC values so

that the time constant of the network isn't too long, which would produce averaging and offset errors.

Linear Technology and Maxim Integrated Products also often recommend a 100-pF capacitor to ground between the op amp and ADC to absorb the transient glitch. Adding this capacitor means that the amplifier has to be able to drive this 100-pF load.

In fact, Linear Technology has just introduced a rail-to-rail amplifier, the LT1368 (no prices are available as this article goes to press) that requires and, thus, is happy driving, a 0.1-μF compensation capacitor on the output. When driving an ADC—typically a low-power and low-frequency device such as the LTC1288—this capacitor forms a filter that reduces the amplifier's output impedance and swamps the current spikes from the ADC. In ADC tests with input signals under 100 Hz, the LT1368 shows less than 1 dB of distortion.

Some final words of advice: Beware of what may happen if you run an op amp at other than the tested and specified power-supply voltages; don't scrimp on testing your own op-amp/ADC pair.

EDN

References

1. Swager, Anne Watson, "High-speed, high-resolution ADCs advance a spectrum of applications," *EDN*, Oct 28, 1993, pg 76.
2. Kester, Walt, "Designer's guide to sampling A/D converters," Parts 1 and 2. *EDN*, Sept 3, 1992, pg 135 and Oct 1, 1992, pg 97.

Acknowledgments

Many thanks for useful discussions. Paul Errico, Jay Cormier, and Steve Rusnak of Analog Devices; Jerome Johnston of Crystal Semiconductor; and Willie Rempfer and Bill Gross of Linear Technology.

You can reach Technical Editor Anne Watson Swager at (215) 645-0544.

VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest
592

Medium Interest
593

Low Interest
594

VISUAL PROGRAMMING PERVERADES DATA-ACQUISITION SOFTWARE DEVELOPMENT

BRIAN KERRIDGE, SENIOR TECHNICAL EDITOR

The first thing you do when devising almost any project or system is to sketch an overview block diagram. Next, you study each block in turn and layer on more and more textual detail until you have a complete description of the design.

Visual programming—also known as graphical, diagrammatic, or iconic programming—for data-acquisition systems works in exactly that fashion. In visual programming, the blocks are preprogrammed software modules that appear as icons on your display. You select and connect icons representing sensor inputs, ADCs, and display outputs in a logical sequence.

Some of the icons, such as displays, are standard for any application, but others correspond to hardware specific to your measurement system. Clicking on an icon opens a dialog box containing a range of properties for that icon's function.

Visual programming gets your data-acquisition system up and running in hours or days, instead of the months needed to use traditional coding in Basic or C. MS Windows is the most popular environment, but its interrupt latency can threaten data integrity in high-speed and control-system applications.

For an ADC card, you type in properties such as channel number, sample rate, and voltage range. Other icons enable you to insert a wide range of math functions to operate on input signals, such as statistical, algebraic, and frequency-domain operators. Finally, and what gives visual programming its greatest impact, you have icons for building a highly impressive user interface for your system. Sliders, pushbuttons, gauges, meters, and graphs offer you unlimited scope in devising a front panel just to your taste.

The overriding benefit of visual programming for data-acquisition systems is the speed with which you can set up a system to take measurements. Traditionally, you could expect to employ the services of a software engineer for a couple of months to code in Basic or C



National Instruments' LabView visual-programming software, which now runs under MS Windows, is a general-purpose tool with extensive icon libraries for data acquisition, instrument control, data analysis and presentation (Ref 1). Device drivers exist for over 100 programmable IEEE-488, VXI, and RS-232C instruments, in addition to the company's range of PC plug-in data acquisition, DSP, and signal conditioning hardware.

before taking a single measurement. With visual programming, you can reasonably expect to reduce the two months spent coding to two days programming visually. The major gain results from the virtual eclipse of a software programmer to make the system run. Experience shows that scientists, hardware engineers, and system developers can easily exercise visual-programming software in the same way they would string together the hardware itself.

DATA-ACQUISITION SOFTWARE

This feature makes visual programming motivational, fun, and naturally appealing, especially when compared with conventional coding, which is irritating and has little to do with the primary objective of acquiring data.

Additionally, visual programming benefits a wide range of users from the lone technologist to companies developing commercial applications. A technologist's priority is to gather data with minimal sidetracking; commercial developers have an overwhelming desire to reduce time to market.

Visual programming has existed for over a decade. One of the first products, National Instruments' LabView, mainly set out to simplify the programming of rack-and-stack IEEE-488 instrumentation systems. Over that decade, volumes of PCs running MS Windows have outstripped IEEE-488 systems, and, now, the major business for visual programming is operating PC plug-in and standard bus cards.

National Instruments' highly developed LabView remains a leading-market product, although most self-respecting PC-card vendors now offer a competitive product.

Rival products look alike

Table 1 surveys a selection of visual-programming data-acquisition software products. At first glance, it's not easy to distinguish product offerings. (Ref 2 reports on a basic bench test of seven of the products listed.) One basic difference is that some products, such as LabView, are stand-alone programs, and later products, such as Keithley's Visual DAS, are adaptations of MS Visual Basic. Also, price does little to distinguish products, and \$995 is a popular number. Prices shown are for software to develop applications, although some vendors offer lower cost run time-only

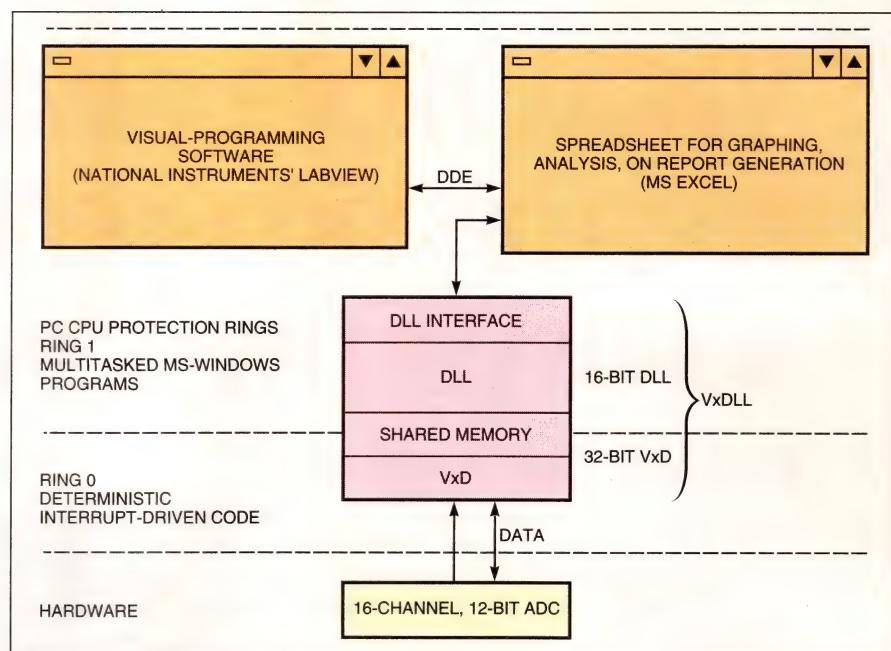


Fig 1—Arcom Control Systems overcame much of MSWindows' interrupt latency by designing virtual DLL SuperDRIVERS (VxDs) for users of their hardware data-acquisition products. VxDs operate at low-level "Ring 0" in an MS Windows environment and enable I/O interfaces to respond to 10,000 interrupts/sec—sufficient for a wide range of data-acquisition and control applications.

versions. Implementations using MS Visual Basic are lower cost, although you need to add around \$199 for Visual Basic.

One product-to-product variation worth investigating is the range of software device drivers that each vendor supplies. Some vendors provide drivers for only their own range of plug-ins, which effectively obliges you to use their data-acquisition hardware. In contrast, an increasing number of third-party hardware suppliers offers MS Visual Basic and Visual C++ drivers that provide more of an open-system environment to developers using these programs.

Another important factor is the

effectiveness of the driver. There's no simple way to compare drivers, and you need to thoroughly evaluate performance before committing to a visual-programming or hardware product.

Although visual programming largely negates the need to be a software programmer, C designers need not fear for job security yet. First, writing software drivers for I/O hardware remains a prime requirement. Drivers involve significant coding, and writing your own can easily consume a man-year of effort. Second, although running data-acquisition systems under MS Windows is very appealing, Windows introduces a heavy cost and physical-size overhead and imprecise timing to the system.

The cost overhead results from the need for a posh PC to run MS Windows and a visual-programming environment. To run Hewlett-Packard's HP-VEE, for example, the company recommends a 33-MHz 80486 PC with a 1024×768-pixel SVGA display, a 16-Mbyte RAM, and 15 Mbytes of hard-disk space. In comparison, a C program would certainly run on an embedded 20-MHz 80386 processor card with less

LOOKING AHEAD

Visual programming will continue to make inroads into the traditionally coded data-acquisition software territory. The installed base of MS Windows environments will ensure its continued popularity. When MS Windows 4.0 (Chicago) arrives, true multitasking abil-

ity promises to expand the scope of data-acquisition systems and should address some existing Windows interrupt-latency concerns. Software speed problems will also diminish as 66-MHz, and beyond, PCs become the norm.

More Recording Systems than the CIA, KGB and FBI.




Getting the right piece of test equipment shouldn't be as tough as extracting state secrets. That's why GE Rental/Lease has expanded its inventory of recorders and other test equipment available for rent, lease or purchase.

Whatever type recorder you need, from thermal array to DAT tape, you'll find it here, along with 120,000 other pieces of equipment. Name brands like Astro-Med, Gould, TEAC, Yokogawa and more. Easy to find in our new catalog, and ready for fast, overnight delivery.

And all backed by a seasoned team of technical specialists, a quality program registered to ISO 9002 and our exclusive Customer Service Guarantee: *If for any reason you're unhappy with your rental, simply dial 1-800-GE-RENTS and ask for a Customer Service Representative. If we cannot make it right, your rental will be free.*

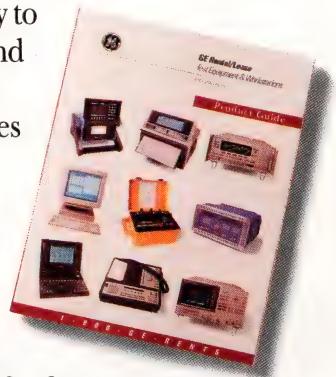Now it's no secret where to go for test equipment. Call 1-800-GE-RENTS.



CIRCLE NO. 76



GE Rental/Lease
Test Equipment & Workstations

A GE Capital Company

DATA-ACQUISITION SOFTWARE

than 1 Mbyte of ROM and EPROM.

Relying on an MS Windows environment to control system timing is far from ideal for some data-acquisition setups. In practice, MS Windows relies on a PC's 55-msec interrupt latency, which is insufficiently deterministic for high-speed data-acquisition or control systems. (Interrupt latency is a measure of the time between an interrupt's asserting that data is available and the point when the CPU reads the data.) MS Windows was never intended to drive speed-conscious hardware and can't hope to compete with dedicated code running under real-time operating systems.

A further justification for retaining some traditionally programmed C-coded data-acquisition software involves safety-critical control-system applications. Without a great deal of beta-site testing, you can't be sure that either MS Windows or the visual-programming environment won't decide

to display an obscure dialog box that halts a process at a critical point. With your own C code, you are still required to beta-test, but, overall, there are fewer unknowns in your own control software.

Programming know-how helps

Although visual programming claims that the user does not need traditional programming skills, some programming experience can benefit your work. Also, some familiarity with MS Windows features such as Dynamic Data Exchange (DDE) and Dynamic Link Library (DLL) is important. Briefly, DDE is a standard MS Windows message-handling system for importing or exporting data between applications. A DLL is a Windows program providing functions that other Windows programs can use when driving I/O hardware, for example.

According to Stephen Salmon, software-design engineer with Arcom Con-

trol Systems, "There's no doubt visual programming enables most technologists to swiftly make a system produce results, although users' initial attempts may produce inefficient and inelegant solutions."

Comparing learning curves using different approaches, Salmon decided that, after two years of coding in C, he was competent enough to design software for data-acquisition systems. Moving on to LabView, he found that he could produce an equivalent system after a matter of days. (Because Visual Basic offers developers more program visibility, using Visual Basic takes a few days longer.)

Salmon advises visual-programming users to think carefully through their early applications and attempt to simplify their designs. He reports that new users typically employ several individual channels from input to display rather than introducing multiplexing. Unnecessarily duplicating sequential-and repetitive-event icons, instead of using for and while loops is another common overcomplication. Littering the display with icons rapidly eats memory that is needed to run a system and can limit operating speed because the program has to interpret the superfluous icons in the run mode.

Salmon also draws attention to the effect of Windows' inherent interrupt latency on operating speed. In many cases, a system's read rate is sufficiently slow that interrupt latency is not significant, as in a temperature-logging system that takes readings every few minutes. But, for high-speed data-acquisition or -control systems, it's important to know precisely when measurements occur, as in real-time logging.

To minimize the effects of interrupt latency, Arcom uses a special form of virtual extended-DLL driver (VxDLL) with its range of hardware, called a "SuperDriver." VxDLLs operate at low-level "Ring 0" in an MS Windows environment, predictably trapping interrupts and enabling I/O interfacing independent of the host program (Fig 1). Any Windows-based program that supports DLL or DDE, such as Visual Basic, Visual C++, or LabView, can call Arcom's SuperDriver code.


Arcom has compared the interrupt-

TABLE 1—REPRESENTATIVE VISUAL-PROGRAMMING DATA-ACQUISITION SOFTWARE

Vendor	Product	Computer type			Requires MS Visual Basic	Price
		Mac	PC	W/S		
		W 3.1	NT			
Analogic Circle No. 341	Snap-Master		X			\$995
Capital Equipment Circle No. 343	Testpoint		X			\$995
Data Translation Circle No. 344	DT VEE		X			\$1995
	VB-EZ		X		X	\$195
G-W Instruments Circle No. 345	Superscope II	X				\$1490
Hewlett-Packard Circle No. 346	VEE		X	X	X	\$1995
Intelligent Instrumentation Circle No. 347	Visual Designer		X			\$995
IO Tech Circle No. 348	VisuaLab		X		X	\$395
Keithley Instruments Circle No. 349	VisualDAS		X		X	\$99
Laboratory Technologies Circle No. 350	Labtech Notebook		X			\$995
Microstar Laboratories Circle No. 351	DASYLab		X			\$9
	DAPwindows		X			\$295
National Instruments Circle No. 352	LabView	X	X	X	X	\$995
Omega Circle No. 353	Centrel	X				\$198
Strawberry Tree Circle No. 355	Workbench PC		X			\$995

Prices shown for base application-development software. Additional advanced-development tool kits and extra device-driver libraries can double base price. Some vendors offer run-only versions under \$500.
W/S—Workstation, MS—Microsoft, W 3.1—MS Windows 3.1, Mac—Macintosh

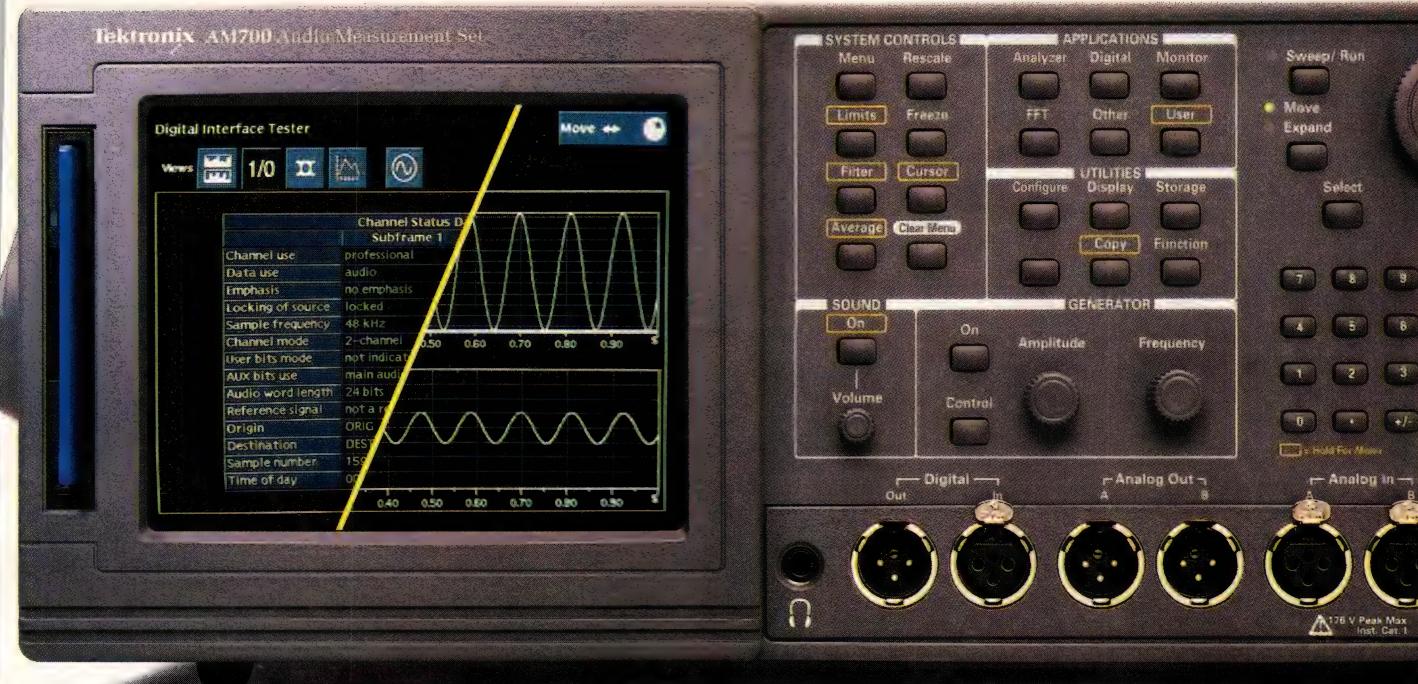The one audio tester you can use in mixed company.



THE TEKTRONIX AM700. THE HIGH PERFORMANCE MIXED SIGNAL AUDIO

TESTER THAT'S VERSATILE AND EASY TO USE. ■ Meet a real crowd pleaser.

■ The AM700. It's designed for virtually any audio test application—analog or digital. Making it the perfect choice for testing car radios, recording equipment, radio and television audio broadcast systems, and more. ■ For starters, it's fast and easy to use. There are no complex commands to learn. Just a simple interface that guides you to any function you need. And a high performance processor that gets the job done pronto. ■ Plus, the AM700 lets

you work any way you want. Automatically, semi-automatically, or manually. It's ideal for design engineers working at the bench

level, test engineers on the production line, and everywhere in between. ■ And it's

completely portable, too. Everything's included in one compact instrument.

■ No wonder it knows exactly what to do in mixed company. ■ Make an appointment for a demonstration by calling your local Tektronix sales office or call 1-800-TEK-WIDE ext.TV




Input and output ports allow you to generate test signals for both analog and digital domains.

Tektronix

CUSTOM Analog Design

Need help designing and manufacturing that specialized analog architecture or plug-in board?

Turn to Analogic...

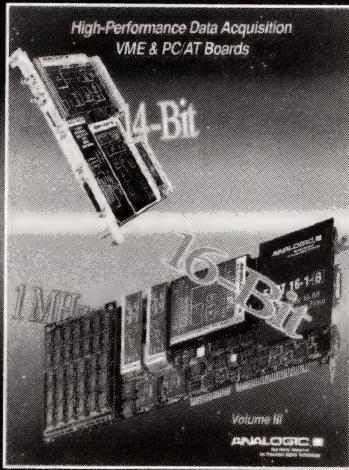

a recognized world leader in precision analog signal technology. We can design to meet your requirements in such modalities as:

PC/AT • VME
PC/104 • PCI • TIM-40
A/D Converter Components
...and more!

Analogic has 25 years of custom design and partnering experience with leading high technology companies.

Call or FAX Today with your custom volume requirements.
Let us be your analog design partner.
1-800-446-8936, Ext. 2388 FAX: 617-245-1274

Analogic Corporation
360 Audubon Road, Wakefield, MA 01880

ANALOGIC
The World Resource
for Precision Signal Technology

CIRCLE NO. 9

EDN

DESIGN FEATURE

FOR FREE INFORMATION...

For free information on the data-acquisition software products discussed in this article, circle the appropriate numbers on the postage-paid Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you read about their products in EDN.

Analogic

Wakefield, MA
(508) 977-3000

Circle No. 341

Arcom Control Systems

Kansas City, MO
(816) 941-7025

Circle No. 342

Capital Equipment

Burlington, MA
(617) 273-1818

Circle No. 343

Data Translation

Marlborough, MA
(508) 481-3700

Circle No. 344

GW-Instruments

Somerville, MA
(617) 625-4096

Circle No. 345

Hewlett-Packard

Loveland, CA
(303) 679-5000

Circle No. 346

Intelligent Instrumentation

Tucson, AZ
(602) 573-3504

Circle No. 347

IOTech

Cleveland, OH
(216) 439-4091

Circle No. 348

Keithley Instruments

Taunton, MA
(508) 880-3000

Circle No. 349

Laboratory Technologies

Wilmington, MA
(508) 657-5400

Circle No. 350

Microstar Laboratories

Bellevue, WA
(206) 453-2345

Circle No. 351

National Instruments

Austin, TX
(512) 794-0100

Circle No. 352

Omega

Stanford, CT
(203) 359-1660

Circle No. 353

Signal Technology

Santa Barbara, CA
(805) 899-8300

Circle No. 354

Strawberry Tree

Sunnyvale, CA
(408) 736-8810

Circle No. 355

VOTE . . .

Please also use the Information Retrieval Service card to rate this article (circle one):

High Interest 595

Medium Interest 596

Low Interest 597

Super Circle Number

For more information on data-acquisition software products available from all of the vendors listed in this box, you need circle only one number on the postage-paid reader service card. **Circle No. 356**

latency performance of its SuperDrivers with other MS-DOS and the Windows VxD drivers using a 40-MHz 80386DX CPU. Results show a range of latencies for each driver: MS-DOS mouse device driver running under Windows—100 to 400 μ sec, Windows terminal emulator—40 to 65 μ sec, and Arcom's SuperDriver—25 to 50 μ sec.

Microstar Laboratories use a different approach to minimizing interrupt-latency effects. The company's PC plug-in data-acquisition boards include an on board processor, memory, and a real-time operating system called DAPL. This on board intelligence handles the time-critical aspects of an application and frees your data-acquisi-

tion hardware from delays and resource demands imposed by Windows. Running under the company's DASYLab visual-programming software, the processor typically achieves a task latency of <500 μ sec. **EDN**


References

1. Johnson, Gary W, *LabVIEW Graphical Programming: Practical Applications in Instrumentation and Control*, McGraw-Hill, New York, NY, 1994, includes disks, \$45.

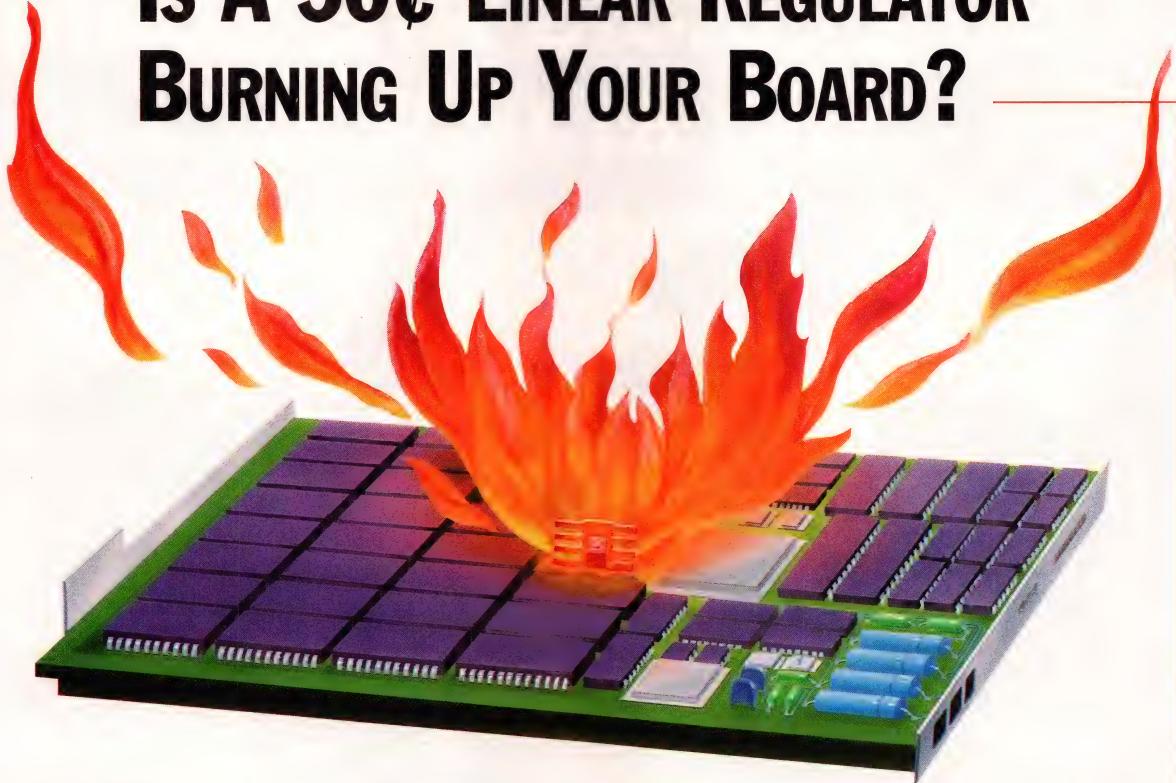2. Eglowstein, Ira, "Friendly Acquisition," *Byte*, July 1994, pg 147.

Senior Technical Editor Brian Kerridge can be reached in the United Kingdom at 508 528435, fax 508 528430.

Is A 50¢ LINEAR REGULATOR BURNING UP YOUR BOARD?



**PLAY IT COOL WITH OUR LOW COST 1 AMP
INTEGRATED SWITCHING REGULATOR**



Do you have a board with a 3-terminal linear regulator that's generating more heat than an irate customer? Are you locked into a tight compact design that leaves no extra space for a larger heatsink?

Fortunately, you can now play it cool with an innovative product from Power Trends – a 1-Amp Integrated Switching Regulator (ISR). Power Trends' 1-Amp ISRs are pin-compatible with existing 3-terminal "78 and 79 Series" linear regulators, fit into the same space, and are just as easy to use. With 85%



efficiency, our ISRs provide a cool replacement alternative for hot linear regulators. Of course they cost more, but they could save you thousands. Specifications include: laser-trimmed output voltages from 3.3 to 12 Volts, calculated MTBF of over 1,000,000 hours, 0.5% line and load regulation, and power densities of 25 to 100 watts per cubic inch. So if you have a heat/space/reliability problem now, or just want to make sure you don't have one in the future – check out Power Trends' super efficient ISRs. Call or write for more information, and ask about samples!

1-800-531-5782.




POWER TRENDS®

1101 North Raddant Road, Batavia, IL 60510 • (708) 406-0900 • Fax (708) 406-0901

CIRCLE NO. 39

EDN September 29, 1994 • 69

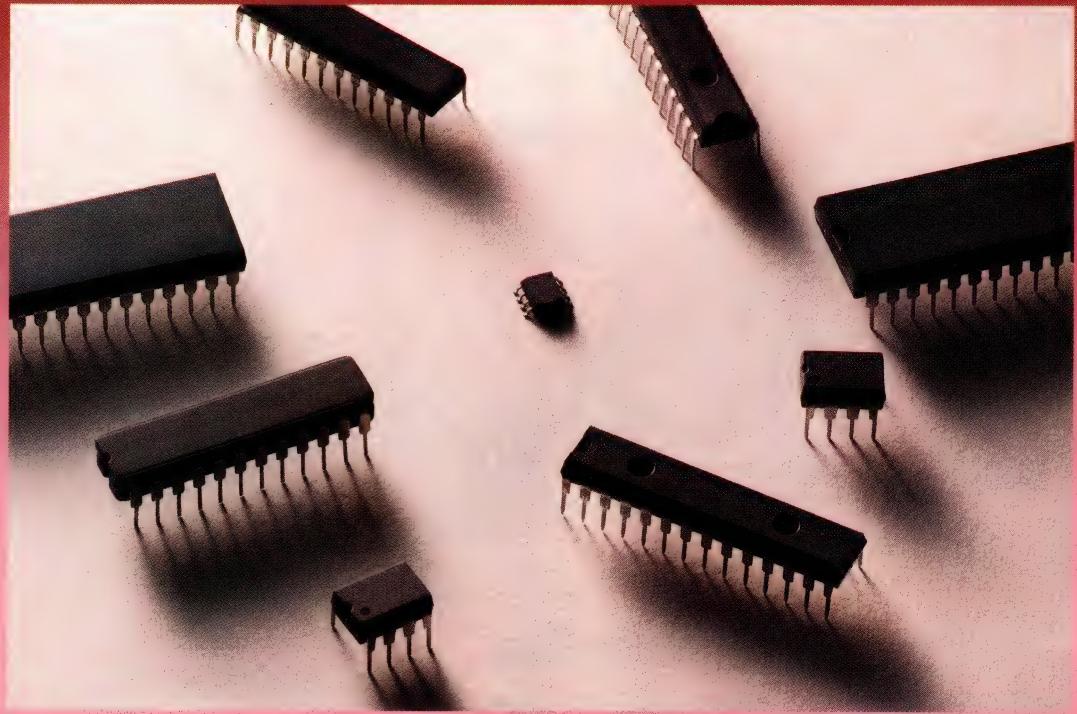Some of Our Competitors Are Really Big in ADCs.




**But we put a 12-bit micropower ADC into
an SO-8 package. For less than \$5.**

With the demand for small, low-cost, battery-powered electronic products accelerating, you face some tough design challenges. Until now, most ADCs were too big, too expensive, and consumed too much power.

You can solve these problems with the industry's smallest, lowest cost, lowest power 12-bit micro-power ADCs, the LTC1286 and the LTC1298. Both devices include a sample-and-hold, serial I/Os, 1- or 2-channel MUX, $\pm 3/4$ LSB maximum DNL, and operate on a single 5V supply.

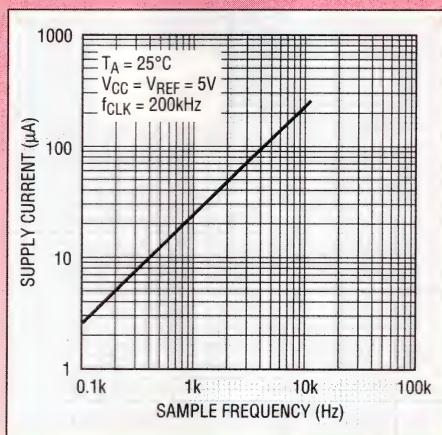Battery operation is extended since the LTC1286 draws only 250 μ A at 12.5ksps, while the



LTC1298 draws 340 μ A at 11.1ksps. Power drain drops even more in auto-shutdown to 20 μ A at 1ksps, and at idle it plunges to 1 nanoamp!

The best news is the price. The LTC1286 and LTC1298 are priced at just \$4.98 for the SO-8 package and \$4.65 for the DIP in 1000 piece quantities.

And for 3V systems, our new LTC1285 and LTC1288 offer the same great features as their 5V counterparts, at even lower power.

For more details, contact Linear Technology Corporation, 1630 McCarthy Boulevard, Milpitas, California, 95035/408-432-1900. For literature only, call 1-800-4-LINEAR.



FROM YOUR MIND TO YOUR MARKET
AND EVERYTHING IN BETWEEN.

CIRCLE NO. 79



DESIGN NOTES

Fast Regulator Paces High Performance Processors

Design Note 87

Mitchell Lee and Craig Varga

New high performance microprocessors require a fresh look at power supply transient response. Pentium™ processors, for example, have current demands that go from a low idle mode of 200mA to a full load current of 4A in 20ns. A transition of the same magnitude occurs as the processor reenters its power saving mode. In addition, the overall supply tolerances have been narrowed significantly from the traditional $\pm 5\%$ for 5V supplies and include transient conditions. When all possible DC error terms are accounted for, the transient response of the power supply when subject to the load step mentioned above must be within $\pm 46\text{mV}$!

To address this problem Linear Technology has developed the LT1585 linear regulator. It features 1% initial accuracy, excellent temperature drift and load regulation, and virtually perfect line regulation. Complementing superb DC characteristics, the LT1585 exhibits extremely fast response to transients. The regulator is offered as an adjustable regulator requiring two resistors to set the operating point, as well as fixed versions which have been trimmed and optimized for 3.3V, 3.38V, 3.45V, and 3.6V outputs. Fixed versions are fully specified for worst-case DC error bounds; in adjustable designs the effects of the external voltage-setting resistors must be taken into account.


Transient response is affected by more than the regulator itself. Stray inductances in the layout and bypass capacitors, as well as capacitor ESR dominate the response during the first 400ns of transient. Figure 1 shows a bypassing scheme developed to meet all of the requirements for the Intel P54C-VR microprocessor. Multiple capacitors are required to reduce the total ESR and ESL, which affect the transient response.

Input capacitors C1 and C2 function primarily to decouple load transients from the 5V logic supply. The values used here are optimized for a typical 5V desktop computer "silver box" power supply input. C5 to C10 provide bulk capacitance at low ESR and ESL, and C11 to C20 keep the ESR and ESL low at high ($>100\text{kHz}$) frequencies. C4 is a damper and it minimizes ringing during settling.

A good place to locate the surface mount decoupling components is in the center of the Pentium socket cavity on the top side of the circuit board. Consider using concentric rings of power and ground plane on the top layer of the board within the socket center for bussing the

L and LTC are registered trademarks and LT is a trademark of Linear Technology Corporation.

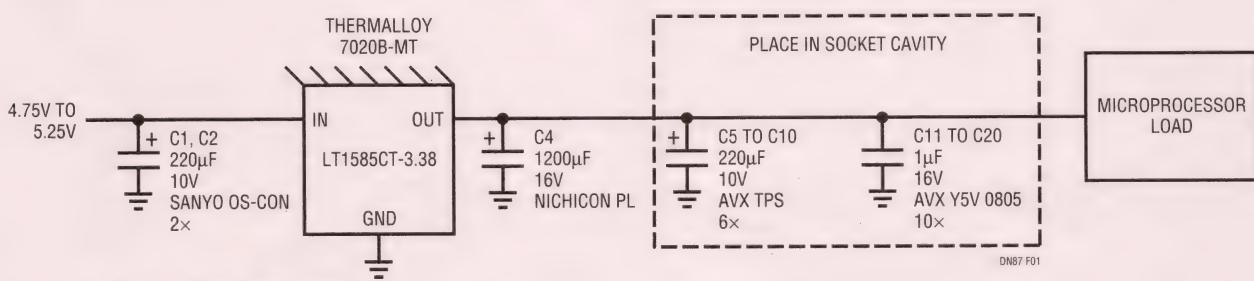Pentium and Power Validator are trademarks of Intel Corporation.



AVX CORPORATION: (803) 448-9411

NICHICON (AMERICA) CORPORATION: (708) 843-7500

SANYO VIDEO COMPONENTS (USA) CORPORATION: (619) 661-6322

THERMALLOY INCORPORATED: (214) 243-4321

FOR CORRECT OPERATION OF MICROPROCESSOR, DO NOT SUBSTITUTE COMPONENTS

Figure 1. Recommended Bypassing Scheme for Correct Transient Response

capacitors together. Tie the main power and ground planes to these cavity planes with a minimum of two vias per capacitor. This will minimize parasitic inductance. The regulator and damper capacitor should be located close to ($<1"$) the microprocessor socket to minimize circuit trace inductance.

Verifying the regulator and microprocessor layout can be accomplished with a controlled load such as the Power Validator™ manufactured by Intel. This device plugs directly into the microprocessor socket and simulates worst-case load transients conditions.

An oscilloscope photograph of the LT1585's response to a worst-case 200mA to 4A load step is shown in Figure 2. Trace C is the load current step, which is essentially flat at 4A with a 20ns rise time. Trace A is the output settling response at 20mV per division. Cursor trace B marks

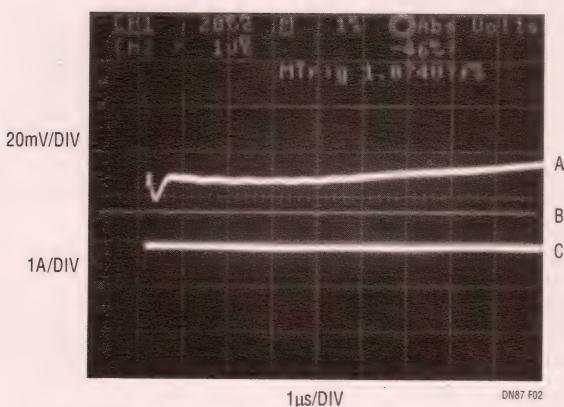


Figure 2. Transient Response at Onset of 4A Load Current Step

-46mV relative to the initial output voltage. At the onset of load current, the microprocessor socket voltage dips to -38mV as a result of inductive effects in the board and capacitors, and the ESR of the capacitors. The inductive effects persist for approximately 400ns. For the next 3μs the output drops as load current drains the bypass capacitors. The trend then reverses as the LT1585 catches up with the load demand, and the output settles after approximately 50μs.

Running 4A with a 1.7V drop, the regulator dissipates 6.8W. The heat sink shown in Figure 1, with 100ft/min air flow is adequate for worst-case operating conditions.

The adjustable version of the LT1585 makes it relatively easy to accommodate multiple microprocessor power supply voltage specifications (see Figure 3). To retain the tight tolerance of the LT1585 internal reference, 0.5% adjustment resistors are recommended. R1 is sized to carry approximately 10mA idling current ($\leq 124\Omega$), and R2 is calculated from:

$$R_2 = \frac{V_O - V_{REF}}{\frac{V_{REF}}{R_1} + I_{ADJ}}$$

where:

$$I_{ADJ} = 60\mu A \text{ and } V_{REF} = 1.250V$$

Figure 3 shows the connections for R1 and R2. Note that C5 to C10 are reduced in value from Figure 1 without compromising the transient response. The addition of C3 makes this possible and also eliminates the need for C4.

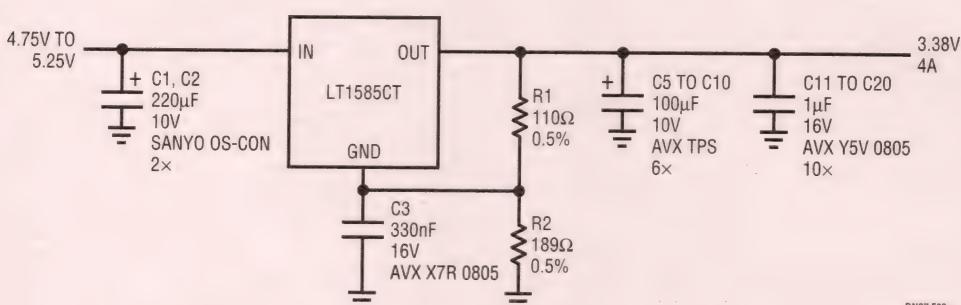


Figure 3. Recommended Adjustable Circuit

For literature on our Linear Regulators,
call **1-800-4-LINEAR**. For applications help,
call (408) 432-1900, Ext. 361

EDITED BY CHARLES H SMALL & ANNE WATSON SWAGER

Spice does digital filters

RICHARD J FAHNREICH, BIO-IMAGING RESEARCH, LINCOLNSHIRE, IL



You can use Spice to simulate digital or discrete time filters as well as analog or continuous time filters. Just as you would use integrator blocks to simulate the 1/s terms for an analog filter, you can use Spice's transmission-line component to simulate the ideal z^{-1} delay elements of digital filters.

Fig 1 shows the block diagram and basic third-order transfer function that describe a digital filter. Simulating this canonical or type II direct form can be insightful because you typically realize IIR digital filters from this form. The basic structure and transfer function are identical to that of an analog filter except that z^{-1} terms replace the analog filter's 1/s terms.


Fig 2 shows a Spice circuit for an ideal delay block using a transmission line. The transmission line statement (T1, T2, and T3 in **Listing 1**) requires you to specify the propagation delay time (TD) or, alternatively, the frequency and wavelength. For this application, the delay time is far more useful because it represents the sampling period of the digital filter. The statement also requires a characteristic impedance, Z_0 . The value isn't critical as long as you terminate the line with a resistor $R1$ of value equal to Z_0 .

To simulate the frequency response of a third-order digital filter, you first typically obtain the filter coefficients by applying the bilinear transform to the analog prototype. The bilinear transform substitutes $s = (2/T) \times (1 - z^{-1}) / (1 + z^{-1})$ into the analog transfer function. Because the bilinear transform distorts the pole and zero locations of the analog filter, you must prewarp the frequencies before applying the transform to obtain the desired response.

The transfer function for a third-order Butterworth digital filter with a 1-kHz cutoff frequency and 10 kHz sampling frequency is

$$H(z) = \frac{0.0181 + 0.0543z^{-1} + 0.0543z^{-2} + 0.0181z^{-3}}{1 - 1.760z^{-1} + 1.1829z^{-2} + 0.2781z^{-3}}$$

Listing 1 is the corresponding Spice netlist, and **Fig 3** shows the simulation result. The response resembles a lowpass filter from dc to the Nyquist frequency of 5 kHz. Note the periodic nature of digital filters: The response repeats itself at a fre-

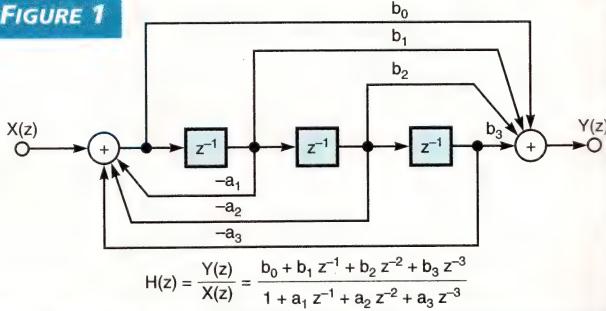FIGURE 1

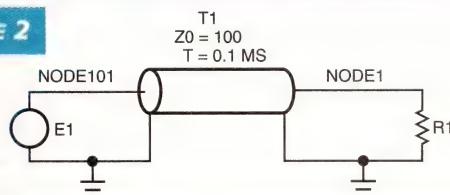
This familiar block diagram and transfer function describe a basic third-order digital filter.

LISTING 1

```

ZTF3.CIR - 3RD-ORDER IIR DIGITAL FILTER
* BUTTERWORTH, LOW-PASS, FC=1000HZ, TS=0.1MS
VS      10    0      AC   1      DC   1
RS      10    0      IE9
*
* TRANSFER FUNCTION, 3RD-ORDER
* FEEDFORWARD AND FEEDBACK - NUMERATOR AND DENOMINATOR COEFFICIENTS
BY 20 0 POLY(4) (11,0) (1,0) (2,0) (3,0) 0 0.0181 0.0543 0.0543 0.0181
EX 11 0 POLY(4) (10,0) (0,1) (0,2) (0,3) 0 1.0000 -1.7600 1.1829 -0.2781
*
R11    11    0      1E9
R20    20    0      1E9
* DELAY 1
E1     101 0  11 0  1
T1     101 0  1 0   Z0=100 TD=0.1MS
R1     1      0      100
* DELAY 2
E2     102 0  1 0   1
T2     102 0  2 0   Z0=100 TD=0.1MS
R2     2      0      100
* DELAY 3
E3     103 0  2 0   1
T3     103 0  3 0   Z0=100 TD=0.1MS
R3     3      0      100
*
.AC LIN 200 1 10000
.TRAN 0.1MS 3MS 0 0.05MS UIC
.PROBE
.END

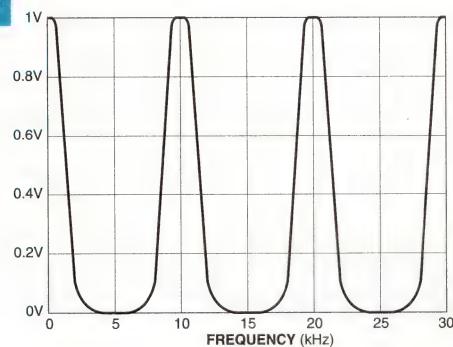
```

FIGURE 2

Spice's transmission-line element serves as the delay or z^{-1} term of a digital filter.

quency interval equal to the 10-kHz sampling frequency. Spice helps you verify that the prewarped frequencies and the bilinear transform produce the required attenuation in the pass and stop bands.

You can also simulate an FIR filter with a similar structure to **Fig 1**, the difference being that an FIR filter's transfer function contains no poles and, thus, the denominator of the

FIGURE 3

This frequency-response plot of a third-order digital filter resembles a lowpass filter from dc to the Nyquist frequency of 5 kHz. This plot helps you verify that the prewarped frequencies and the bilinear transform produce the required attenuation in the pass and stop bands.

transfer function is equal to 1. However, simulating FIR filters may not be practical because they can have several to over one hundred coefficients. Because each coefficient requires a delay line, one FIR filter may require a large Spice file implying long simulation times.

To simulate and analyze the transient response of a digital filter, you must apply the digital filter to a continuous signal and then sample the continuous output of the filter to obtain the discrete-time results. Theoretically this is possible because a system with ideal delay blocks operates equally well with continuous or discrete input signals. Thus, to simulate the time response of a digital filter, you first perform the standard transient analysis with a continuous-time input and then print the output data only at the sampling period intervals. The print interval, 0.1 msec, of the .TRAN statement performs the "sampling." Some versions of Spice automatically set the maximum time step of the transient analysis to one-half msec times the smallest transmission line delay. For this filter, the .TRAN statement explicitly sets the

maximum time step to this value, which is 0.05 msec.

Spice mimics an input step using the 1V dc voltage source (VS) and the .TRAN statement. The presence of the UIC parameter in the .TRAN statement directs Spice not to compute the dc-bias solution. Instead, the UIC parameter uses the value in the .IC statement as the initial transient condition. Because the file doesn't contain an .IC statement and thus doesn't specify any initial conditions, the initial voltage at VS is 0V. Then, at the first time step, VS assumes its dc value of 1V.

You should be aware of the limitations of using Spice to analyze discrete time structures. First, transmission lines consume large amounts of memory during transient analysis. Second, transmission lines with short delay times compared with the total simulation interval can result in long simulation times. (DI #1585)

EDN

To Vote For This Design, Circle No. 375

PC acts as RS-232C protocol analyzer

J S HOLMES, BOEHRINGER MANNHEIM, INDIANAPOLIS, IN



The circuit in Fig 1 is an inexpensive and easy-to-build PC-based alternative to a dedicated protocol analyzer. The circuit taps into an RS-232C line between J_1 and J_2 , and IC_1 's charge pump converts the RS-232C signals to CMOS levels. Many different types of RS-232C charge pumps work well in this circuit. One of the drivers in IC_1 then converts the mixed signal back to RS-232C levels and transmits the data to the PC out of J_3 .

The PC must be running a monitor program to use this data. For applications in which the unit under test transmits and receives ASCII data, a commercial terminal emulator program, such as Procomm or Crosstalk, works well. If, however, the data on the signal line is binary, then Listing 1's QuickBasic program can make the data legible.


The program assumes a data rate of 9600 baud. You must make sure that the monitor baud rate matches the baud rate of the unit under test. The most efficient realization of this program involves putting the communication parameters in a file and reading it in at the beginning of execution. The program then goes into an infinite loop. The loop checks to see if there are any characters in the serial port, checks to see if the escape key is pressed, then repeats. In the event that a character comes into the serial port, it is displayed in ASCII and as a decimal equivalent. If you implement this program in a system that communicates with large numbers of char-

acters, you can send the results to a file instead of to the screen. This will allow you to review the results of the communication attempt in a text editor. (DI #1588)

EDN

To Vote For This Design, Circle No. 376

FIGURE 1

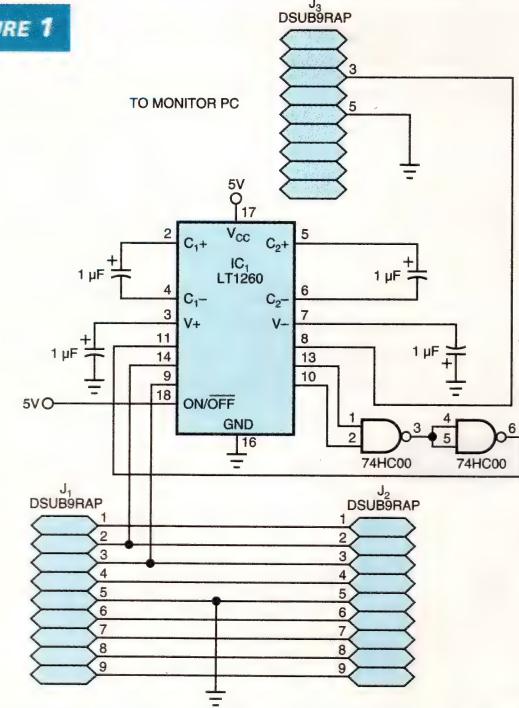

GaAs

SWITCHES

\$2³⁰

DC-2GHz Immediate Delivery from \$2³⁰ (1000 qty.)

Finally! A line of SPDT absorptive, reflective and transfer switches that appeals to your technical side, and business side as well! It's

Mini-Circuits GaAs switches...providing outstanding performance features such as very high isolation (up to 60dB), superfast 3nsec switching speed and excellent compatibility with surface mount

soldering techniques. Additionally, the entire series is built extremely tough and is immediately available from stock with a

1 week shipment guarantee. At only \$2.95 (qty.10), this top-of-the-line value is priced with your bottom line in mind!





To order, call or Fax Mini-Circuits with your requirements today.

Mini-Circuits...we're redefining what VALUE is all about!

Model No.	Freq. (GHz)	Insertion Loss ① dB (max.)	1dB Comp. ① dBm (typ.)	In-Out Iso. ① dB (typ.)	Price \$ea. (qty.10)
MSW-2-20 (Reflective)	DC-2.0	1.0	+24	34	2.95
MSWA-2-20 (Absorptive)	DC-2.0	1.3	+27	40	3.45
MSWT-4-20 (Transfer)	DC-2.0	1.8 TX ② 2.0 RX ③	+28 TX ② +27 RX ③	30	3.95

① Midband, 500-1000MHz ② Transmit ③ Receive

All Units: SOIC 8pin Package

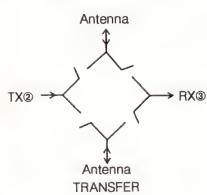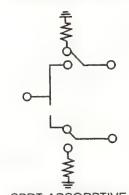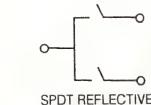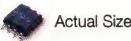

Mini-Circuits®

P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS ...Let Our Experience Work For You.

CIRCLE NO. 84

EDN September 29, 1994 ■ 75

Maximum voltage sorter uses analog multiplexers

ALAN L GILES, TAO SYSTEMS, HAMPTON, VA

The voltage-sorting circuit in Fig 1 continuously finds the maximum of eight input voltages and the corresponding binary address with the aid of two analog multiplexers, IC₁ and IC₂. The circuit compares each input sequentially with the current maximum voltage and updates the maximum voltage and address when it finds a new maximum. IC₂ and IC₃ act as storage elements. IC₄ ensures that latching can't occur at the beginning or the end of a given address, thereby preventing an incorrect address from being latched at an address transition. The sorter can also find the minimum of its input if you swap the CMP01 comparator's input.

The analog multiplexers, which typically have combined switching and settling times of 0.5 to 1.5 μ sec, determine the minimum sorting time of this circuit. Overall sorting time is


limited to about 1 μ sec multiplied by the number of inputs. Given this constraint, you need to determine the desired overall sorting time and set the clock frequency accordingly. If V_{MAX} is used elsewhere, you should buffer it to avoid a voltage drop across the analog multiplexer's on resistance.

You can expand this eight-input sorter to 16 inputs without increasing the chip count by simply using two 16:1 analog multiplexers instead of two 8:1 multiplexers. This circuit already includes the next counter bit and D flip-flop required for the fourth address bit. You can further double the number of inputs to 32 by using three chips to form two 32:1 analog multiplexers. (DI #1586)

EDN

To Vote For This Design, Circle No. 377

FIGURE 1

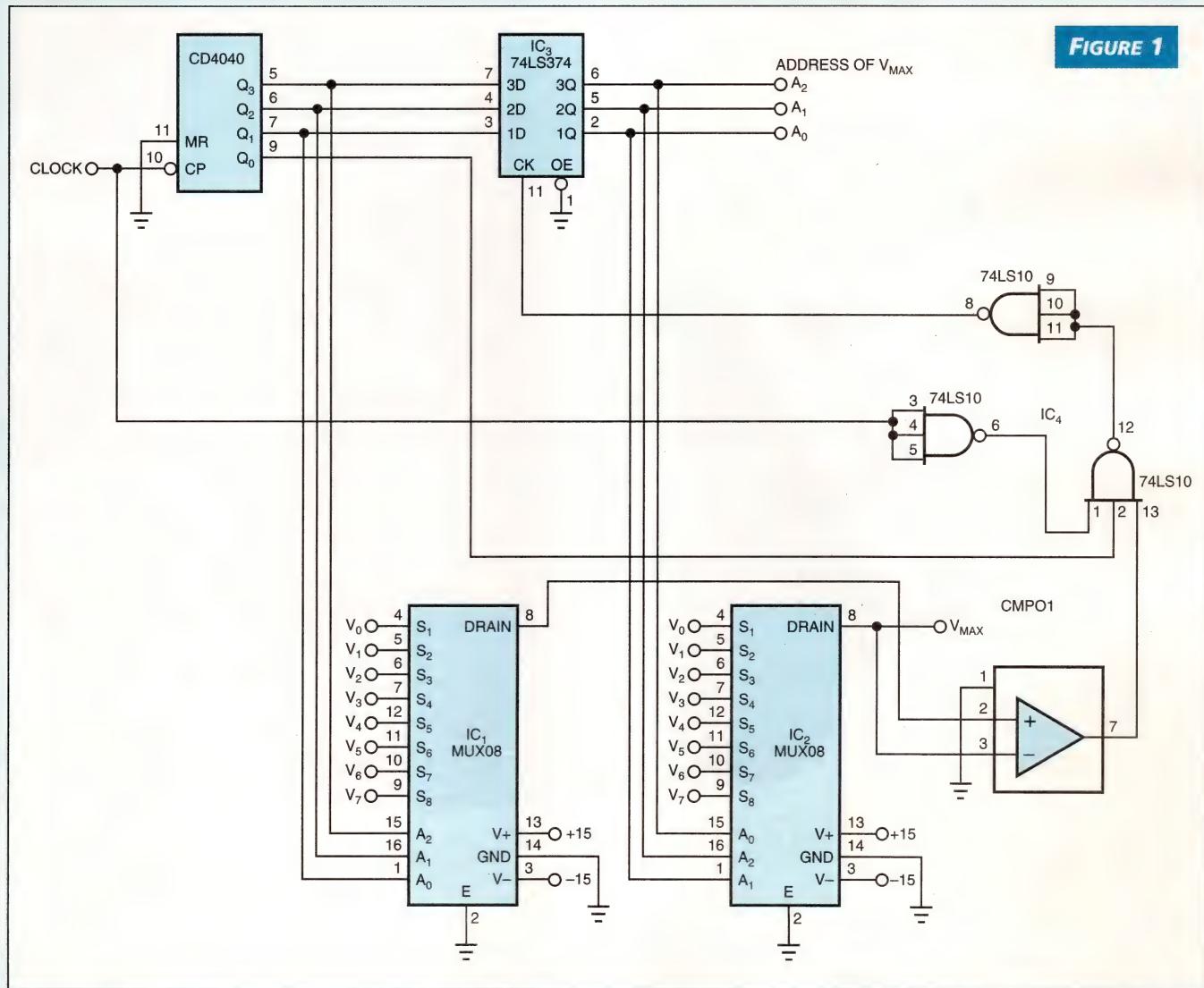


This voltage sorter uses two analog multiplexers to continuously search for the maximum of eight input voltages.

TRIPLE 8-BIT DACs REPLACE TRIMPOTS—ONLY 65¢/DAC[†]

3V and 5V Serial DACs Shut-Down to 1µA

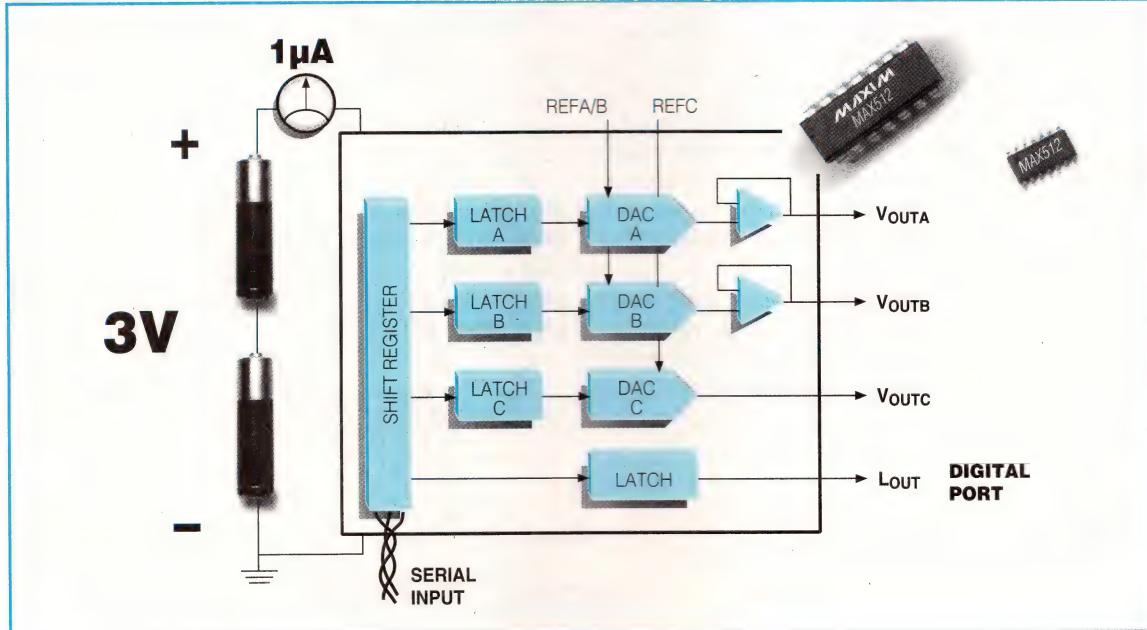Get the **first & only** 3V triple-DACs available, for your next design, and save power, space, and cost. Our new MAX512 and MAX513 low-cost digital-to-analog converters are ideal for your low-power applications, including digitally adjustable RF bias circuits, digital gain and offset adjustments, and programmable attenuators.



- ◆ Three 8-Bit Voltage-Output DACs
- ◆ Single or Dual Supply:
5V or ±5V—MAX512
3V or ±3V—MAX513
- ◆ 1mA Operating Current
- ◆ 1µA Shut-Down Current
- ◆ Guaranteed Monotonic
- ◆ Microwire™, SPI™, QSPI™ Compatible Serial Interface

FREE D/A Converter Design Guide—Sent Within 24 Hours!
Includes: Data Sheets and Cards for Free Samples

CALL TOLL FREE 1-800-722-8266
For a Design Guide or Free Sample

MasterCard® and Visa® are accepted for Evaluation Kits or small quantity orders.



Distributed by Arrow, Bell, CAM RPC, Digi-Key, Elmo, Hamilton Hallmark, Nu Horizons, and Zeus. Authorized Maxim Representatives: AL, EnVision; AZ, Techni Source Inc.; CA, (Northern California) Maxim Integrated Products, (Southern California) Mesa, Infinity Sales, Inc.; CO, Component Sales; CT, Comp Rep Associates; DE, TAI Corporation; FL, Sales Engineering Concepts; GA, EnVision; ID, E.S. Chase; IL, Industrial Representatives, Inc; IN, Technology Marketing Group; IA, JR Sales Engineering, Inc.; KS, Deltron; LA, Maxim Integrated Products, Inc.; MD, Micro Comp, Inc.; MA, Comp Rep Associates; MI, Micro Tech Sales; MN, Mel Foster Technical Sales, Inc.; MO, Deltron; MT, E.S. Chase; NE, Deltron; NH, Comp Rep Associates; NJ, Parallax, TAI Corporation; NM, Techni Source Inc.; NY, Parallax, Reagan/Compar; NC, EnVision; OH, Lyons Corporation; OK, Maxim Integrated Products, Inc.; OR, E.S. Chase; PA (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; SC, EnVision; TX, Maxim Integrated Products, Inc.; UT, Luscombe Engineering Co.; VA, Micro-Comp, Inc.; WA, E.S. Chase; WI, Industrial Representatives, Inc.

Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.

Austria, Allmos Electronics Belgium, Master Chips Denmark, Arrow-Exatec A/S Finland, Yleiselektronika Oy, France, Maxim France, France/Distributors: Maxim France, ASAP Germany, Maxim GmbH Germany/Distributors: Maxim GmbH, Spezial Electronic KG Ireland, FMG Electronics Italy, Consystem S.r.l., Italy/Distributor: Esco Italiana Electronics Supply Netherlands, Koning En Hartman Norway, Berendsen Technology Poland, Uniprod, Ltd. Portugal, ADM Electronics, S.A. Spain, ADM Electronics S.A. Sweden, Egevo AB Switzerland, Laser & Electronics AG Turkey, Interex (U.S.A.) U.K. Maxim Integrated Products (U.K.), Ltd., U.K./Distributors: Maxim Integrated Products (U.K.), Ltd., 2001 Electronic Components, HB Electronic

†MAX512 10,000 pc. price is \$1.95, FOB USA

*SPI and QSPI are trademarks of Motorola, Microwire is a trademark of National Semiconductor.

Maxim is a registered trademark of Maxim Integrated Products. © 1994 Maxim Integrated Products

Frequency comparer produces binary results

JAY KIRSCHENBAUM, COLUMBIA UNIVERSITY, NEW YORK, NY

Instead of resorting to full-blown frequency counters, the simple circuit in Fig 1 uses four ICs to rapidly compare the frequency of two pulse trains. The circuit produces a binary 0 if f_1 is greater than f_2 and a binary 1 if f_1 is less than f_2 . The circuit exploits the fact that inevitably two consecutive leading edges of the higher frequency pulse train will follow each other in time without an intervening leading edge from the other pulse train. The circuit uses two pairs of flip-flops, IC₂ and IC₃, as 2-bit binary counters. A dual monostable multivibrator, IC₁, marks the leading edges of the input pulses by producing spikes of approximately 100 nsec in duration. The circuit couples each stream of spikes to the clock input of one counter and to the reset input of the other.

When one counter's clock receives two consecutive spikes without the arrival of an intervening reset pulse, the high-order bit of that counter goes high. Then, a latch formed by two NOR gates of IC₄ sets or resets depending on which of

the two pulse trains has the higher frequency. If f_1 is greater than f_2 , the latch resets to 0; if f_1 is less than f_2 , the latch sets to 1. The latch holds its state until there is a change in the relative magnitudes of the two frequencies.


For frequencies f_1 and f_2 , the maximum response time of the circuit is given by the following

$$T_{MAX} = \frac{1}{f_1} \times \frac{f_2}{\Delta f}, f_2 > f_1.$$

At 1 kHz and for f_1 and f_2 within 1% of each other, the circuit responds within 100 msec. One important note: The circuit is designed to handle asynchronous pulse trains, and it won't work if f_1 and f_2 are synchronous integral multiples of each other. (DI #1587) www.edn.com/design/digital/1587 EDN

To Vote For This Design, Circle No. 378

FIGURE 1

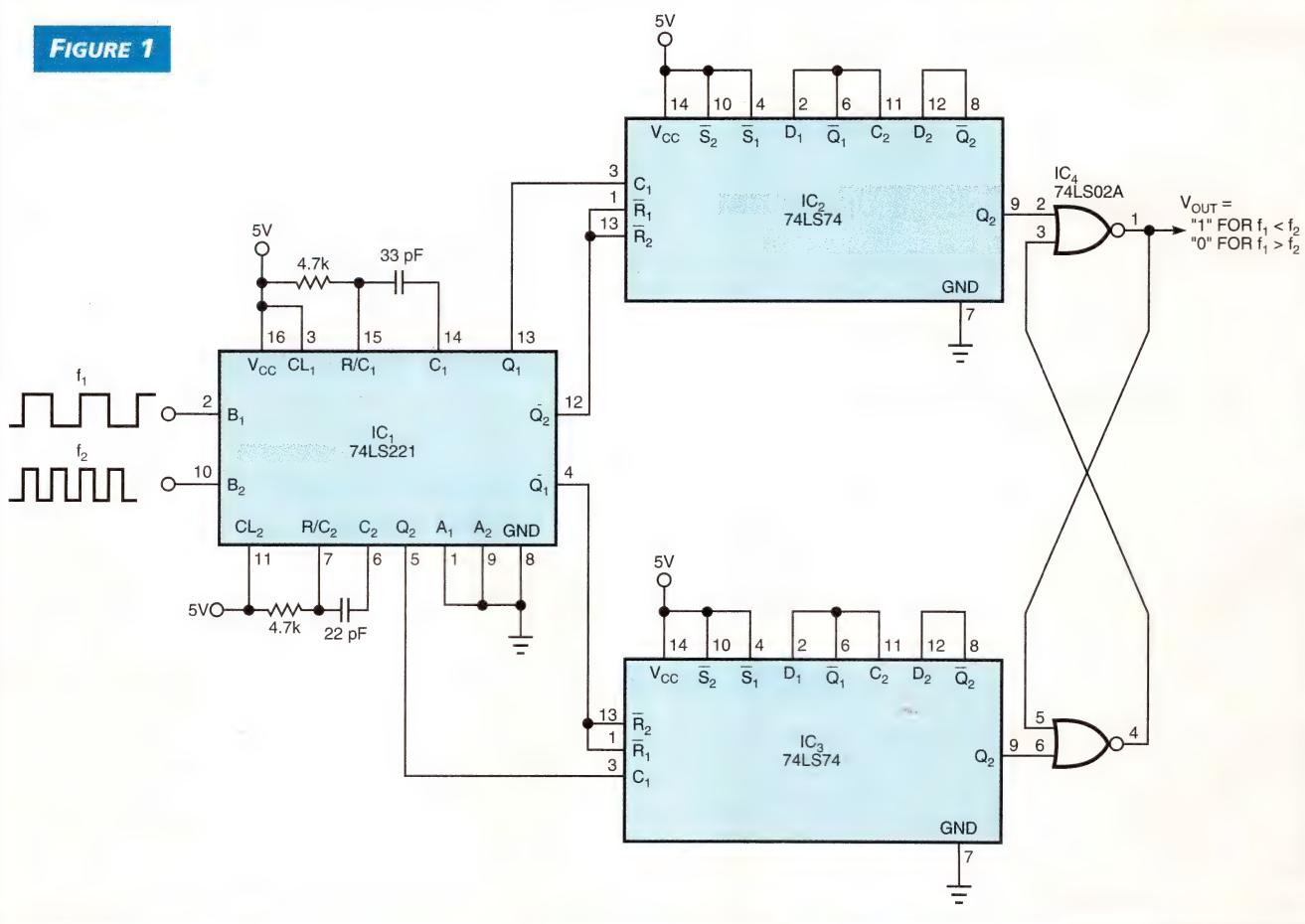


If f_1 is greater than f_2 , the output of this frequency comparer is a 0; if f_1 is less than f_2 , the output is a 1.

REPLACE "8" 13-BIT DACS AND "8" AMPS WITH ONE IC!

Upgrade Your 12-Bit System to 13-Bits at Only \$3.70/DAC*

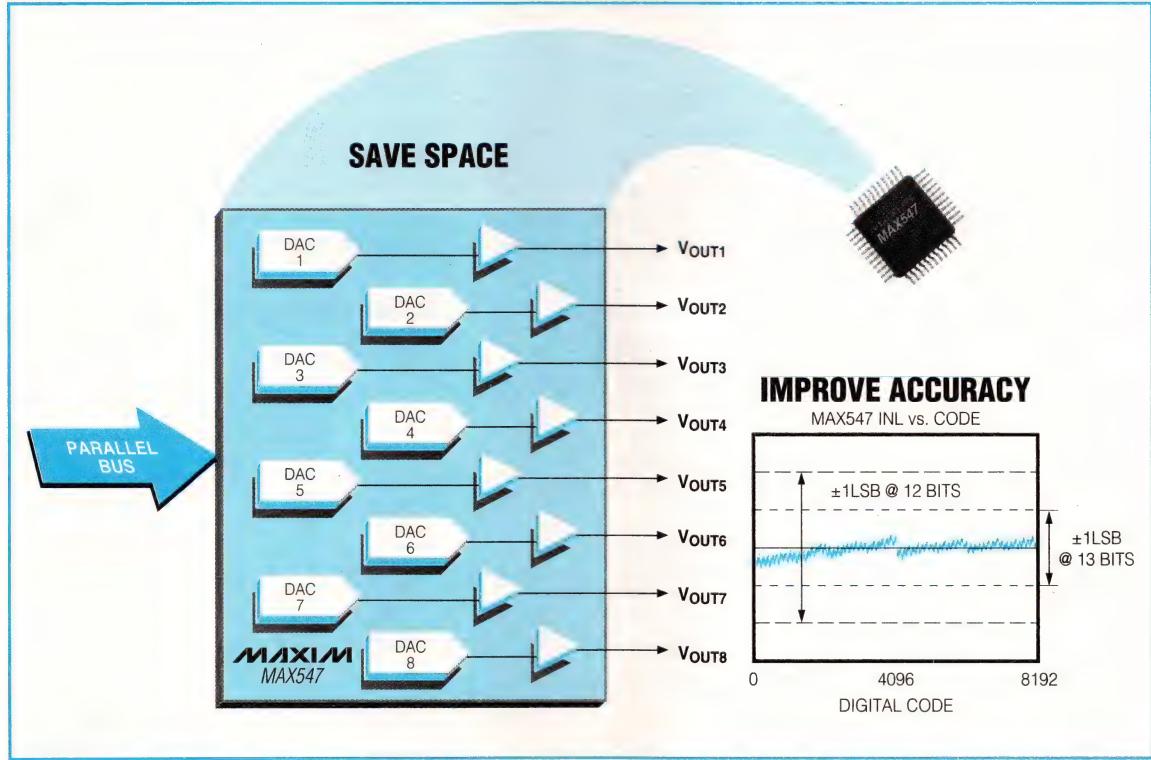The new MAX547 fits eight 13-bit DACs with output amplifiers in the space of one, while providing twice the resolution of 12-bit alternatives.



- ◆ Buffered Voltage Outputs
- ◆ Guaranteed Monotonic Over Temperature
- ◆ Unipolar or Bipolar Output Ranges
- ◆ High-Speed Parallel Interface
- ◆ Available in PLCC or Flatpack

FREE D/A Converter Design Guide—Sent Within 24 Hours!
Includes: Data Sheets and Cards for Free Samples

CALL TOLL FREE 1-800-722-8266
For a Design Guide or Free Sample

MasterCard® and Visa® are accepted for Evaluation Kits or small quantity orders.



MAXIM



Distributed by Arrow, Bell, CAM RPC, Digi-Key, Elmo, Hamilton Hallmark, Nu Horizons, and Zeus. Authorized Maxim Representatives: **AL**, EnVision; **AZ**, Techni Source Inc.; **CA**, (Northern California) Maxim Integrated Products, (Southern California) Mesa, Infinity Sales, Inc.; **CO**, Component Sales; **CT**, Comp Rep Associates; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, EnVision; **ID**, E.S. Chase; **IL**, Industrial Representatives, Inc; **IN**, Technology Marketing Group; **IA**, JR Sales Engineering, Inc.; **KS**, Deltron; **LA**, Maxim Integrated Products, Inc.; **MD**, MicroComp, Inc.; **MA**, Comp Rep Associates; **MJ**, Micro Tech Sales; **MN**, Mel Foster Technical Sales, Inc.; **MO**, Deltron; **MT**, E.S. Chase; **NE**, Deltron; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, EnVision; **OH**, Lyons Corporation; **OK**, Maxim Integrated Products, Inc.; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, EnVision; **TX**, Maxim Integrated Products, Inc.; **UT**, Luscombe Engineering Co.; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase; **WI**, Industrial Representatives, Inc.

Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.

Austria, Allmos Electronics **Belgium**, Master Chips **Denmark**, Arrow-Exatec A/S **Finland**, Yleiselektronikka Oy, **France**, Maxim France, **France/Distributors**: Maxim France, ASAP **Germany**, Maxim GmbH **Germany/Distributors**: Maxim GmbH, Spezial Electronic KG **Ireland**, FMG Electronics **Italy**, Consystem S.r.l., **Italy/Distributor**: Esco Italiana Electronics Supply **Netherlands**, Koning En Hartman **Norway**, Berendsen Technology **Poland**, Uniprod, Ltd. **Portugal**, ADM Electronics, S.A. **Spain**, ADM Electronics S.A. **Sweden**, Egevo AB **Switzerland**, Laser & Electronics AG **Turkey**, Interex (U.S.A.) **U.K.**, Maxim Integrated Products (U.K.), Ltd., **U.K./Distributors**: Maxim Integrated Products (U.K.), Ltd., 2001 Electronic Components, HB Electronic

Maxim is a registered trademark of Maxim Integrated Products. © 1994 Maxim Integrated Products

Power amplifier has transient rail-to-rail swing

YISHAY NETZER, YUVALIM, ISRAEL

Fig 1a's conventional common-drain MOSFET-based power op amp, with a simple and stable configuration, has a dynamic response identical to that of IC₁. However, as a power amplifier, it exhibits a limited-output voltage swing that is typically less than either supply by 6V. This limitation results from the combination of the turn-on voltage of the MOSFET transistors and the limited voltage swing of the monolithic op amp. Usually this deficiency is overcome by an auxiliary pair of higher voltage power supplies for the monolithic op amp. Alternatively, other suggested configurations combine an op amp with a complementary common-source power stage. However, these configurations are inherently unstable and difficult to compensate because of the added wideband gain of the output stage.


In reality, a large voltage swing is necessary only in transient situations and not in the steady state. This is typical of

loudspeaker drivers as well as servo-motor drivers. The modified power op amp in **Fig 1b** attains transient rail-to-rail voltage swing by adding just a few passive components to **Fig 1a's** design. The bootstrapping mechanism implemented by clamping network R₁, C₁, D₁, and D₂ for the positive power supply and by R₂, C₂, D₃, and D₄ for the negative power supply automatically increases the op amp's supply voltage when necessary. R₁ limits the boost amount and protects the output voltage from destroying D₁ and D₄. Along with the supply current of the op amp, C₁ and C₂ determine the cut-on frequency above which the output-voltage-swing range starts to increase. The range is typically 300 Hz for the values in the figure. (DI #1589)

EDN

To Vote For This Design, Circle No. 379

FIGURE 1

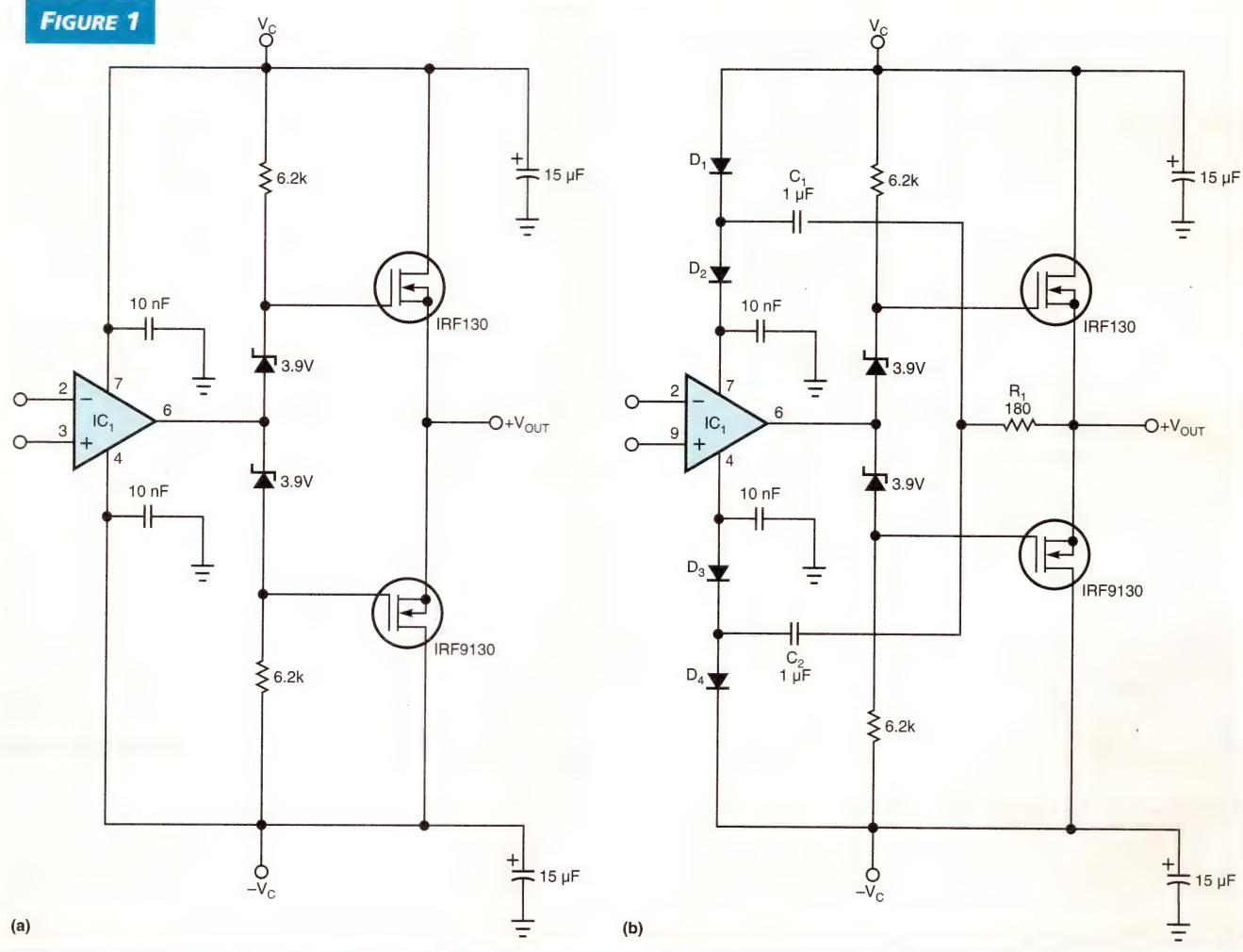

By adding bootstrapping components to the circuit in (a), which has a limited output swing, the circuit in (b) provides a transient rail-to-rail output swing.

Check Out the Standard in Power Components

ISO 9001 Certified

Worldwide Agency Approvals

Largest Selection of Input/Output Combinations in the Industry

Over 2.5 Million Modules in the Field

1-800-735-6200



Component Solutions For Your Power System

Vicor Corporation 23 Frontage Road, Andover, MA 01810 USA • TEL: (508) 470-2900 • FAX: (508) 475-6145

Vicor GmbH Carl-Von-Linde-Strasse 15 D-85748 Garching-Hochbruck, Germany • TEL: +49-89-329-2763 • FAX: +49-89-329-2767

Vicor Far East 6F-3A, 293 - 3 FU-Hsing S. Rd. Sec. 2, Taipei, Taiwan, R.O.C. • TEL: +886-2-73643490 • FAX: +886-2-7337341

VICOR

*Lower cost and **twice** the PERFORMANCE:*
Introducing the Extraordinary
WINDOW RAM.

*[In GUI applications, it eats VRAMs for **LUNCH.**]*

Nowadays, graphical user interfaces are everywhere. But they're also terribly slow.

We at Samsung decided it was time somebody fixed that.

Which is why we've designed a new product—with a new architecture—that not only outperforms VRAMs*

but sells for much less.

The 8-Mbit Window RAM gives you a $1024 \times 1024 \times 8$ -bit frame buffer.

Its 20 ns extended data out Fast Page Mode will give you a minimum of 33% more speed than the fastest VRAMs. And the Window RAM incorporates several dedicated GUI-

accelerating features. All of which means that—yes—it eats VRAMs for lunch.

You'll find that the Window RAM's familiar interface makes designing with it easy. And you'll also find that a new generation of graphics controllers will support it. So you'll not only be able to put the Window

*SURPASSES VRAMS IN PERFORMANCE BY UP TO 180% IN BENCHMARKS. © SAMSUNG SEMICONDUCTOR, INC., 1994.

Samsung's Highly Innovative WRAM (and Also Our VRAMs.)

PART	ORG.	ACCESS TIME	ULTRA FAST PAGE CYCLE TIME	VOLTAGE
KM4232W259	256K x 32	60 ns	20 ns	5.0V
KM4232X259	256K x 32	60 ns	20 ns	3.3V

WRAMs in 120-pin PQFP. Also available: our state-of-the-art 1-meg and 2-meg VRAMs: KM4216C256 and KM4216C258 (both 256K x 16), KM428C256 and KM428C257 (both 256K x 8), in both 5 and 3.3 volt.



RAM to use, you'll be able to do it almost effortlessly.

We're able to offer the chip at a low cost because of its streamlined design, which eliminates the unused overhead that comes with VRAMs—such as serial write, write transfer, and flash write.


And with this kind of performance at this kind of cost, we're confident the Window RAM will be chowing down on VRAMs for some time to come.

For information on designing-in this latest piece of memory wizardry from Samsung, call 1-800-446-2760 or

408-954-7229 today. Or write to WRAM Marketing, Samsung Semiconductor Inc., 3655 N. First St., San Jose, CA 95134.



SEMICONDUCTOR
A Generation AHEAD.

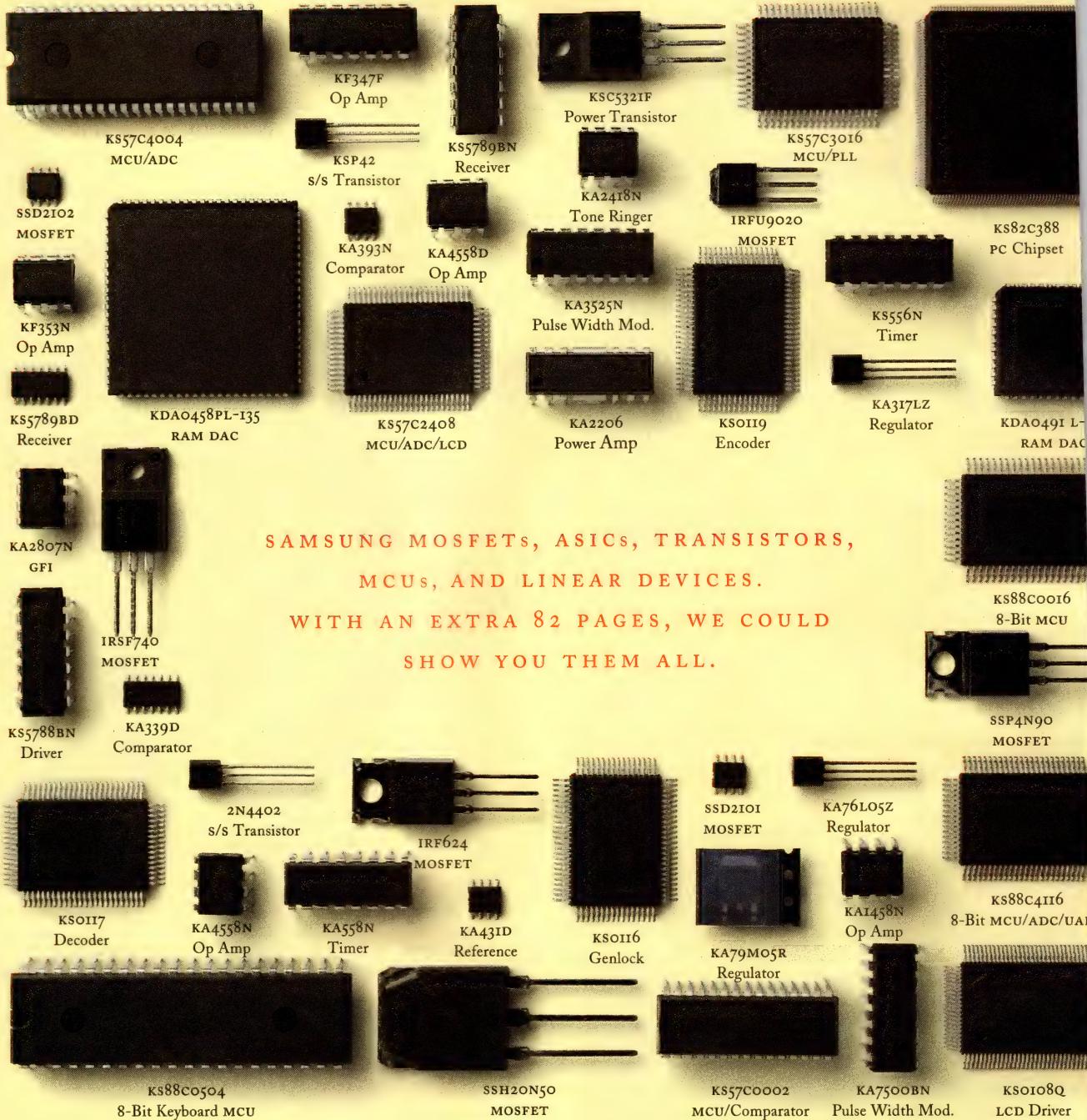

SAMSUNG MOSFETS, ASICS, TRANSISTORS,
MCUS, AND LINEAR DEVICES.
WITH AN EXTRA 82 PAGES, WE COULD
SHOW YOU THEM ALL.

Four thousand, one hundred thirty seven. At last count, that's the number of discrete devices, ASICs, microcontrollers, and linear devices that Samsung makes. Or about 42 times the number shown by the rather small smattering on these two pages.

Many people are surprised to learn that Samsung is one of the


largest suppliers of these parts on earth. However, a number like 4,137 may make this fact a little less surprising.

Our product line is among the broadest available anywhere, and may in fact be compared with Motorola's and Texas Instruments'.

Fine, you are perhaps saying just about now. But why does

this interest me?

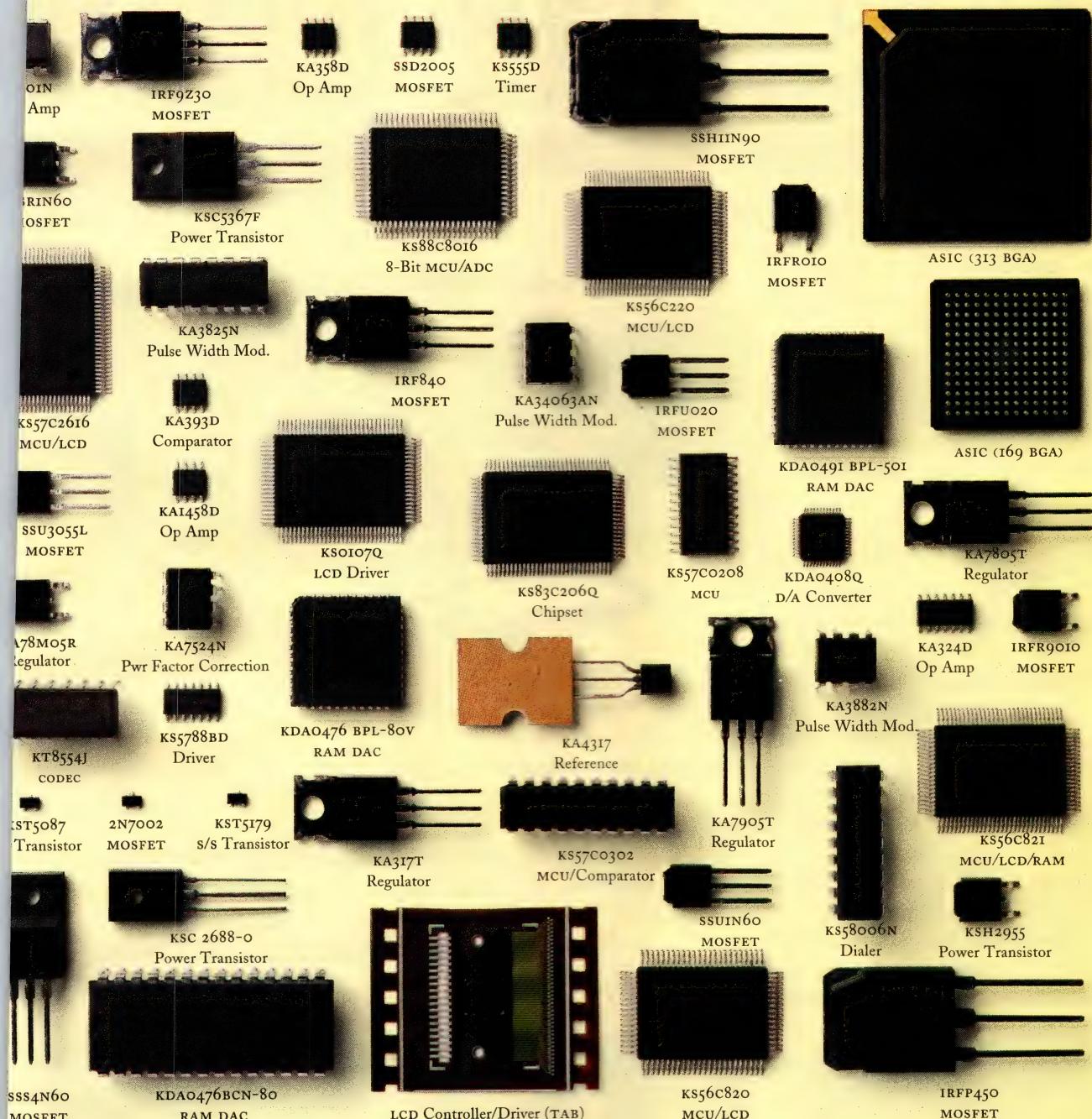Two reasons. First, because we'll help you cut down on the number of vendors you use. After all, since we make so many products, it does mean you can get all those products from one place. (A place, incidentally, that you may well be doing business with already, in these parts or in



memory products, where we're the world leader.)

Second reason: as one of the largest industrial firms and one of the largest semiconductor makers in the world, we're here to stay.

Which means we represent an extremely stable and reliable source of supply. And our products are so superior in quality that the entire

offering has won the coveted ISO 9001 Certification.

If you build something electrical, electronic, or with electrical or electronic components, we almost certainly make parts for it.

For a more complete product listing, or for information that will help you qualify Samsung, please call 1-800-446-2760 or

408-954-7229 today. Or write to Micro Marketing, Samsung Semiconductor Inc., 3655 North First Street, San Jose, CA 95134.

It will help us avoid running an 84-page ad.

SAMSUNG
SEMICONDUCTOR

A Generation AHEAD.

Dynamic Signal Analysis with SRS FFT Spectrum Analyzers


The new SR770 FFT Analyzer

has the outstanding performance and value you've come to expect from SRS Spectrum Analyzers – 90 dB dynamic range, 100 kHz real-time bandwidth – plus a versatile synthesized source that generates clean sinewaves, two-tone signals, white and pink noise, and chirps.


The low distortion (-80 dBc) source is internally synchronized to generate frequency response measurements accurate to 0.05 dB. Both the SR760 and the SR770 quickly perform harmonic, band, sideband and 1/3 octave analysis. Additional capabilities including data tables, GO/NO GO testing and selective windowing bring performance and versatility to every measurement.

- 476 µHz to 100 kHz frequency range
- 90 dB dynamic range
- Low distortion source (SR770 only) – sine, two-tone, chirp, white and pink noise
- 3.5 inch DOS formatted disk drive
- Direct hardcopy to printers and plotters
- GPIB, RS-232 and printer interfaces

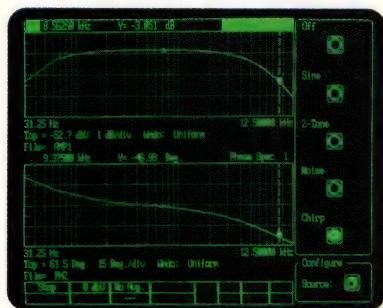
SR770 \$6500 **SR760** \$4750 (U.S. list)



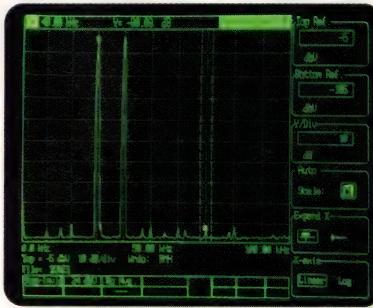Frequency response - Using the SR770's low distortion synthesized source, Bode plots of amplitude, phase and group delay are quickly generated.



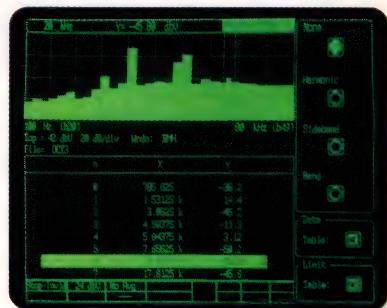Two-tone response - Intermodulation products at -90 dBc are easily measured with the outstanding dynamic range of the SR760 and SR770.



Data analysis - Easy to use analysis functions include 1/3 octave, band, sideband and THD. Math functions and a responsive marker provide power and flexibility.



STANFORD RESEARCH SYSTEMS

1290-D Riemwood Avenue • Sunnyvale, CA 94089
TEL (408)744-9040 • FAX 4087449049

CIRCLE NO. 103

To build data-acquisition systems that run from 5 or 3.3V, know your ICs

KERRY LACANETTE, NATIONAL SEMICONDUCTOR CORP

Continued demands for lower power, lower cost systems increase the likelihood that your next mixed-signal design will operate from a single 3.3 or 5V power supply. Doing away with traditional ± 15 V analog power supplies can help you to meet your power and cost goals, but it also will eliminate some of your design options.

Fortunately, when you select a data-acquisition system's most critical component, the ADC, you have many low-voltage parts from which to choose. But after you pick an ADC, critical decisions still lie ahead. This article looks at how low-voltage ADCs, amplifiers, and other components work together in practical systems, and how you can avoid some of the most common problems that occur when you combine these functions in low-voltage equipment.

Most low-voltage ADC and DAS (data-acquisition system) chips are designed for easy analog and digital interfacing. The ICs' digital interfaces are generally compatible with popular microcontrollers, and the devices can almost always accept analog input signals that range from ground to the positive supply voltage; the span is set by an internal or external band-gap voltage reference. Virtually all ADCs that operate from 5V or less are CMOS devices that use arrays of switches and capacitors to perform their conversions. Although the architectural details vary from design to design, the input stage of this type of converter usually includes a switch and a capacitor that present a transient load to the input signal source. **Fig 1**'s simplified schematic shows how these input stages affect the circuits that drive them.

R_{ON} is not a separate component; it is the on-resistance of the internal analog switch. Sampling capacitor C_s connects to an internal bias voltage whose value depends on the ADC's architecture. In a sampling ADC, the switch closes once per conversion, during the acquisition (sampling) time.

The on-resistances of the sampling switches range from about 5 to 10 k Ω in many low-resolution successive approximation ADCs to 70 Ω in some multistep or half-flash converters. The capacitors can be as small as 10 pF in lower res-


Data-acquisition systems that take power from a single 3.3 or 5V supply share many design considerations with systems that run from ± 15 V. Some concerns are unique to low-voltage, single-supply operation, however. To avoid problems, you need a thorough understanding of the ICs you use.

olution successive-approximation converters and 100 pF or more in higher resolution devices.

When the sampling switch closes, the capacitor begins to charge through the switch and source resistances. After a time interval that is usually controlled by counters or timers within the ADC, the switch opens, and the capacitor stops charging.

The time during which the switch is closed and the capacitor charges is called the "acquisition time." As long as the source impedance is low enough, the capacitor has time to charge fully during the sampling period, and no conversion errors occur. Most input stages are conservatively designed and can work properly at their rated speeds with a reasonable source resistance (1 k Ω is common). Larger source imped-


FIGURE 1

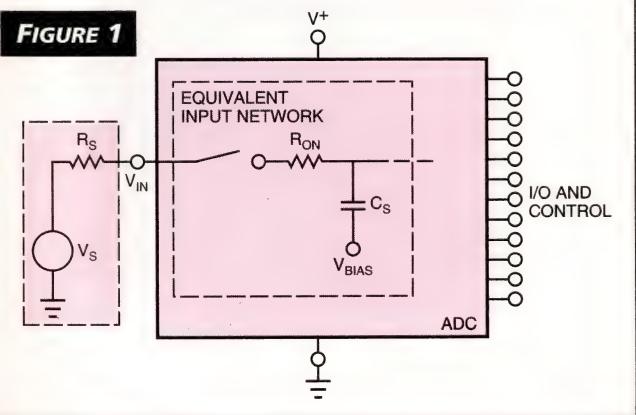

This circuit is a simplified version of the load that a low-voltage ADC presents to a signal source. The capacitor is normally referred to a bias voltage between ground and V+. When you connect a low-voltage ADC to a signal source, the source impedance, the on-resistance of the internal switch, and the sampling capacitor form a network whose time constant may be too long for accurate sampling of the input voltage.


LOW-VOLTAGE DATA ACQUISITION

FIGURE 2

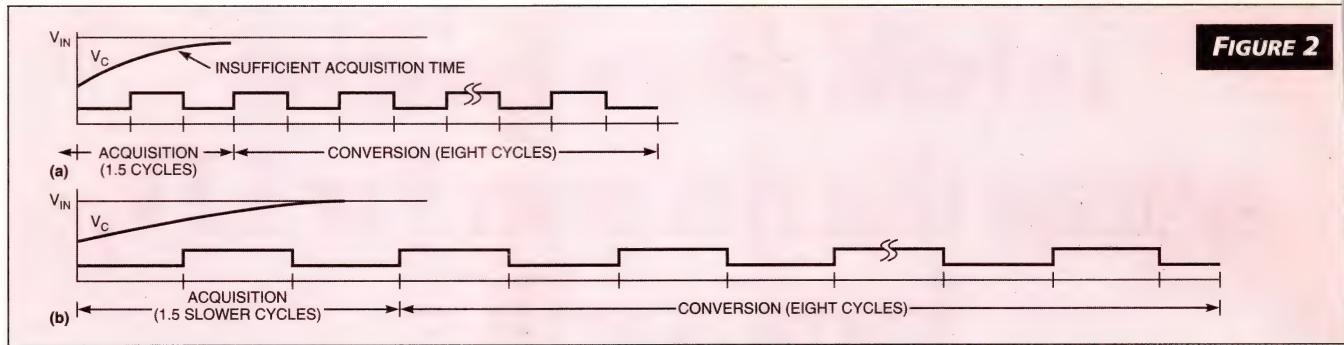

A low-voltage ADC that is designed to operate properly with source resistances under $1\text{ k}\Omega$ may encounter conversion errors if the source resistance increases to $2\text{ k}\Omega$ (a). The larger source resistance prevents the voltage on the internal sampling capacitor from fully charging during the ADC's acquisition time (1.5 clock cycles in this case). When the source impedance is too high to allow accurate signal capture during the nominal acquisition time, you can often extend the duration of the acquisition window by slowing the converter clock (b). This approach slows conversion, however. A good alternative is to slow the clock only during acquisition and then return to the normal clock rate during the conversion itself.

FIGURE 3

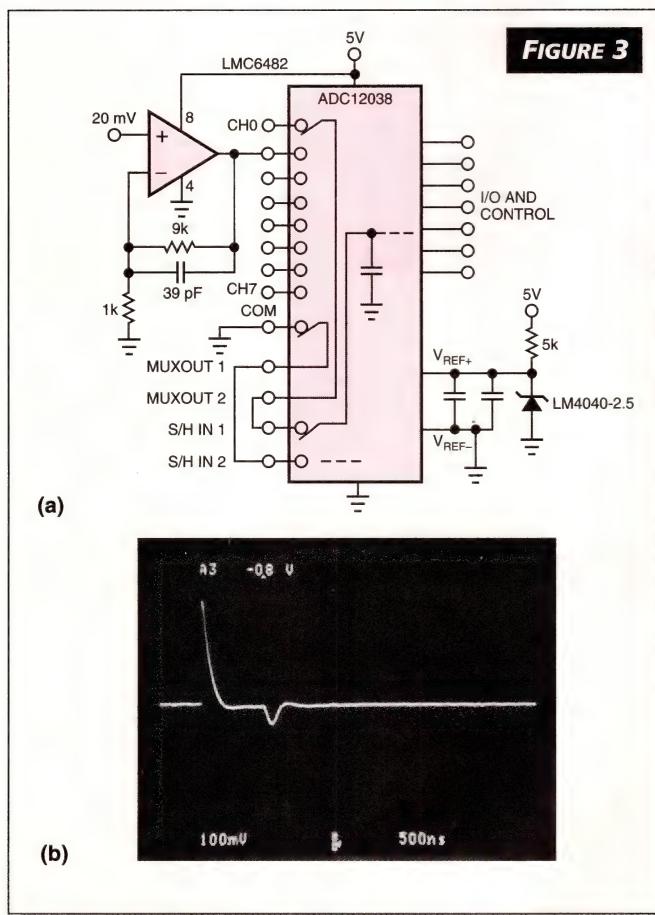

Even a load that should be easy for an op amp to drive can disturb the amplifier if the load suddenly switches to the amplifier's output (a). This typical amplifier-ADC combination operates from a 5V supply. The scope photo (b), shows how the low-voltage CMOS op amp in (a) responds to the switching transients at the ADC input. The amplifier's output settles to within 1 LSB 1.5 μsec after the start of the ADC's acquisition period. Use the ADC's adjustable acquisition time to ensure that the acquisition window doesn't close until the amplifier settles.

ances slow the charging of the sampling capacitor and cause significant errors unless you take steps to avoid them.

Source resistance can be unsettling

When the source impedance is high enough to degrade the conversion accuracy, a simple remedy is to increase the acquisition time to allow the capacitor more time to charge. The acquisition time depends on the conversion technique and other ADC characteristics. Often, you can adjust the acquisition time externally. For example, many sampling successive-approximation converters are clocked devices that sample the input signal for a specific number of clock cycles. Although you can adjust these devices' acquisition time simply by altering the clock frequency, doing so is not always desirable, because slowing the ADC's clock also lowers the conversion speed. Assuming that the loss in conversion speed is acceptable, this technique can increase the acquisition time by as much as two or three orders of magnitude, depending on the ADC. Check the ADC data sheet to verify that the converter operates properly at a sufficiently slow clock frequency; leakage currents that discharge the internal capacitors and cause conversion errors if the clock is too slow dictate most clocked ADCs' minimum clock frequencies.

As an example, imagine that the ADC in Fig 1 is designed to yield correct conversion results for source resistances less than $1\text{ k}\Omega$ when using a 4-MHz clock. Signal acquisition takes 1.5 clock cycles, and conversion takes eight more, so the nominal acquisition-plus-conversion time is $375\text{ nsec} + 2\text{ }\mu\text{sec} = 2.375\text{ }\mu\text{sec}$. If the source resistance increases to $2\text{ k}\Omega$, the nominal acquisition time is no longer sufficient. Fig 2a shows that at the nominal clock frequency, the sampling capacitor doesn't charge fast enough to ensure accurate conversions. If the system must operate properly with a $2\text{-k}\Omega$ source, you must double the acquisition time to 750 nsec. An easy way to do this is simply to halve the clock frequency. This doubles the acquisition-plus-conversion time to 4.75 μsec and slows the throughput rate accordingly. In Fig 2b, the clock frequency is halved, and the capacitor can charge sufficiently during the acquisition time.

When conversion time is critical, you may not be able to cut the throughput rate in half to accommodate a high

source impedance. Instead, you can run the clock at full speed during conversions and slow it only during the acquisition period. In this case, the total acquisition-plus-conversion time becomes $750 \text{ nsec} + 2 \mu\text{sec} = 2.75 \mu\text{sec}$, a significant improvement compared with $4.75 \mu\text{sec}$.

You can also eliminate the effects of high source resistance by using a buffer amplifier ahead of the ADC. This approach requires an additional component, but accommodates very high source impedances with little or no loss in sampling rate, especially if you use a CMOS amplifier. Low-voltage amplifiers have limitations of their own, but they are sometimes the only solution when signals originate in high-impedance sources.

The amplifier/ADC interface

A discussion of low-voltage data acquisition isn't complete unless it considers amplifiers. Operational amplifiers are nearly always present in data-acquisition systems, performing basic signal conditioning ahead of the ADC. Their interactions with ADCs affect system performance. Although many amplifiers are good at driving a variety of static loads, the switched nature of the ADC input stage can introduce problems with some amplifiers, especially the low-power, low-speed devices that are most likely to be used in 3 and 5V systems. Using the simple model of **Fig 1**, the load presented to the amplifier by the ADC input keeps switching abruptly between an open circuit and a series RC network connected to an internal voltage source. The op amp's response to the sudden load-current and impedance change depends upon several parameters. Among them are the device's gain-bandwidth product, slew rate, and output impedance.

Fig 3a shows a low-voltage CMOS operational amplifier wired for a closed-loop gain of +10 and operating from a 5V supply. It drives one of the inputs of an ADC12038, a 5V, 12-bit CMOS ADC with eight analog input channels. The ADC's input network comprises $1.6 \text{ k}\Omega$ of series resistance and 75 pF of capacitance.


The oscilloscope photo in **Fig 3b** shows the output of the amplifier when it drives the ADC. In this case, the amplifier is an LMC6482 dual CMOS op amp with rail-to-rail input- and output-voltage swing. The first transient, which occurs when the input multiplexer switch closes, has a peak amplitude of 280 mV. The second, smaller transient, which occurs when the sampling switch closes, corresponds to the beginning of the ADC12038's acquisition period. The amplifier's output voltage settles to 1 LSB $1.5 \mu\text{sec}$ after this second transient. The worst-case settling for this amplifier-ADC combination for output voltages from 20 mV to 4.98V is 2 μsec . The settling waveform with a 3V supply looks similar, but the worst-case settling time increases by about 15%.

If an ADC samples an input signal for a period longer than the driving amplifier's worst-case settling time (roughly 2 μsec for the LMC6482/ADC12038 combination), the conversion results will be accurate. However, if the amplifier's output is still recovering from the load transient when the acquisition window closes, the voltage at the converter's input may differ significantly from the real input voltage, and the resulting conversion data will be wrong. Slow-settling amplifiers are unusable in many applications but can sometimes provide reasonable results with slow or low-resolution ADCs.

As in the case of high source resistances, you can improve system accuracy by increasing the ADC's acquisition time. You can do this by slowing the conversion clock. An alternative is to use an ADC or a DAS with adjustable acquisition time.

The ADC12038 (**Fig 3a**) has a signal-acquisition window that is adjustable from 1.2 μsec to 6.8 μsec (when using a 5-MHz clock), which allows for a wide range of amplifier settling times. For the LMC6482 operating at a gain of 10, setting the acquisition time to 2 μsec (10 clock cycles with a 5-MHz clock) provides adequate performance, and a new conversion can begin every 14.8 μsec , resulting in a 67.6-kHz sampling rate. If, instead, you use the ADC12H03, the high-

FIGURE 4

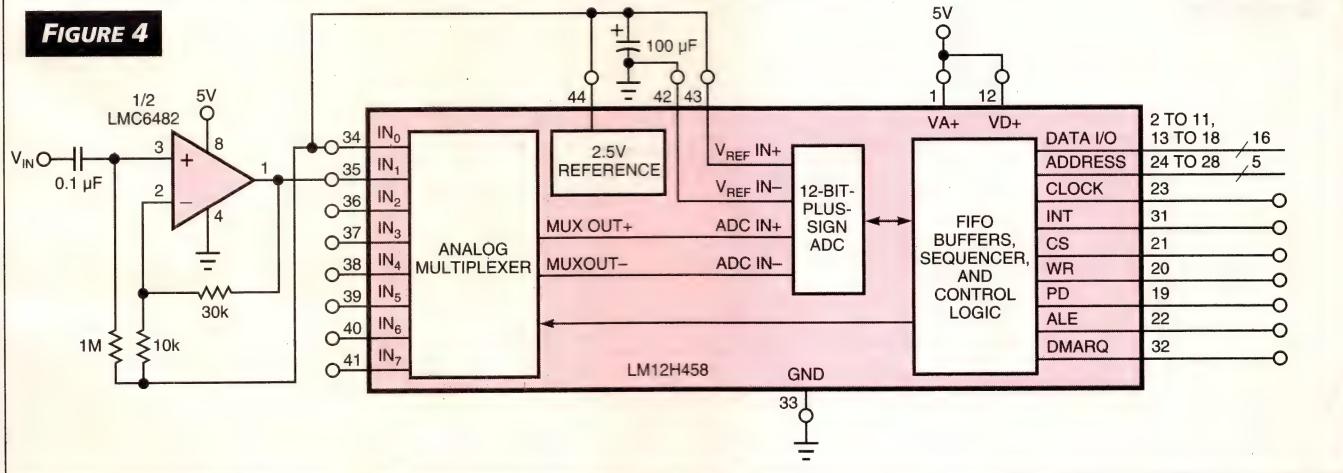

An operational amplifier with rail-to-rail output swing simplifies this amplifier-ADC circuit for digitizing ac signals with 13-bit resolution. Because the amplifier's output can swing to within a few millivolts of V_+ and ground, you can use nearly all of the ADC's input dynamic range. If the amplifier's output swing limited, say, 500 mV from V_+ and ground, you'd need a second reference to avoid losing 2 dB of dynamic range.

LOW-VOLTAGE DATA ACQUISITION

speed version of the ADC12038, the clock rate can increase to 8 MHz, which decreases the conversion time. If you select an 18-cycle acquisition window, the acquisition period will be 2.25 μ sec, and the maximum sampling rate will be 99 kHz. Other ADCs and DAS chips with adjustable acquisition times (the LM12458 and LM12438 families, for example) can take advantage of this technique as well.


Which amplifier should you use? It depends on the speed, resolution, and accuracy you need. Look for amplifiers with gain-bandwidth products in the 1-MHz or greater range for 12-bit data acquisition at conversion rates between 50 and 100 kHz. Low-power, low-speed amplifiers are usually acceptable only if you're sampling slowly and can achieve a long enough acquisition time. The time required for the output to

settle after a load transient is not something you find on most amplifier data sheets; you have to test the amplifier-ADC combination to verify that it works properly in your system.

Do you need rail-to-rail outputs?


The amplifier that precedes the ADC conditions the input signal; it may buffer a high source impedance, provide gain or level shifting, or alter the transfer function in some non-linear way to compensate for sensor characteristics. In a ± 15 V system, an amplifier whose output can swing to within a couple of volts of the supply rails may be perfectly adequate, but in a 3 or 5V system, the amplifier must swing much closer to the supplies. Do you need rail-to-rail output swing? Not always, but it's helpful in many applications.

FIGURE 5

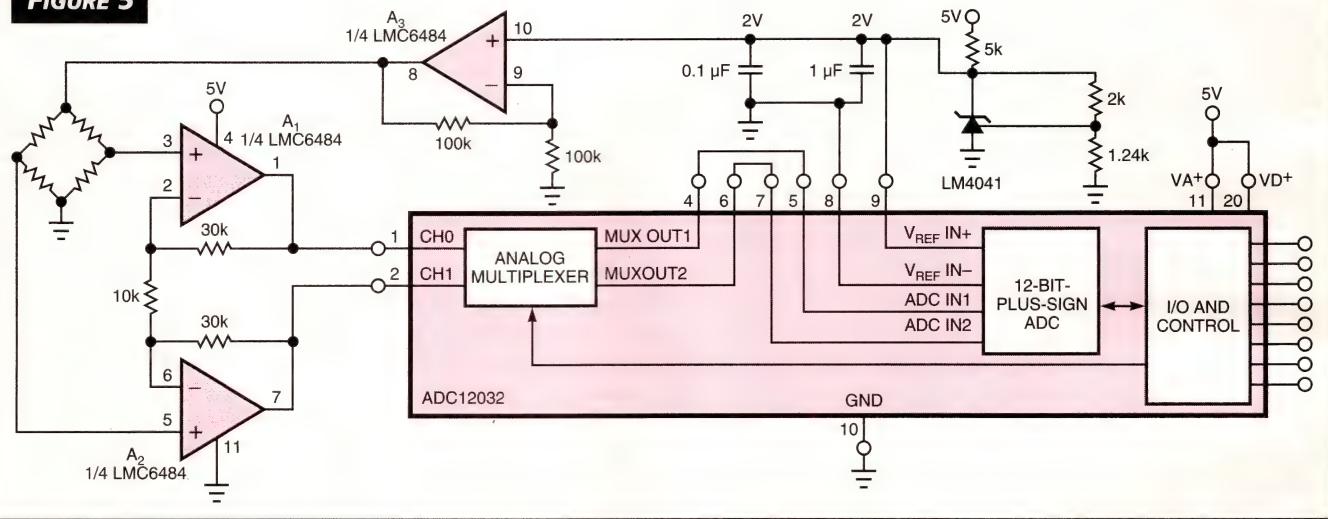

In this circuit, low-voltage amplifiers A₁ and A₂ provide differential gain to the output of a load cell and differential drive to an ADC's differential inputs. A₃ doubles the 2V ADC reference to provide bias for the bridge.

FIGURE 6

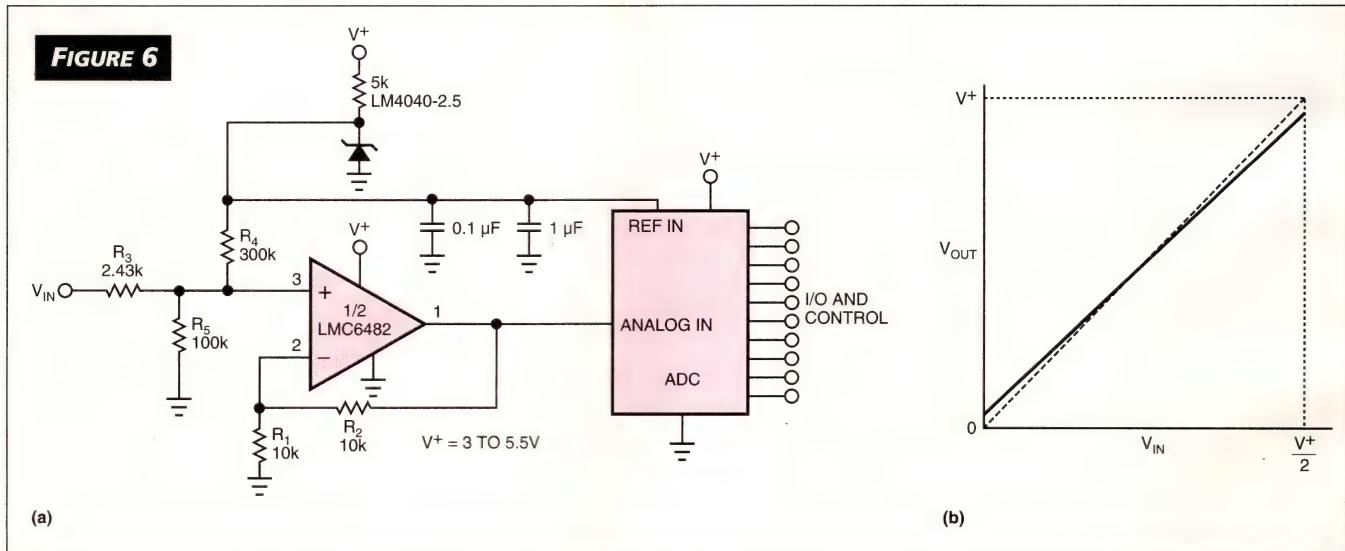

When you can't afford to lose very-near-ground signals to offset and swing limitations, you can add some offset to the input signal (a). R₃, R₄, and R₅ reduce the ADC's nominal input range but increase the usable input range because they also reduce the range of signals applied to the amplifier input (b).

Fig 4 shows a simple amplifier circuit that provides gain or an ac signal at sampling rates up to 140 kHz. You can set the dc voltage at the amplifier's output to a convenient voltage near the half-supply point; in this 5V circuit, the output is biased at the 2.5V reference voltage. The circuit takes advantage of the DAS chip's differential inputs and sign bit to achieve 13-bit resolution. IN₀ and IN₁ are a differential input pair; IN₀ is connected to V_{REF}=2.5V. Input signals that swing above 2.5V have a positive sign bit; those below 2.5V have a negative sign bit. If the amplifier can swing to within 25 mV of ground and V+, you can use 99% of the ADC's full-scale input range. Using an amplifier whose output stage limits at, say, 500 mV, will lose 20% of the full-scale range and reduce the S/N ratio by about 2 dB unless you reduce the amplifier's gain and develop a second, lower reference voltage to drive the ADC's reference input pin.

In **Fig 5**, the output from a load cell drives a pair of amplifiers that differentially amplify the cell voltage. The differential output voltage from A₁ and A₂ drives the ADC's differential inputs. The reference voltage can match to the amplifiers' output swing. Because the LMC6484 amplifier can swing within a few millivolts of the supplies, a 2V reference works well. A₃ doubles the ADC's reference voltage to provide bridge bias. As in the ac-amplifier example, arriving at a practical design is easier if the amplifiers can swing very close to the supply rails, but it's not critical that they do so.

Living on the edge

Limited output swing causes more trouble when you need to work with input signals near ground. For example, a non-inverting amplifier with a gain of 10 can take a 0- to 250-mV input signal up to 0 to 2.5V at the ADC's input. Virtually all low-voltage ADCs accept input voltages anywhere within the

ADCs' supply rails, so a 3 or 5V ADC can easily handle a 0 to 2.5V input range.

Unfortunately, single-supply amplifiers can't produce usable signals closer to the supply rails than a few millivolts. If you need to digitize signals very near ground at 12 bits of resolution, your amplifier may not be up to the task. (The first code transition for a 12-bit ADC with a 0 to 4.096V range is at 0.5 mV.) In addition, if the amplifier's offset voltage is negative, you will be throwing away input signals that are too small to overcome the offset-voltage and output-swing limits.


Fig 6 shows a simple way to recover input range lost to amplifier offset and output-swing limits. Resistors R₃, R₄, and R₅ shift the amplifier's output range up by 20 mV. Even when the input signal is at ground, the amplifier's output exceeds the output stage's limit voltage and is linearly related to the input.

Handling bipolar input signals

The ADCs discussed here have unipolar supplies and input ranges, but input voltages aren't always unipolar. Although it is uncommon to generate any negative or bipolar signals in a system that operates from a single positive supply, you may occasionally need to accept negative or bipolar signals generated outside your system.

Fig 7 shows the simplest way to deal with these signals: A pair of equal-valued resistors is connected to V_{REF}, the amplifier's input, and the signal source. This circuit converts an input signal whose range is $\pm V_{REF}$ into an output with a range of ground to $+V_{REF}$; the network shifts the input voltage and divides the input signal by two. Input signals near ground shift up to $V_{REF}/2$, so they are always within the ADC's input voltage range. In this 3.3V system, the input voltage swing is $\pm 2.5V$. In a 5V system, the reference

FIGURE 7

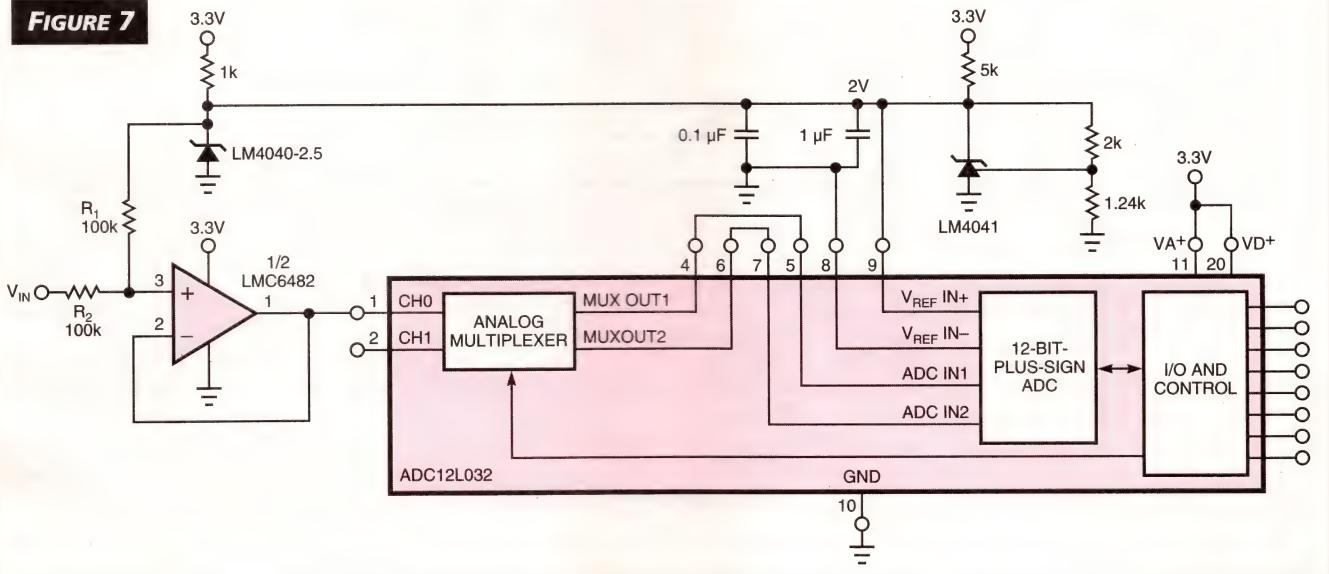

A pair of resistors at the amplifier's input transforms a bipolar input signal into a unipolar one that can drive a single-supply ADC. The analog-input range is now $-V_{REF}$ to $+V_{REF}$. You can make this circuit work on a 5V supply if you substitute an ADC12032 for the ADC12L032. With a 5V supply, you can extend the input voltage swing to $\pm 4.096V$ simply by using a 4.096V reference.

LOW-VOLTAGE DATA ACQUISITION

voltage might be 4.096V, resulting in a $\pm 4.096V$ input swing.

If you're interested in accurately converting input signals that reach all the way to $-V_{REF}$, you run into output-swing and input-offset-voltage-swing limitations. You can deal with these by slightly altering the resistor ratio or reference voltage to keep the minimum worst-case input voltage above the amplifier's limit voltage. Most of the time, an amplifier's input voltage should range from ground to $+V_{REF}$. But having an input common-mode range that extends to ground isn't necessary if you aren't interested in input signals that extend all the way to $-V_{REF}$.

In most applications, the resistors should be relatively large so that they won't attenuate your signal source; something in the 10- to 100-k Ω range is typical for R_1 and R_2 . The op amp buffers the high source impedance to eliminate the effect of source impedance on acquisition time. An op amp with extremely low input bias current is best for this application. The LMC6482 is used here because of its extremely low input bias current and rail-to-rail input and output-voltage swings.

Remember that the matching of the resistors affects the accuracy of the overall circuit. When precision is critical, you'll need precision resistor arrays (available from Beckman, Caddock, and Allen Bradley), with two or more matched devices (0.01 to 0.05% matching and better than 15-ppm temperature tracking) in a single package.

System calibration

Whenever you perform analog signal processing ahead of your ADC, your signal-processing circuits can degrade the

accuracy of your system. Amplifier offsets, reference errors and resistor tolerances can cause offset and gain errors in the output data. This is true in many systems but is especially true in low-voltage systems because amplifiers that work in those systems are rarely precision devices. In some systems a small amount of gain or offset error is inconsequential, but when the error budget is tight, you may need to perform some sort of calibration or error correction on the system.

Fig 8 provides an example of the concept of system-calibration. The circuit uses a simple but effective offset-calibration scheme. R_3 , R_4 , and R_s provide offset shift. With typical op amps and resistors, several tens of millivolts of offset error can be present, and the precision with which R_3 , R_4 , and R_s can be matched also affects the gain. The DAS chip's input multiplexer helps to perform calibration.

The calibration sequence begins by enabling the connection between IN_3 (ground) and $MUXOUT+$ and performing a conversion. This zero-scale calibration reading is called D_z . Next, the connection between IN_0 , (V_{REF}), and $MUXOUT+$ is enabled to get full-scale reading, D_F . D_F and D_z can now be used to correct subsequent conversion results. Whenever a conversion is performed, the result, D_M (measured data), is adjusted to obtain the real input voltage within the resolution and accuracy limitations of the ADC:

$$V_{IN} = V_{REF} (D_M - D_z) / (D_F - D_z)$$

Switch on-resistance has a strong effect on the performance of this circuit. If the on-resistance mismatch is to affect the correction accuracy by less than 1 LSB, any mismatch between the analog switches' on-resistance should be less than $(R_4 || R_s) / 2^{n-1}$, where n is the converter's resolution in


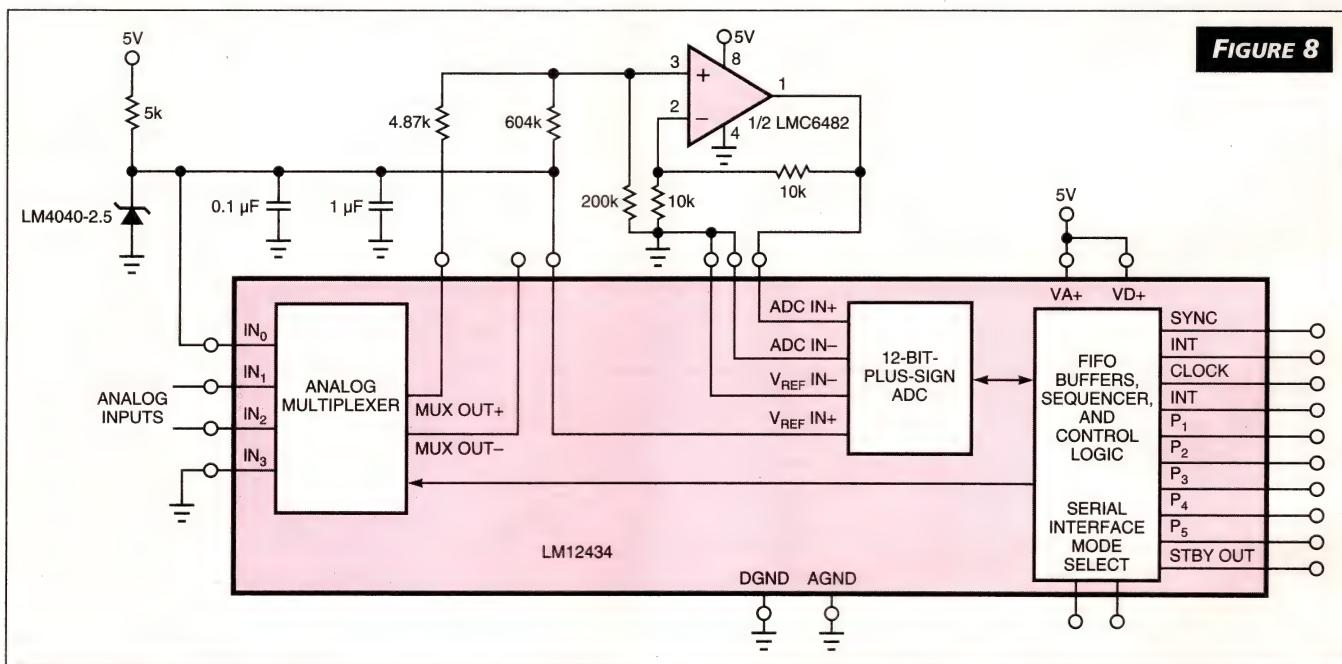


FIGURE 8

Using an external multiplexer or the multiplexer switches in an ADC or DAS, you can measure the amplifier circuit's offset and full-scale errors and use them to correct subsequent readings. This circuit uses a 4-channel DAS chip. The circuit uses two of the input channels for calibration; the other two serve as the analog inputs. You can operate the circuit from a 3V supply by replacing the LM12434 with an LM12L434.


VIEWLOGIC PRO SERIES™

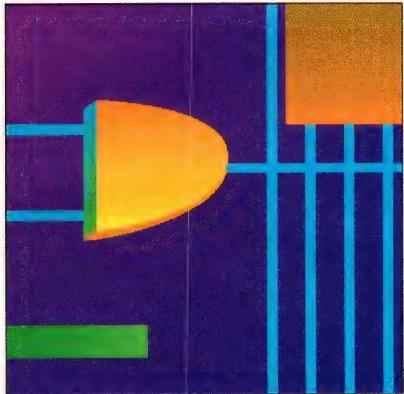The world's most powerful
Windows-based design tools
starting from
\$1,995




PROcapture™

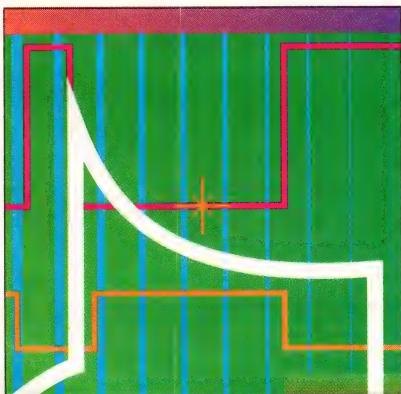EDN Reader's Choice Survey rated Viewlogic tools as the best schematic entry solution. **\$1,995**




PROanalog™

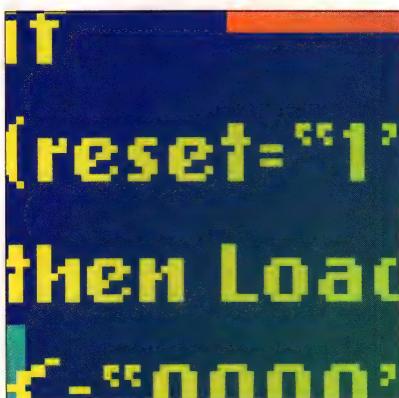Windows-based analog design and SPICE simulation. **From \$2,995**




PROvhdl™/PROsynthesis™

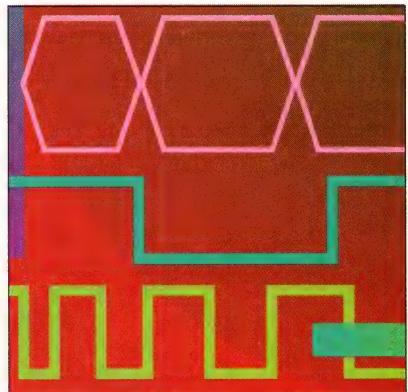VHDL, simulation and synthesis for FPGA and CPLD design. **From \$1,995**



PROsim™

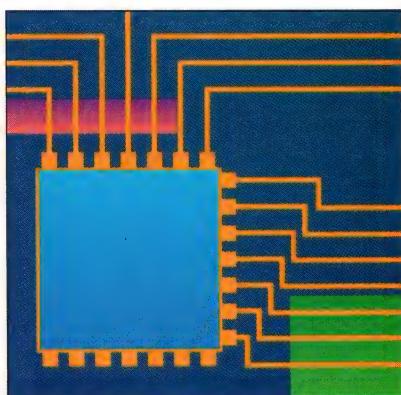28-state, high-performance timing simulation. **\$4,995**



PROdeveloper™/PROchip™

For complete PLD, FPGA and systems design including design entry, verification and place and route. **From \$9,995**

VIEWlogic

PROSeries

CALL 1-800-USE-VIEW NOW FOR A FREE DEMO DISK

© 1993 Viewlogic Systems, Inc. All trademarks and registered trademarks are the property of their respective owners.

CIRCLE NO. 96

EDN September 29, 1994 • 95

LOW-VOLTAGE DATA ACQUISITION

bits. For a typical 12-bit ADC, the on-resistance of the internal multiplexer switches might be on the order of 1.5 k Ω max. If the switches match to within 5% (75 Ω), $R_4||R_5$ must be at least 150 k Ω , which might result in a value for R_3 on the order of 3 to 5 k Ω . When lower on-resistances are necessary, you can use an external multiplexer with lower R_{ON} .

You can modify the circuit of **Fig 8** for 3V operation simply by replacing the LM12434 serial DAS chip with its low-voltage version, the LM12L434. The technique is not restricted to DAS chips; it works with any multichannel ADC with MUXOUT and ADCIN pins.

When do you need input protection?

When a data-acquisition circuit's supply voltage is only 5 or 3V, you have abundant opportunities to overdrive the ADC's inputs. The lower the power-supply voltage, the more likely it is that a signal greater than the supply voltage will inadvertently drive the device.

When the analog input signal applied to a CMOS ADC exceeds the power-supply voltage, incorrect conversions, latch-up, or even permanent damage can result. Most ADCs

begin to run into trouble with overdrive voltages of just a few hundred millivolts, while others can withstand several volts of overdrive.

When the ADC's analog inputs connect to the outside world, almost any input voltage can appear. One solution is to add clamp diodes to the circuit (**Fig 9a**). R_2 , which limits the current into the IC, can be as small as 100 to 200 Ω because the clamp diodes turn on at a voltage very close to the ESD-protection diodes' turn-on voltages (assuming the clamp diodes are silicon devices). R_1 , which limits the clamp-diode current, depends on the maximum current rating of the clamp diode and the maximum expected overdrive voltage. For example, if the maximum possible input overdrive is 50V, a 500 Ω R_1 limits the external clamp-diode current to less than 100 mA. This value is compatible with most CMOS ADC input stages and doesn't slow the charging of the sampling capacitor enough to affect conversion accuracy.

If your system includes amplifiers or other components to condition analog signals ahead of the ADC (and this is probably the case), you can often use these devices to protect the ADC's inputs. For example, a 5V CMOS operational amplifier can operate from the same 5V or supply as the ADC and, therefore, can't overdrive the ADC. The problem now becomes protecting the op amp from damage due to large input signals. Unlike a current-limit resistor at the input to the ADC, however, a resistor at the op amp's input pin doesn't affect conversion accuracy as long as the amplifier's input bias current is low. In fact, a CMOS op amp like the one in **Fig 9b** has virtually no input bias current (40 fA), so the primary error source is high-frequency roll-off due to the current-limit resistor and the input capacitance.

With a 10-k Ω input-protection resistor as in **Fig 9b**, the upper cutoff frequency is typically on the order of 8 MHz, which is much greater than the gain-bandwidth product of the amplifier. If you convert from bipolar to unipolar signals as in **Fig 7**, the level-shifting resistors protect the amplifier from overdrives, and additional resistors are unnecessary.


Some recent ADCs include built-in protection for overdrive voltages well in excess of the supply voltage. The ADC12038 in the circuit of **Fig 3** and the LM12434 in **Fig 8**, for example, can handle overdrives at least 5V beyond the supply voltage. Therefore, for limited overdrives, they need no protection at all.

When powering-down equals blowing up


If a system is designed for low power dissipation, chances are good that it operates from a 3 to 5V supply. It's also likely that the system uses some form of power management. A common approach to reducing power dissipation involves shutting down sections of the system that are not in use at a given time.

A simple technique is to shut off the power supply to the unneeded circuits. You can accomplish this conveniently using a voltage regulator with a shutdown logic input. When a system does not need the analog circuits, the microcontroller shuts them down via the voltage regula-

FIGURE 9

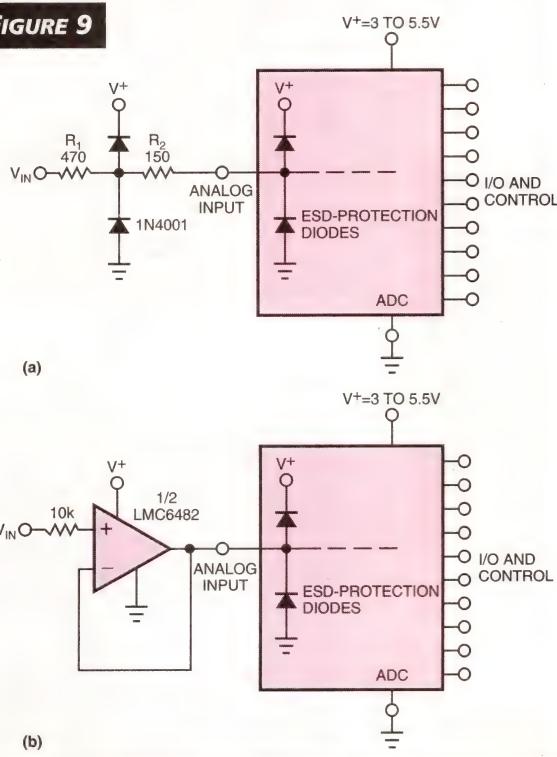

By using clamp diodes (a), relatively small resistors protect an ADC's input from large overdrives and avoid the long acquisition times often needed with high-value protection resistors. In (b), an amplifier makes an excellent protection device. Because it operates from the same 3V supply as the ADC, the amplifier can't overdrive the ADC's logic input. If its input bias current is low, the amplifier's input resistor doesn't add any dc errors. Watch out for noise, though; if the resistor is too large, its thermal noise will be significant at high gains.

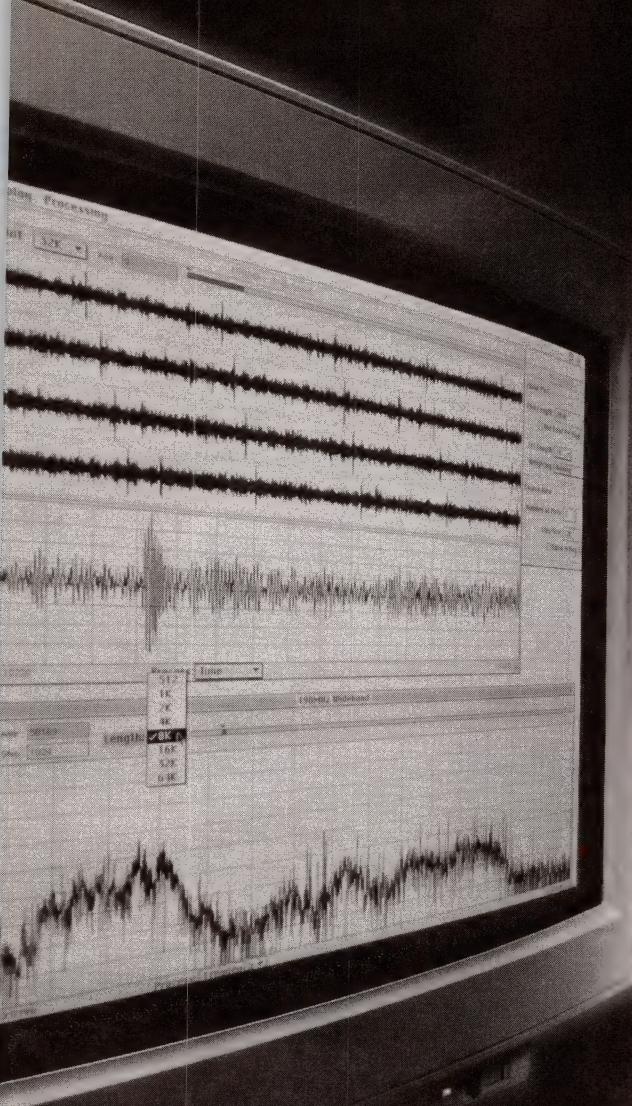

Proof?



Positive!

Why fret over development test? Think positive. Prove your results beyond the shadow of a doubt with the TRW VP8000 Wideband Signal and Test System.

The key is deep memory. The TRW VP8000 has up to 64 megabytes of it. With 500 Msample/sec capture and generation in both analog and digital. That's a 200MHz instantaneous bandwidth to soak up more real-world

signal. In more detail. In less time. With less retesting. This assures that you catch problems in the lab. Not in production.

The TRW VP8000 proves to be a positive in other ways, too. A single workstation-based system, it replaces stacks of test and measurement devices. Integrating the accessibility of computers with the power of instrumentation. Delivering fast test set-up... a smooth

upgrade path... portability... and affordability. So, don't just prove results the usual way – improve. Give us a call at

1-800-354-6195.


And let us prove how the TRW VP8000 will erase all your doubts about development test.

The TRW VP8000 – there's no doubt about it.



LOW-VOLTAGE DATA ACQUISITION

FIGURE 10

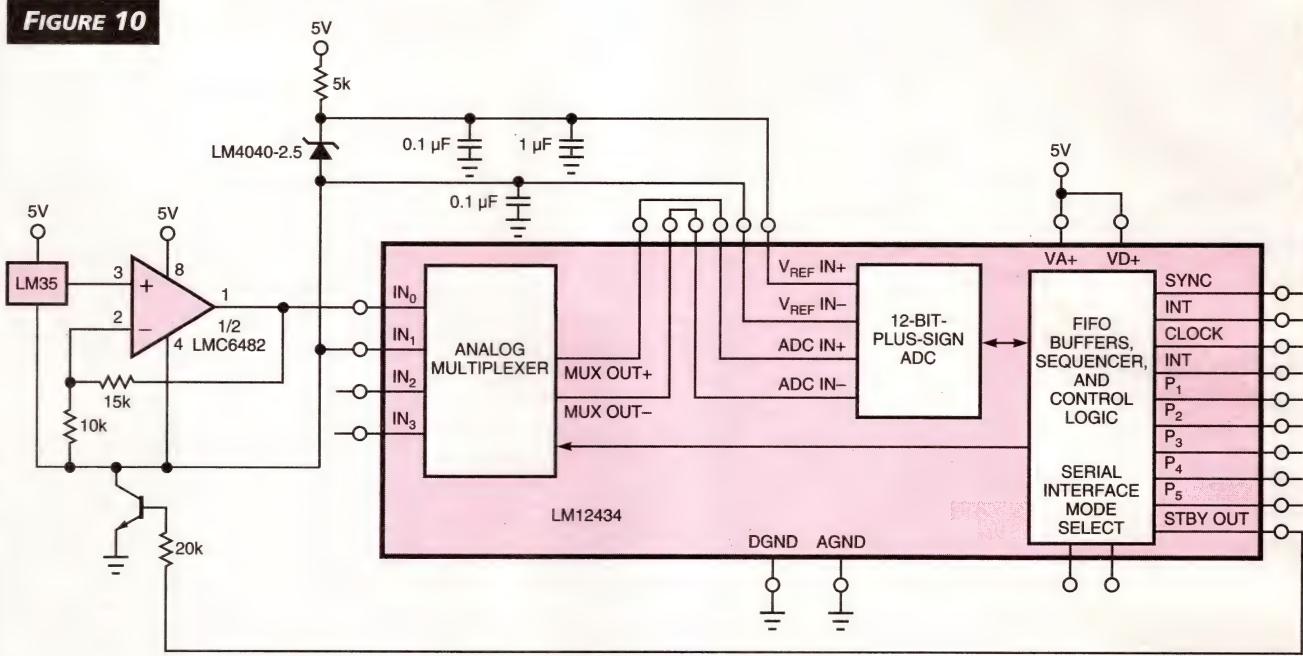

When you can shut down your ADC or DAS, you can reduce power drain between conversions without running the risk of overdrive by logic signals. In this temperature monitor, for example, when the DAS chip goes into shutdown mode, it also shuts down the temperature sensor, amplifier, and reference via its standby output pin and an external npn transistor. When you shut down the circuit, you reduce its power dissipation to only 50 mW.

tor's shutdown pin. The drawback to this approach is that the digital parts of the system are still active. If one of the ADC's digital input lines is pulled high by a digital circuit that remains powered up, that input can be damaged, or the IC may latch up because the logic signal exceeds V_+ , which is 0V when the power supply is shut down. In some systems, it is a simple matter to keep the digital circuitry from driving the ADC while its supply voltage is off, but this is not practical in every system, especially if the ADC connects to a bus.

Because of this problem and because shutting down a voltage regulator often requires additional components and circuit-board area, several recent ADCs include power-down functions on-chip. Either driving a shutdown pin to a specified logic level or issuing a software command through the ADC's I/O forces the ADC into a low-power state with its supply voltage still applied. Since the supply voltage is present, digital circuitry operating from the same supply can't overdrive the ADC during shutdown. An example appears in **Fig 10**. In this 0 to 100°C temperature monitor, the µP directly shuts down the LM12434 serial DAS chip. The npn transistor, which is driven by the DAS chip's standby output pin (STBY), shuts off the temperature sensor, amplifier, and 2.5V bandgap reference. The circuit, therefore, requires no additional lines from the microcontroller other than those that control the DAS.

When active, the DAS-amplifier-sensor-reference subsystem dissipates less than 43 mW. When shut down, the sub-

system dissipates about 50 µW. When the circuit is active, the differential inputs on the DAS look at the amplifier output and reference with respect to the npn transistor's collector, thus eliminating any errors caused by the transistor's saturation voltage. By simply shutting off the converter and other analog components between conversions, you can achieve very low power dissipation, even with a relatively fast, high-performance converter. **EDN**

Author's biography



Kerry Lacanette is data-acquisition applications manager at National Semiconductor Corp in Santa Clara, CA, where he has worked for 16 years. Lacanette is responsible for defining data-acquisition products and designing circuits that use data-acquisition ICs. He holds BSEE and MSEE degrees from the University of California, Santa Barbara, and is a member of the Audio Engineering Society.

VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest
589

Medium Interest
590

Low Interest
591

INTERFACE & SUPERVISORY



RS-232 TRANSCEIVER CONSUMES 75% LESS POWER

The new 5-V ADM202 two-channel RS-232 transceiver consumes only 4 mA max I_{DD} , 75% lower than its nearest competitor. It operates on a single 5-V supply, works with 0.1 μ F capacitors, and is ideal for battery-powered and other power-sensitive applications.

The ADM202 is also suitable for high data rate applications. It drives 120 kbps into 1-nF loads, allowing users to transfer files over long cable lengths at maximum speed. It is available in 16-pin DIP, and both wide and narrow SOIC packages. The ADM202 is pin compatible with industry standard 232 devices. Prices begin at a low \$1.20.[†]

ADM202 KEY FEATURES

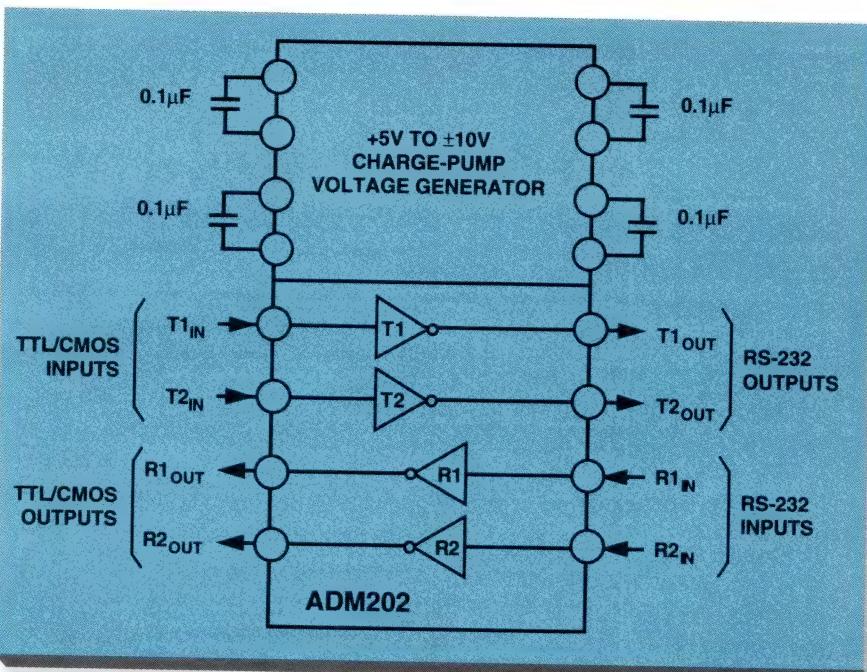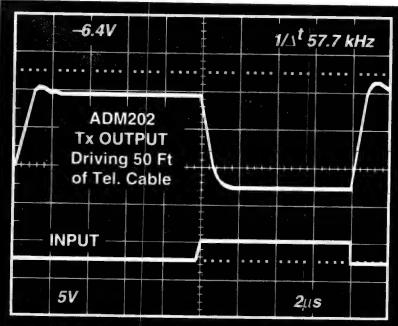- 4 mA max I_{DD}
- Operates on single 5-V supply
- Industry standard pinout



OCTAL LINE DRIVERS/RECEIVERS OFFER SUBSTANTIAL POWER SAVINGS



The ADM5170 and ADM5180 are complementary octal RS-232/422/423 line drivers and receivers that require substantially less power than other solutions. The ADM5170 octal line driver requires only 2 mA disabled and 25 mA enabled. The ADM5180 octal line receiver requires a supply current of only 3.5 mA, one-seventh that of its nearest competitor.

Both are available in space saving 28-lead PLCC packages, with prices starting at \$2.72.

ADM5170/5180 KEY FEATURES

- Low power consumption
- Octal drivers/receivers
- 28-lead PLCC package

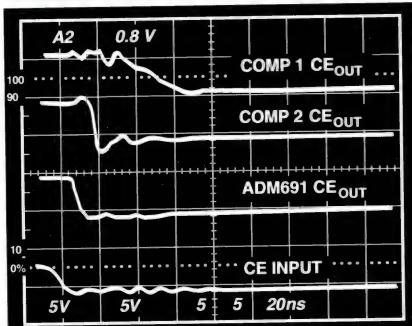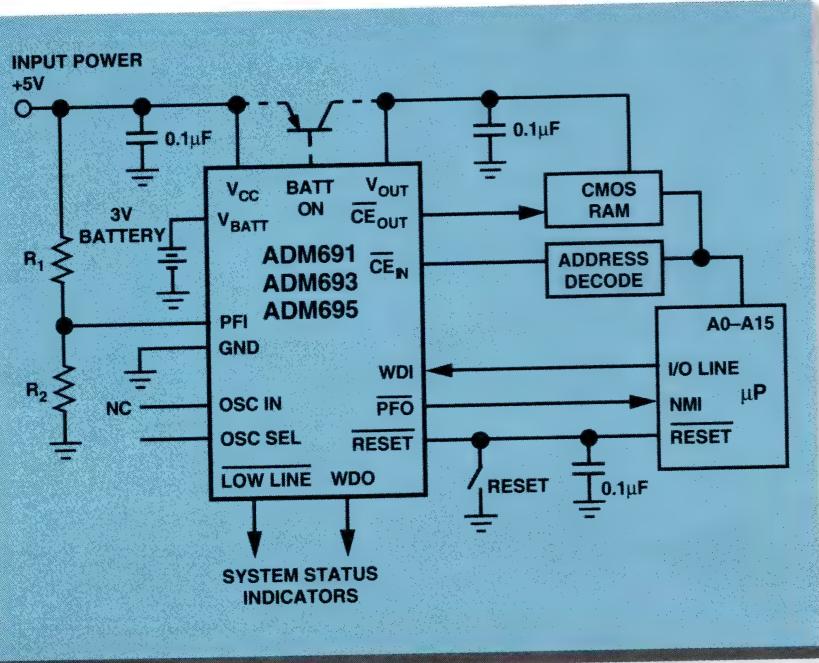[†] All prices shown in USD, in 1,000s, recommended resale, FOB USA.



ADM691 KEY FEATURES

- 9 ns max prop delay
- Less than 2 mA max I_{DD}
- Switches battery currents up to 100 mA

LOW COST 5-V RS-232 CONSUMES ONLY 4 mA MAX

The ADM232L runs at 120 kbps, and combines low power – 4 mA max – with low cost – just \$1.20. The ADM23xL family of RS-232 transceivers offer the best cost/power ratio in the industry, and are latch-up free. These low-cost, low-power devices are ideal for your volume requirements.

ADM232L KEY FEATURES


- 4 mA max I_{DD}
- Latch-up free
- Low cost

MICROPROCESSOR SUPERVISOR BREAKS THE 10 ns CHIP ENABLE PROP DELAY BARRIER

The ADM691 microprocessor supervisor has a prop delay of just 9 ns max over the full industrial (-40 to +85°C) temperature range. It is the first to break the 10 ns barrier, an important consideration where RAM needs to be disabled quickly after a power failure has been detected.

The ADM691 is able to switch battery currents of up to 100 mA and generate a valid reset 120 ns after a fault condition. Yet, it consumes less than 2 mA max I_{DD}.

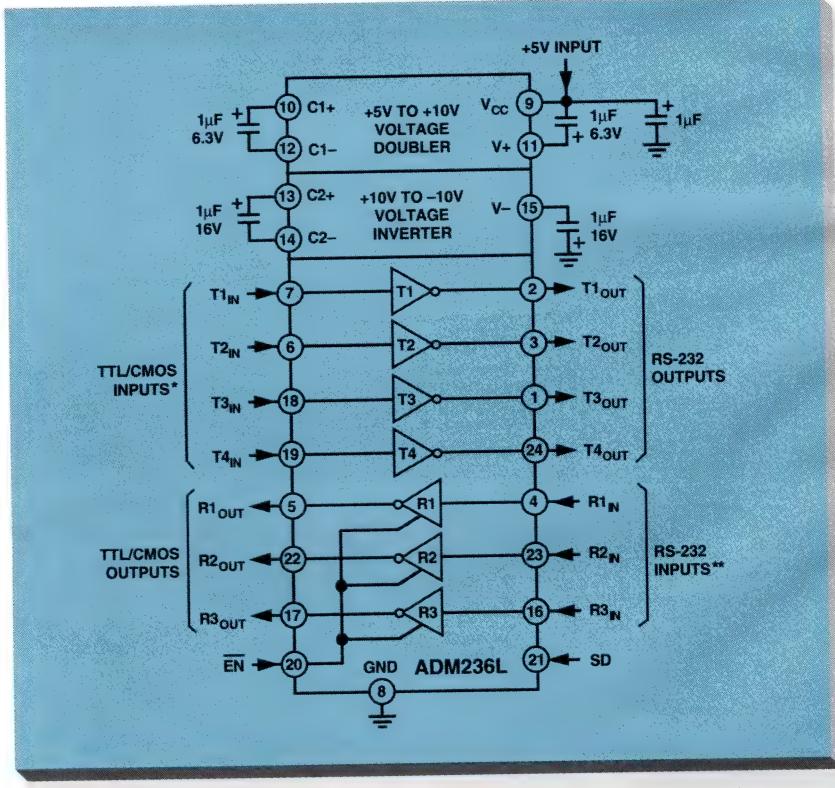Analog Devices can meet all your power management needs with the ADM69x family of microprocessor supervisors. In addition to the ADM691, it includes devices with reset generation, battery steering, power fail warning and watchdog timer functions. Pricing for the ADM691 begins at \$2.60.




FOR DATA SHEETS OR SAMPLES

HIGH DATA RATE/LOW SKEW RS-485 CONSUMES ONLY 2.2 mA

For applications that require high speed and low skew, but with minimal supply current, investigate the ADM485 and ADM1485 from Analog Devices.

The ADM485 is a 5 Mbps, 2.2 mA single RS-485 transceiver in an 8-pin package. The ADM1485 blazes along at 30 Mbps, and still requires a miserly 2.2 mA. Both have typical 0 ns driver output-to-output bar skew, so you may relax your "skew budget" for cables and other devices.

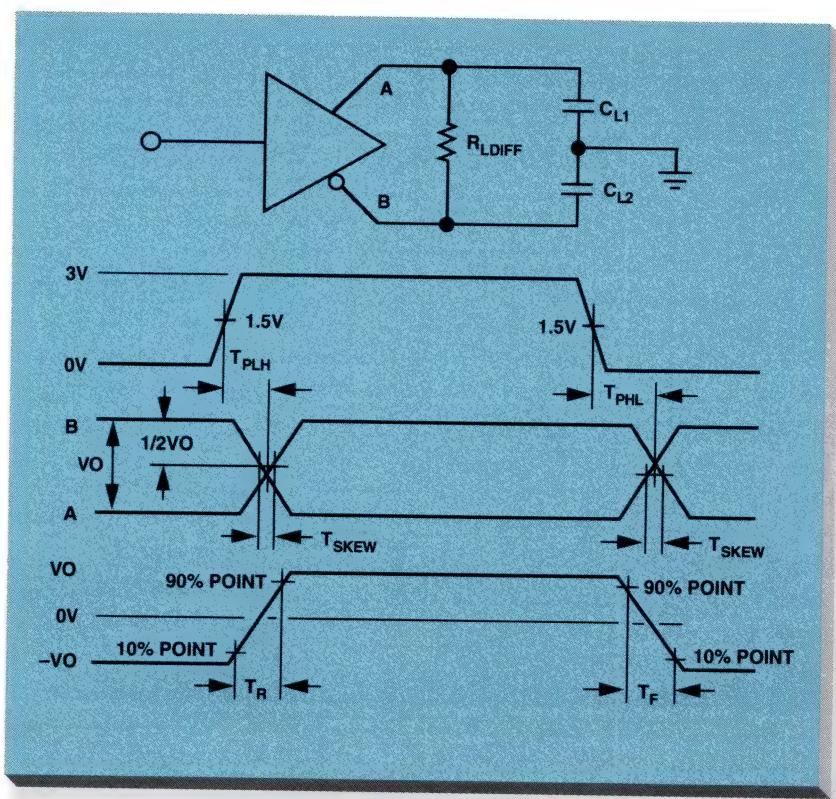Pricing begins at \$1.24 for the ADM485, and \$1.55 for the ADM1485.



ADM1485 KEY FEATURES

- 30 Mbps
- 2.2 mA max
- Zero output-to-output bar skew

3.3-V NOTEBOOK PC SERIAL PORT DRIVES 100 FEET CABLE WITH FULL RS-232 LEVELS AT 116 kbps


The new ADM560/1 complete serial port transceivers consume only 1.5 mA typical, but are capable of driving serial port mice and supporting 116 kbps data rates on 100 foot cables at 3.3 V.

The ADM560/1 feature maximum data rates of 230 kbps. Their digital inputs may be driven up to 5 V with a 3.3-V supply, allowing use in split-supply systems.

The ADM560/1 are pin compatible with xxx241, and are available in SSOP packages. Prices start at \$2.10.

ADM560/1 KEY FEATURES

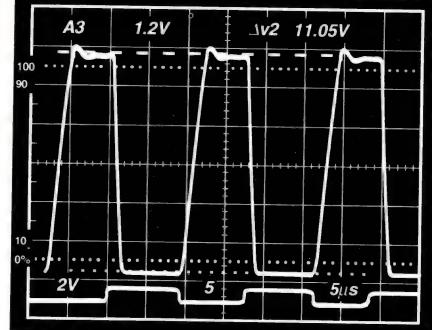- 1.5 mA I_{CC} typical
- 230 kbps max data rate
- Drives serial port mice



Signal measured at receiver input when ADM560/1 used to drive 100 feet of RS-232 cabling at 116 kbps. Fully meets RS-232 levels while providing clean waveforms to ensure error-free communications.

LINEAR REGULATOR PROVIDES 3-V, 5-V AND VARIABLE VOLTAGE AT 100 mA

Analog Devices' new linear regulators, the ADM663A and ADM666A, feature the patented Tri-Mode system. This system allows you to select a pre-trimmed 3.3-V, 5-V or adjustable output voltage. Additionally, the regulators provide 100

mA current, thermal shutdown, ultralow power shutdown of 6 µA (typical) and many other industry-leading features.


The ADM663A and ADM666A are ideally suited for applications requiring, for example, 9 V to 5 V or 5 V to 3.3 V at up to 100 mA with shutdown – using no external components and providing 5% accuracy.

Now you can achieve 3.3 V or 5 V with power fail warnings, shutdown, programmable current and other capabilities using only the tiny 8-pin SOIC package of the ADM663A/666A and a single 0805 body stability capacitor.

Pricing begins at \$1.40 for the ADM663A, and \$1.65 for the ADM666A.

ADM663/6A KEY FEATURES

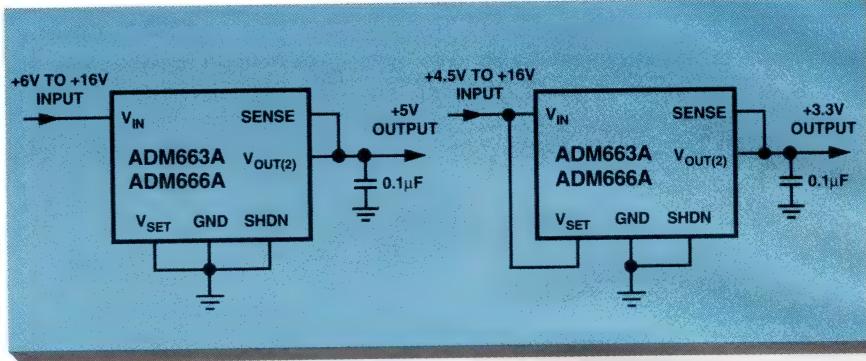- Pre-trimmed 3.3-V, 5-V or adjustable output voltage at 100 mA
- Low power shutdown of 6 µA (typical)
- 8-pin SOIC package



CHOOSE HIGHEST PRECISION/LOWEST NOISE OR LOWEST POWER WITH ANALOG DEVICES' REFERENCES

Whether you need the industry's highest precision/lowest noise 2.5-V voltage reference, or the lowest power 2.5-V or 5.0-V voltage references, Analog Devices can meet your requirements.

Analog Devices' AD780 is the highest precision 2.5-V voltage reference available, and can also provide 3.0-V output while maintaining industry standard pinout. It has a temperature coefficient of 3 ppm/°C, and initial accuracy of 1 mV over the entire industrial temperature range. The AD780 offers the lowest noise, 100 nV/√Hz, in its category. It also offers the lowest price, beginning at \$3.30, of any high precision, low

noise reference. The AD780 is available in various package options, including both surface mount and through-hole.

The REF192 and REF195 are the first two members of our new micro-power precision voltage reference family. For portable or battery-powered applications, these references feature a low quiescent current of 45 µA (max), and 15 µA in sleep mode. The REF192 and REF195 provide 2.5-V and 5.0-V outputs, respectively, with initial accuracy of ±2 mV and temperature coefficient of ±5 ppm/°C.

The REF195 also features a low dropout voltage of 100 mV with a 1 mA load. Maximum load current is 30 mA for both references, allowing dual use as micropower regulators. Future micropower reference products will cover your complete reference needs

for 3-V and 5-V systems. The REF19x reference pricing starts at a low \$1.94.

AD780 KEY FEATURES

- Temperature coefficient of 3 ppm/°C
- Initial accuracy of 1 mV
- Noise 100 nV/√Hz

REF192/195 KEY FEATURES


- Low quiescent current of 45 µA max, 15 µA in sleep mode.
- Low dropout voltage of 100 mV with a 1 mA load
- Pricing starts at a low \$1.94.



WORLDWIDE HEADQUARTERS

Analog Devices, Inc.
One Technology Way
P.O. Box 9106
Norwood, MA 02062-9106
Tel: (800) 262-5643
Fax: (617) 326-8703

Deadline Extended To
October 30, 1994

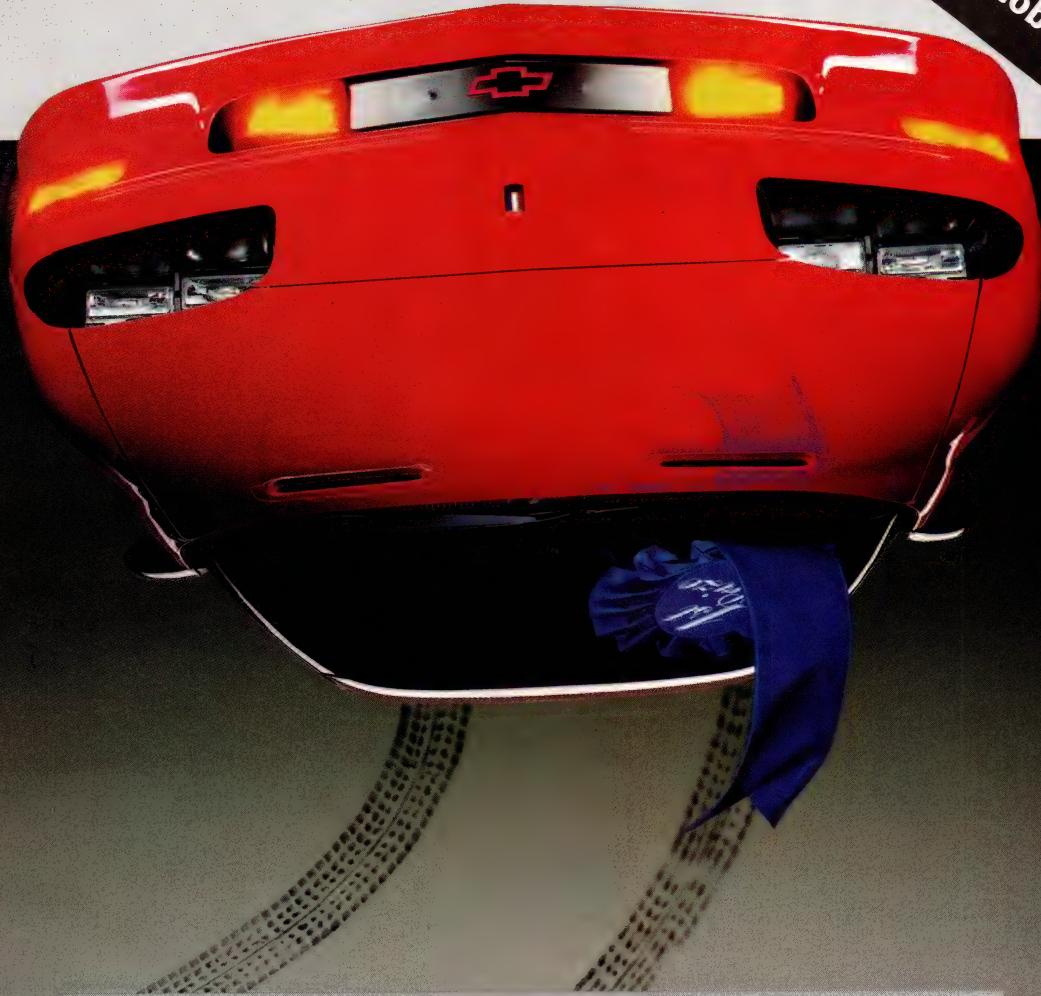

A DESIGN CONTEST FOR ENGINEERS WHO SEE THINGS DIFFERENTLY.

If conventional thinking drives you up the wall, order the Philips DS-750 development tool kit.

It helps you dream up great designs using our 8-bit 8XC750 microcontroller. Including the design that could win you a hot new Camaro!

For the low price of just \$4750 (plus shipping), the Philips DS-750 gives you all the hardware, software and documentation needed to quickly build, emulate and debug 8-bit designs using our 8XC750.

The 8XC750 is our powerful, low-cost entry into the full family of Philips 80C51 microcontrollers.



© Philips Electronics North America Corporation, 1994

Together, they give you winning designs.

Which is why you should be sure to enter the exciting Philips Dream Machine 8XC750 DESIGN CONTEST. Just submit a design to us using the 8XC750 or any Philips 80C51 microcontroller derivatives by September 30, 1994. If it turns our judges on their heads, you could win the Camaro or a color or monochrome laptop computer.

So turn it up. Use your credit card to order the DS-750 today. We'll also send you more information on this incredible design contest:

I-800-447-1500, ext. 1120 DN



Co-sponsored by EDN

Philips
Semiconductors



PHILIPS

EPSON

The Crystalmaster

Founder of the crystal-timing era and master of the latest crystal technology, Epson has the broadest lines available for Crystals, Crystal Oscillators, and Real Time Clocks.



CRYSTALS

More Epson Crystals to choose from

THRU HOLE

C-2

Low frequency tuning fork type
32.768 KHz
20 to 165 KHz

CA-301

AT-Strip High frequency type
4.0 to 64.0 MHz

SMD

MC-405/6

has heat resistive C-2H crystal
L10.4xW4.06xH3.56mm
20 to 165 KHz

MA-406 and MA-505/6

have heat resistive CA-303
crystal
4.0 to 64.0 MHz

MINI-SMD

MC-306

utilizes new advanced EPSON
tuning fork technology
L7.9xW3.8xH2.5mm
32.768 KHz

MA-306

employs new AT-strip
technology
L7.9xW3.8xH2.5mm
17.7 to 40.0 MHz



OSCILLATORS

*Latest technology Epson
Crystal Oscillators*

THRU HOLE

SG-51

Full Size



SG-531

Half Size

Auto-insertable
Frequency range 1.025 to
67.0 MHz

SMD

SG-615

has internal heat resistive CA-303
crystal
L14.0xW9.8xH4.7mm
1.025 to 67.0 MHz



MINI-SMD

SG-636

utilizes new advanced EPSON
AT-strip technology
L10.3xW5.8xH2.8mm
2.20 to 67.0 MHz



**Request your copy of the
Crystalmaster Catalog today!**

EPSON® EPSON AMERICA, INC.
COMPONENT SALES DEPARTMENT
TEL: (310) 787-6300, FAX: (310) 782-5320

REAL TIME CLOCKS

*Epson Real Time Clocks...
built-in Crystal for every
application*

*DIP and SOP Type RTC's... Second-to-year
and day-of-the-week*

RTC-4553 Serial data bus, miniature
package, user SRAM (30 x 4 bit).

RTC-58321/3 4 bit parallel bus, I/O
connection.

RTC-62421/3 4 bit parallel bus, low
standby current consumption.

RTC-72421/3 4 bit parallel bus, low
standby current consumption.


RTC-63421/3 4 bit parallel bus, alarm
function.

RTC-64611 8 bit parallel bus, alarm
function.

RTC-65271 8 bit parallel bus, 4K bytes
SRAM, battery holder.

RTC-658X 8 bit parallel bus, 114 bytes
SRAM, battery holder.

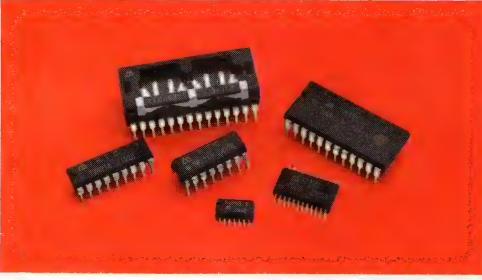RTC-659X 8 bit parallel bus, 114 bytes
SRAM, alarm, battery holder.



EPSON Sales Representatives: AL-GA-TN Concord Components 205/772-8883 • AZ-NM Fred Board Assoc. 602/994-9339 • CA-No. Costar 408/446-9339 • CA-So. Bager Electronics 714/957-3367 • CO-UT Wn. Region Mktg. 303/428-8088 • FL Dyne-A-Mark 407/660-1661 • IL-WI LTD Technologies 708/773-2900 • KS-MO-IA Microtronics 913/262-1444 • MA-NH-CT Rosen Assoc. 617/449-4700 • MD-VA Tech Sales Assoc. 301/461-7802 • MI-IN-KY C C Electro 317/921-5000 • MN Electromark 612/944-5850 • NC-SC Envision 919/231/9939 • NJ JMR Sales 908/525-8000 • NY Elcom Sales 716/385-1400 • METRO-NY Niktronix 516/929-4671 • OH J.D. Babb Assoc. 216/934-4454 • OR-WA Matrex 503/245-8080 • PA Omega Sales 215/244-4000 • TX-OK Component Tech. 214/783-8831 • CANADA Dynasty Components, Inc. 613/596-9800

FREE INFO, FREE POSTAGE
Use our postage-paid reader-service cards to get more information on any of these products.

Three-phase brushless motor controller in surface-mount package. The Si9979CS controller integrates a high-side drive and low-voltage regulator functions. The controller provides commutation from Hall-effect sensors, letting you use 60 or 120° spacing. Other features include inputs for direction, quadrature selection, PWM and braking control with cross-conduction protection, current limiting, and undervoltage lockout. The device handles motor currents from 1 to 5A. When combined with the company's Little Foot power MOSFETs, the total board space is less than 3.5 in.² for controlling 20 to 40V motors. The Si9979CS costs \$7.09 (1000). **Siliconix**, Santa Clara, CA. (408) 988-8000.

Circle No. 414

Video op amp features a 3-dB bandwidth of 110 MHz at a gain of 2. The op amp drives double-terminated 75Ω coaxial cable to video levels and has a TTL-compatible disable function. Enable and disable times are 75 nsec. The device operates on any supply voltage from ±5 to ±16V and consumes 7.5 mA, regardless of supply-voltage level. You can connect outputs of multiple devices for multiplexer applications. Differential gain and phase are <0.01% and 0.01°, respectively, at 500Ω. The EL2166 comes in eight-pin plastic DIP and SOIC packages and costs \$2.90 (1000). **Elantec Inc**, Milpitas, CA. (408) 945-1323.

Circle No. 415

Digitally controlled potentiometer has audio log taper. The X9314 audio log taper E²POT provides 32 steps arranged in an audio log taper. Chip-select, direc-

tion, and increment signals select the output level, and the setting is stored in EEPROM. End-to-end resistance is 10 kΩ. \$0.86 (10,000). **Xicor Inc**, Milpitas, CA. (408) 432-8888.

Circle No. 416

DSP offers on-chip flash memory. The FlashDSP 1616 executes 50 MIPS at 5V and 30 MIPS at 3V. The on-chip 12k-word flash memory lets you quickly load, test, and reload development software. Because the FlashDSP behaves the same as the ROM-coded version, system performance does not change when you use the flash-based DSP for development and then change to a ROM-based version for production. The FlashDSP 1616 costs \$1000 (10) and is available now. Development kits with three engineering samples, software, and hardware-development tools will be available by year-end for \$20,000. **AT&T Microelectronics**, Allentown, PA. (800) 372-2447.

Circle No. 417



3.3V SRAM available in TSOP. The 15-nsec, 256-kbit M5MV278DVP-15 is configured as a 32k×8-bit device. The standby current is 100 μA max (10 μA typ) in power-down mode. Active current is 90 mA max (80 mA typ). The high speed, low power, and small package suit the device to cache-memory systems in portable


computers. In addition to the 28-pin TSOP, the device comes in DIP, SOJ, and SOP packages. \$6. (1000). **Mitsubishi Electronics America Inc**, Sunnyvale, CA. (408) 730-5900. **Circle No. 418**

64-bit RISC processor offers 150-MHz operation, family price reduction. The Orion R4600 Mips RISC μP family offers lower prices than previous versions and a 150-MHz version. The device suits Unix and Windows NT applications. Prices are \$175 for the 100-MHz version, \$250 for the 133-MHz version, and \$325 for the new 150-MHz version. All versions are available. **Integrated Device Technology Inc**, Santa Clara, CA. (800) 345-7015. **Circle No. 419**

DSP-based codec handles four speech channels. For use in private-branch-exchange and central-office switches, the SICOFL-4 PEB 2465H handles as many as four analog subscriber channels. The chip interfaces four analog telephones to the digital-switch environment, including encoding, decoding, and pulse-code-modulation circuitry. Programmable DSP functions include impedance matching to eliminate telephone-line echo, transhybrid balancing to eliminate echoes and signal losses in the subscriber-line interface circuit, and two programmable filters. Production quantities will be available in the third quarter and cost \$12.70 (10,000). **Siemens Components Inc**, Cupertino, CA. (800) 777-4363, ext 274. **Circle No. 420**

High-power semiconductor family uses ISOTOP package. The ISOTOP (SOT-227) package offers a 2500V isolation rating, a parasitic inductance of <5 nH, and a thermal resistance of 0.27°C/W in a 5-cm³ volume. The package suits

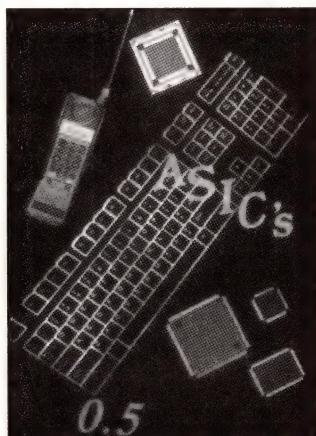500W to 3-kW industrial applications and works with the company's new TMOS family of MOSFETs, ultrafast rectifiers, and Schottky rectifiers. The TMOS devices have $R_{DS(on)}$ values from 5.5 to 80 mΩ and voltage ratings from 100 to 500V. The MTE-215N10E costs \$20 in production quantities. **Motorola Semiconductor Products Sector**, Phoenix, AZ. (602) 244-3071. **Circle No. 421**




3.3V 0.5-μm embedded-cell ASICs have 170-psec gate-access time. The M6010X devices have a gate-usage rate of approximately 70% and a maximum of 1 million available raw gates. The company offers embedded high-speed synchronous or asynchronous, single-port RAM with up to 256 kbytes per block. A 512-word×32-bit synchronous RAM has a 3.7-nsec worst-case access time. Multiport RAM is also available. The clock-distribution system can drive 5000 flip-flops with worst-case skew of <300 psec. The ASICs have a PLL with lock ranges selectable to 40 to 120 or 120 to 180 MHz. **Mitsubishi Electronics America Inc**, Sunnyvale, CA. (408) 730-5900. **Circle No. 422**

Two-chip set handles 486 system logic and X-bus peripheral control. The VT82C496 system-controller chip includes a CPU and a local-bus interface, a cache controller with write-back and write-through for caches

from 32 kbytes to 1 Mbyte, a page-mode DRAM controller, a synchronous ISA bus controller, an integrated power-management unit, and an embedded VL bus IDE controller. The other chip in the set, the VT82C406MV IXP X-bus peripheral controller, includes a multiclock generator, a keyboard controller, a real-time clock, and miscellaneous functions. The Pluto chip set is available now and costs \$18 in volume. **Via Technologies Inc**, Fremont, CA. (510) 683-3300.

Circle No. 423

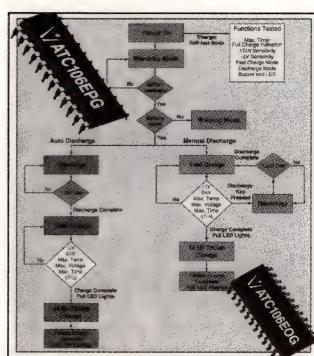

μP-based fast battery charger uses special features for NiCd and NiMH batteries. The ATC106 battery-charging IC uses industry-standard techniques, $-\Delta V$ and $\Delta T/\Delta t$, for NiCd batteries. Automatic or manual discharging is also available. For safety, the IC measures maximum temperature and maximum voltage during the charge cycle. The IC does not limit the number of batteries being charged, and it accommodates either PWM or linear-power supplies. Because NiMH batteries do not always show a peak voltage when being fast-charged, the charger IC stops charging if the voltage remains unchanged or exhibits a zero ΔV after a period of fast charging. The charger also stops trickle charging NiMH batteries after 15 hours to avoid damage. The ATC106 includes self-test and costs \$3.50 (1000). **Shoreline Electronics Inc**, Santa Clara, CA. (408) 987-7733.

Circle No. 424

2-to-1 video multiplexer has 210-MHz bandwidth at 1.4V p-p signal level.

The MPC104 multiplexer has two identical open-loop buffer amplifiers offering 79-dB channel crosstalk and 86-dB off-channel isolation at 30 MHz. Differential gain-and-phase errors are 0.03% and 0.01°, respectively. Switching transients are +13 and -4 mV. The 1-pF typ output capacitance lets you assemble multiple multiplexers into large crosspoint fields. Performance is specified for ± 5 V supplies. \$4.94 (100). **Burr-Brown Corp**, Tucson, AZ. (602) 746-1111.

Circle No. 425

PCMCIA and X-bus controllers.

The three-chip set includes the VT82C425 system controller for CPU and local-bus interface, DRAM control, ISA bus control, power management, and local bus IDE control; the VT83C465 PCMCIA socket controller for full implementation of two PCMCIA 2.0 sockets; and the VT82C406MV X-bus peripheral controller, including multiclock generator, keyboard controller, and real-time clock. The Diana chip set costs \$20 in volume. **Via Technologies Inc**, Fremont, CA. (510) 683-3300.

Circle No. 428

Low-cost 5V, 16-bit ADC combines on-chip modulator, decimator, reference, and clock. The two-channel AD1877 features a fourth-order modulator, a three-stage decimator, a voltage reference, and a clock divider. Minimum dynamic range within the 20-Hz to 20-kHz bandwidth is 92 dB, and minimum signal-to-noise is 88 dB. The converter interfaces directly to standard μPs and DSPs. Available in a 28-pin SOIC, the AD1877 starts at \$10 (1000). **Analog Devices Inc**, Wilmington, MA. (617) 937-1428.

Circle No. 426

Op amps offer high speed and low noise. The CLC426 uses a voltage feedback architecture to provide a 230-MHz gain-bandwidth product with noise specifications of $1.6 \text{ nV}/\sqrt{\text{Hz}}$ and $2 \text{ pA}/\sqrt{\text{Hz}}$. The op amp has a 400-V/μsec slew rate and settles to 0.05% in 16 nsec. The CLC426 is internally compensated for gains of two or more. The CLC428, a unity gain-stable-dual op amp, is also available. Prices start at \$3.95 (1000). **Comlinear Corp**, Fort Collins, CO. (303) 226-0500.

Circle No. 427

Three-chip set for notebook computers includes

400 to 700 MHz and provides adjustable gain for up to 40 dB of dynamic range. Each baseband may be filtered using the included fifth-order Butterworth low-pass filter, variable from 1 to 30 MHz. The device also includes a programmable counter for variable sample rates and a signal-detection function. The baseband sample rate is 60M samples/sec. Available in a 100-pin MQFP, the MAX2101 costs \$17.95 (1000). **Maxim Integrated Products**, Sunnyvale, CA. (408) 737-7600 ext 6087.

Circle No. 431



32- and 64-bit GUI accelerators have live-video capability.

The DRAM-based graphical user interface (GUI) accelerators include on-chip, 16-bit VESA advanced-feature connector DACs to provide live video. The chips allow the display of both full-screen and windowed full-motion video in noninterlaced 1024x768-pixel resolution using $\frac{1}{2}$ Mbyte of DRAM. The 32-bit TGU19440AGI includes an on-chip 108-MHz pixel clock and RAMDAC to display a 1280x1024-pixel image at 60 Hz noninterlaced. The 64-bit TGU19660XGI uses an on-chip 135-MHz pixel clock to display a 1280x1024-pixel image at 75 Hz noninterlaced. The 32-bit chip costs \$17 (OEM), and the 64-bit chip costs \$27. **Trident Microsystems Inc**, Mountain View, CA. (415) 691-9211.


Circle No. 432

6-bit quadrature digitizer combines quadrature demodulation with A/D conversion.

The MAX2101 accepts input signals from

12-bit ADC with sample-and-hold in 8-lead SOIC package. The converter uses three-wire serial I/O and consumes 20 μA at a 1k-sam-

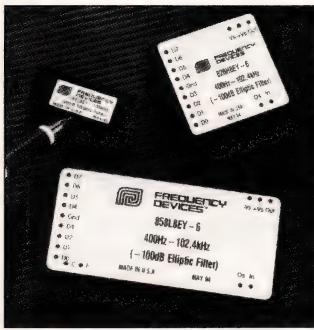ple/sec conversion rate. The converter operates from 3V supplies and is suitable for battery-power applications. When not converting, power consumption drops to 1 nA. The LTC1285 uses differential inputs, and the LTC1288 has a two-channel multiplexed input. \$6.22 (1000) in plastic DIP and \$6.63 (1000) in SOIC. **Linear Technology Corp**, Milpitas, CA. (408) 432-1900. **Circle No. 433**



Active filters provide -100-dB attenuation with low noise. A line of fixed and programmable linear-active filters provides high attenuation, and noise and distortion are low enough for use with 16-bit ADCs. The filters are factory-tuned to a user-specified corner frequency or an 8-bit tuning range from 1 Hz to 102.4 kHz. Lowpass filter types include Butterworth, Bessel, elliptic, and constant delay. Butterworth and elliptic filters are also available for highpass filtering. The D68 fixed-frequency filters start at \$120 (1000), and the programmable-frequency 828 and 858 filters start at \$275 (100). **Frequency Devices Inc**, Haverhill, MA. (508) 374-0761. **Circle No. 434**

Source-routing transparent interface for token-ring chip sets. The MU9C8148 SRT interface works with token-ring chip sets and the company's LAN content-addressable memory, providing a 128-entry instruction buffer that holds as many as seven downloadable filtering and purging

routines. The interface meets IEEE standards and provides address-filter rates of 150,000 frames/sec for minimum-length frames. \$30 (1000). **Music Semiconductor**, Colorado Springs, CO. (719) 570-1550. **Circle No. 435**

ICs provide building blocks for digital-communication networks.

The STC104 uses the DS-link serial protocol developed by the vendor and now being adopted as an IEEE standard. Each chip has 32 DS-link inputs and outputs connected through a 32x32 crossbar switch that lets you route data streams from all inputs to all outputs simultaneously. Each input link has its own programmable routing engine that lets the chip handle 200 million packets/sec. The STC101 Parallel DS-link adapter provides an interface between the serial DS-links and external systems, such as buses, peripherals, and μPs. The STC104 costs \$200, and the STC101 costs \$20 in OEM volumes. **SGS-Thomson Microelectronics**, Lincoln, MA. (617) 259-0300. **Circle No. 436**


Digital CMOS clock chip has 300-psec delay. The Equality 6600 clock-chip family have 10 adjustable outputs from 30 to 170 MHz. The chip uses digital techniques instead of voltage-controlled oscillators and PLLs to generate the clock signals. Pin-to-pin skew is 250 psec. \$18 (500). **PLX Technology Inc**, Mountain View, CA. (415) 960-0448. **Circle No. 437**

RGB-to-NTSC/PAL analog encoder drives RGB monitors directly. The AD721 includes a pin-selectable encode or bypass mode. 100-MHz triple-video amplifiers with a gain of 2 can drive 75Ω reverse-terminated loads. The monolithic encoder provides the necessary

lowpass filters and delay lines and operates from ±5V supplies. Suitable for applications such as PC-video plugin cards and multimedia systems, the device provides composite video output with 0.1% differential gain and 0.1° differential phase errors. The 29-pin PLCC costs \$6.25 (10,000). **Analog Devices Inc**, Wilmington, MA. (617) 937-1248. **Circle No. 438**

Transceiver chip set aims at 2.4-GHz wireless applications.

The TQ9205 amplifier/switch front end provides transmit and receive switching configured for half-duplex operation at both the antenna and filter ports. The receive path contains a low-noise amplifier, and the transmit path contains a 100-mW power amplifier. The TQ9206 RF up/down-converter contains mixers, buffers, and an on-chip VCO for tuning over the 2.400- to 2.483-GHz band. The buffered output may be connected directly to the divider input of a PLL synthesizer. \$9.77 (10,000). **Triquint Semiconductor Inc**, Beaverton, OR. (503) 644-3535. **Circle No. 439**

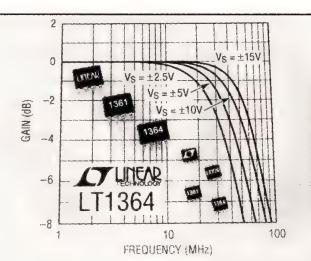

High-speed op amps offer dc accuracy and low power consumption.

The LT1361/62 voltage-feedback dual/quad op amps have a 50-MHz gain-bandwidth product and slew at 800 V/μsec, yet consume only 4 mA per amplifier. Maximum input-offset voltage is 1 mV. The LT1364/65 have a 70-MHz gain-bandwidth product, 1000-V/μsec slew rate, and 1.5-mV maximum input-offset voltage and consume 6 mA per amplifier. Differential gain is 0.06%, and differential phase is 0.04° when driving a 150Ω load. The LT1361 and LT1364 dual op amps start at \$3.37 (1000), and the quad op amps start at \$5.88 (1000). **Linear Technology Corp**, Milpitas, CA. (408) 432-1900. **Circle No. 441**

Nine-line active SCSI terminator works with 3V systems.

The UCC5614 active SCSI terminator works with 3 to 5V systems and features a selectable 110Ω and 2.5-kΩ termination mode. Channel capacitance is 2pF. \$2.90 (1000). **Unitrode Integrated Circuits Corp**, Merrimack, NH. (603) 424-2410. **Circle No. 442**



Monolithic 900-MHz GaAs down-converter operates off single 5V supply.

The AWR0900 down-converter includes an oscillator and image filter and has a 3-dB noise figure and a 15-dB conversion gain. Low-power consumption makes the device suitable for battery-powered systems. \$5 (1000). **Anadigics**, Warren, NJ. (908) 668-5000. **Circle No. 440**

SRAM modules offer 2x512kx8-bit capacity.

The EDI9F81025C-BPC CMOS SRAM module is a 36-pin SOIC package available with 70-, 85-, and 100-nsec access times. The memories are available in standard or low-power versions with data retention at 2 or 3V. Prices start at \$346 (100) for the 100-nsec version. **Electronic Designs Inc**, Westborough, MA. (508) 366-5151. **Circle No. 443**

Wide and deep FIFO buffer provides color pixel formatting. The GT-24001 color pixel formatter comprises three 32-bit-wide by 1104-location-deep synchronous FIFOs. Although usable as a 33-MHz dual-port SRAM-based FIFO, the device includes features such as data packing and the use of a planar mode to reduce frame buffer memory by 25% in color printers, scanners, and copiers. The planar mode stores each color in a separate

address space. \$89.75 (5000). Galileo Technology Inc, San Jose, CA. (408) 451-1400.

Circle No. 444

Hard-disk-drive read channel features low-power operation. The CXA1771R hard-disk-drive read channel requires 80 mA when fully powered in the read mode, 50 mA in the write mode, and 10 mA during standby. The read channel is capable of 32-Mbit/sec

data transfers and operates from 3.3 to 5.5 V. Packaged in a 64-pin QVFP, the IC costs \$15 (1000). Sony Electronics Inc, San Jose, CA. (408) 432-0190

Circle No. 445

SHORTS

The MAX662A improved 12V supply for flash memories has a 185- μ A quiescent current, a 1- μ A shutdown current and delivers 30 mA from a 4.75V input without inductors. From \$1.81 (10,000). Maxim Integrated Products, (408) 737-7600, ext 6087.

Circle No. 446

SystemView™

BY ELANIX



Workstation power on your PC. Performs in the familiar Microsoft Windows environment.

PERSONAL DYNAMIC SYSTEM SIMULATOR: Powerful. Intuitive. And instantly productive.



The industry's most flexible and versatile system design tool for today's applications:

- DSP systems
- Communications
- Signal processing
- Control systems

Industry-leading features include:

- Analog, digital, mixed mode, and multi-rate system development
- Linear and non-linear system design
- Laplace and z-domain linear system specification

Join the enthusiastic users in industry and in universities worldwide... Discover SystemView: the most powerful system design tool available today.

Call ELANIX now. **1-800-535-2649**

5655 Linder Canyon Rd., Suite 304 • Westlake Village, CA 91362 • (818) 597-1414 • Fax (818) 597-1427. © ELANIX, Inc. 1994. SystemView is a trademark of ELANIX, Inc.

The AD600 and AD602 dual-channel variable-gain amplifiers and the single-channel AD603 are now military-qualified. Duals start at \$52.50 (100), and the AD603 starts at \$35 (100). Analog Devices Inc, (617) 937-1428.

Circle No. 447

The following ADCs and voltage references have received standard military drawing numbers: AD87-1SD/883B, AD871SE/883B, AD87-2SD/883B, AD872SE/883B, AD67-4BTE/883B, AD757SE05/883B, and AD780-SQ/883B. Analog Devices Inc, (617) 937-1428.

Circle No. 448

The ADC4322B 16-bit sampling ADC digitizes at 2M samples/sec, has no missing codes, and operates from -25 to +85°C. The hybrid costs \$1194 (100). Analogic Corp, (508) 977-3000.

Circle No. 449

Weitek Corp is lowering the price of its SPARC Power µP. The device, a CPU upgrade for SPARCstation 2 and IPX workstations, now costs \$1200 with an installation kit and \$995 for additional devices, with discounts for 100-piece orders. Weitek Corp, (408) 738-8400.

Circle No. 450


Analog Devices has introduced a number of improved second sources with competitive prices: the ADM202, 222, 232A, and 242 dual RS-232C transceivers; the ADG441, 442, and 444 quad SPST switches; the ADG406, 407, and 426 16-channel multiplexers; and the ADM663 and 666 linear regulators. Analog Devices, (617) 937-1428.

Circle No. 451

New! Electrical Engineering Pack

"A Must for Electrical Engineers..."

Call 1-800-441-MATH

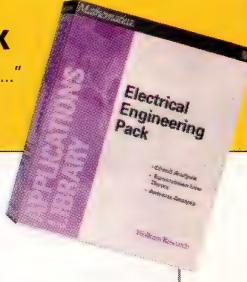


OTHER SYSTEMS CAN GET YOU ONLY SO FAR...



Engineers and scientists who start with other technical software programs soon reach a point they can't get past. The project isn't finished, but the software is. What can they do then but buy and learn yet another program for the next leg of the project, or return to pencil and paper to finish it out.

Fortunately, many engineers and scientists start with *Mathematica*. And they just keep going.

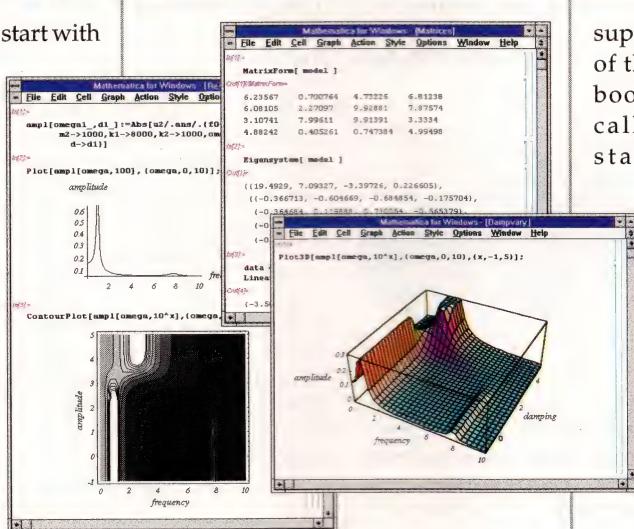Mathematica helps them past the standard calculations, and on to the more complex. Thousands of algorithms are at their fingertips to help them solve all kinds of technical problems. And nearly a hundred special-purpose packages are included free with *Mathematica* to take you even further. Add to that a revolutionary user interface, graphical abilities beyond comparison, and a



Only Mathematica notebooks enable users to create interactive documents combining text, live formulas, and graphics that can be modified within the document at any time and easily organized into a hierarchical outline.

symbolic programming language that makes it unprecedentedly easy to translate ideas into programs—and your possibilities are endless.

The award-winning guide that comes with the program gets you started quickly and easily. For even more


support, you can always turn to one of the over 50 *Mathematica*-related books, tutorials, and journals, or call on one of our user support staff for personal assistance.

So you see, *Mathematica* is *the complete system* that never leaves you stranded.

To get the latest information call:

1-800-441-MATH

(U.S., Canada)

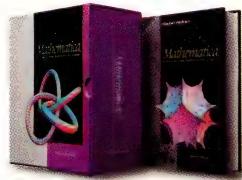

Wolfram Research

Wolfram Research, Inc.

+1-217-398-0700; fax: +1-217-398-0747; email: info@wri.com

For European inquiries:

Wolfram Research Europe Ltd.

+44-(0)1993-883400; fax: +44-(0)1993-883800

email: info-euro@wri.com

Representatives in over 50 countries; contact main offices.

FREE INFO, FREE POSTAGE
Use our postage-paid reader-service cards to get more information on any of these products.

Multibus II CPU and I/O-controller board operates at up to 100 MHz. The CP 486/CBX offers a choice of processors ranging from the 33-MHz 486DX to the 100-MHz 486DX4. Memory modules let you populate the board with up to 32 Mbytes of DRAM. A CBX 16-bit memory-expansion interface lets you create I/O subsystems within a Multibus II system, using the company's digital- and analog-I/O cards. The board also accepts iSBX modules. Prices start at \$3552 for a 33-MHz 486 with 8 Mbytes of DRAM. **Concurrent Technologies Inc**, Champaign, IL. (217) 356-7004.

Circle No. 467


VME-based FDDI adapters have OS-9 and Internet support package. The PT-VME600 adapter works with multimode optical fiber and provides reliable and secure data transmission between nodes. The PT-VME602 node adapter for unshielded twisted-pair category 5 cable takes advantage of existing wiring and helps reduce the cost per node. The PT-VME600 starts at \$4195, and the PT-VME602 starts at \$3095. The OS-9 Internet support package is available on all of the company's FDDI node adapters. **Performance Computer**, Rochester, NY. (716) 256-0200.

Circle No. 468

Emulator board converts the Motorola 68HC0-5P8EVS system for real-time in-circuit emulation. The EVSK1-ICE recreates the 68HC705K1 interrupt function and 64-bit personality EPROM subsystem in hardware for real-time emulation in target systems. The interrupt function provides external-


level triggering or edge-triggering interrupt capability on the IRQ and PA0-PA3 pins. \$295. **Wytec Co Inc**, Bloomingdale, IL. (708) 894-1440. **Circle No. 469**

VMEbus board is compatible with the Sun SPARCstation 5. The CPU-5CE uses a microSPARC II processor and delivers performance comparable to that of the SPARCstation 10 Model 40, according to the manufacturer. Onboard memory can range from 8 to 64 Mbytes of DRAM. The board includes a full range of I/Os, including fast SCSI, Ethernet, floppy disk, parallel port, serial and keyboard/mouse port. Software for the processor includes Solaris 1.1 and 2.3. Wind River Systems' VxWorks is available for users requiring a real-time operating system. Including 16 Mbytes of memory, the 6U VME board costs \$4995. **Force Computers Inc**, San Jose, CA. (408) 369-6000. **Circle No. 470**

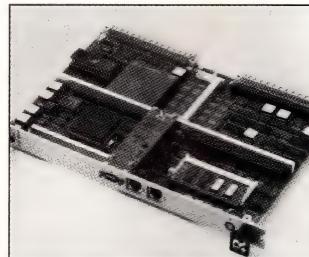

VMEbus communications controller provides high-bandwidth serial communication channels. The SBCC-1 communications-controller board provides four high-bandwidth and three low-bandwidth-serial-communication channels. The board includes support for eight communication protocols, including HDLC, LAPB, X.25, Ethernet, ISDN T1/E1, and X.21. The four serial communication channels operate autonomously, allowing simultaneous operation of different protocols. If the

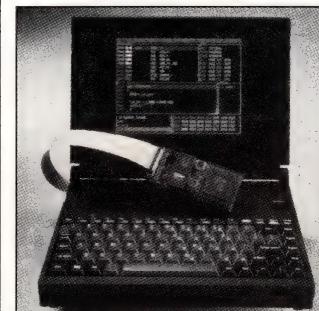board's performance becomes processor-limited by the internal 68360 processor, you can add a 68040 processor and obtain a fourfold increase in performance. \$3495. **Radstone Technology Corp**, Montvale, NJ. (201) 391-2700. **Circle No. 471**



Development system for TMS320C5x DSPs provides nonintrusive, full-speed emulation. The EDS320C5X expandable development system provides access to all memory and internal DSP registers. The development system connects to a PC's bidirectional printer port and obtains power either from the target system or from an external wall-mount supply. Based on a card-stacking design, the development system lets you add additional memory and other options by adding cards. The source-level debugger is compatible with Texas Instruments' C compiler and assembler. \$1499. **Spectrum Digital Inc**, Sugar Land, TX. (713) 561-6952. **Circle No. 472**

VME64 single-board computers feature micro-SPARC and microSPARC II processors. The micro-SPARC-based SPARC LXEP-PLUS is compatible with Sun's SPARCclassic, and the microSPARC II-based SPARC 5/64 is compatible with Sun's SPARCstation 5. Both boards offer 8 to 96 Mbytes of DRAM. Software for the boards includes Solaris 1.1, 2.3, and real-time operating

systems such as VxWork 5.1. Prices start at \$5495. **Themis Computer**, Pleasanton, CA. (510) 734-0870. **Circle No. 473**

Real-time multitasking kernel for R4000 Mips processor. The Nucleus PLUS kernel includes pipes, queues, and mail boxes for intertask communications. The kernel provides counting semaphores, events, and signals for intertask synchronization. The kernel costs \$7495, including source code and licensing for a single product line. There are no runtime royalties. **Accelerated Technology Inc**, Mobile, AL. (205) 661-5770. **Circle No. 474**

Family of VMEbus boards uses Analog Devices ADSP-21060 SHARC DSP. The 6U VMEbus boards contain one to eight DSPs and offer 120- to 960-Mflops performance. The IXZ8xxx four-processor board has three banks of global memory with a capacity of up to 256 Mbytes in each bank, two high-bandwidth I/O module connectors, eight link ports with 40-Mbyte/sec capacity. The IXZ8xxx costs less than \$15,000. **Ixthos Inc**, Silver Spring, MD. (301) 572-6700. **Circle No. 475**

Development system for TMS320C5x includes µP support. The Slalom-50 development system includes two 57-MHz TMS320C51 DSPs, 64k words of program memory for each DSP, 64k words of data memory for each processor, 4kx16-bit dual-port shared memory, and a source-code debugger. The development system is suitable for developing single- or dual-processor designs, shared-memory systems, time-division multiplex, and serial-port interprocessor communication schemes. \$3995.

White Mountain DSP Inc, Nashua, NH. (603) 883-2430. **Circle No. 476**


Mezzanine board for VMEbus transfers data at 200 Mbytes/sec.

The AutoBahn Spanceiver kit lets you create systems with high sustained data-transfer rates. The starter kit costs \$4990. **PEP Modular Computers**, Scottsdale, AZ. (602) 483-7100.

Circle No. 477

Multiband digital-receiver modules for VME and Multibus II. The modules accept 12-bit digitized data at sample rates as high as 70 Msamples/sec. Two narrowband receivers and one wideband receiver perform frequency down-conversion, lowpass filtering, and decimation of the sampled output. The modules implement conventional radio-receiver functions with digital circuits, providing a front end suitable for digital signal-processing systems. Both the VMEbus Model 4272 and the Multibus II Model 4372 start at \$8995. **Pentek Inc**, Norwood, NJ. (201) 767-7100.

Circle No. 478

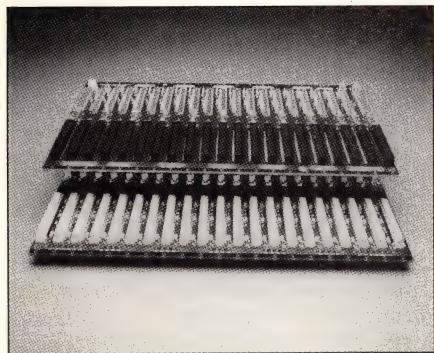

Monolithic VMEbus backplanes offer automatic daisy-chain option. The monolithic backplanes improve the performance and reliability of VMEbus systems by using a common J1/J2 substrate for better impedance matching, instead of separate substrates. The backplanes meet all requirements of the VME 64 standard. Prices range from \$310 for a two-slot backplane to \$950 for a 21-slot backplane. **Dawn VME Products Inc**, Fremont, CA. (510) 657-4444.

Circle No. 479

S-Bus board uses AT&T's floating-point DSP32C. The SB32C board is available with one or two processors. The single-processor version features 25-Mflops peak performance and

includes one stereo codec and 512 kbytes of private SRAM. The dual-processor version features 50-Mflops peak performance and includes 512 kbytes of private SRAM for each processor and four CD-quality audio input/output channels. The single-processor SB32C1 costs \$1500, and the dual-processor SB32C2 costs \$2500. **Communication Automation & Control Inc**, Allentown, PA. (610) 776-6669. **Circle No. 480**

Family of ruggedized commercial and military enclosures.

Open-architecture chassis systems for VME, Multibus, Futurebus+, ISA, and EISA are available. Form factors include rack-mount, ATR, hard-point and mobile mountings for industrial, shipboard, aircraft, and ground mobile applications. **AP Labs Inc**, San Diego, CA. (619) 546-8626. **Circle No. 481**


Create Custom PC Applications Without Custom Programming!

**VISUAL
DESIGNER™
BEYOND PROGRAMMING...**

**For Test,
Measurement,
Control & More.**


Acquire Your Data in Just Two Steps

Create the applications you need—without programming! Visual Designer is a revolutionary, new software development tool. With it you'll save days, weeks, even months of development time. To create your application just select the appropriate function blocks, and then connect them with your mouse. Test, measurement, control, streaming data to disk, spectrum analyzers, strip chart recorders, instrument panels—and much more. It's that simple.

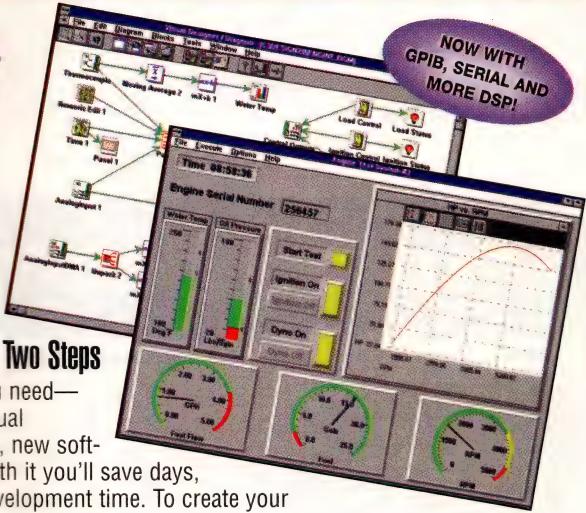

Your Complete Solution \$995!

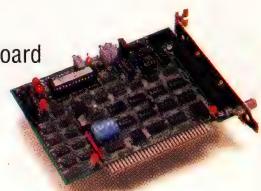Buy Visual Designer and our new low-cost data acquisition board by Dec. 30, 1994 and save \$455! You'll get Visual Designer, the PCI-20428W and a termination panel for just \$995. Best of all, the board comes complete with a lifetime warranty.



PCI-20428W Low-Cost Data Acquisition Board

- 16SE/8Diff Analog Inputs, 100kHz
- Gains (1, 2, 4, 8) or (1, 10, 100)
- 2 Analog Outputs, 100kHz
- 1 Counter/Timer, 2 Rate Generators
- 8 Digital Inputs, 8 Digital Outputs
- DMA Channels for Analog I/O
- Streaming to Disk/Transient Capture
- List Price: \$395 (without termination)

Order Today!

Call (800) 685-9911, Operator 619

Fax: Attention 619, (602) 573-0522

Mail: Intelligent Instrumentation

Order Desk 619

6550 S. Bay Colony Dr., MS130

Tucson, AZ 85706



MICROSOFT
WINDOWS
COMPATIBLE

**INTELLIGENT
INSTRUMENTATION™**

INTERNATIONAL OFFICES:
France • Germany • Italy • Japan • United Kingdom

A Burr-Brown Company



FREE INFO, FREE POSTAGE
Use our postage-paid reader-service cards to get more information on any of these products.

Design tool helps FPGA vendors test and refine new architectures. The Figaro Architect's Workbench uses parameterized behavior models to test new architectures. According to the company, the tool can cut development time by as much as 50%. The tool lets FPGA vendors test architectures during the design stage against PREP benchmarks or actual customer applications. Architect's Workbench starts at \$250,000. Cadence Design Systems Inc, San Jose, CA. (408) 943-1234. **Circle No. 394**

Simulator runs faster when using VITAL-compliant models. The V-Systems VHDL simulator now runs two to eight times faster for designs using VITAL-compliant gate-level models or

primitives. V-Systems costs \$2495 for use on PCs under Windows and \$9995 for a floating workstation license. **Model Technology Inc**, Beaverton, OR. (503) 641-1340. **Circle No. 395**

Graphical state-machine design tool offers animation for following state transitions.

BetterState Pro V2.0 lets you graphically design state machines and then automatically generates the state machine code in C, C++, Verilog, or VHDL. In addition to standard state-machine design techniques, the tool lets you use extended state diagrams with hierarchy and concurrence and multirate-firing Petri Net design-entry methods. During design, you can interactively view a series of state transitions graphically. After designing and simulating a state machine, you can use the tool's animated playback capability to view state-transition sequences. The software also computes state-visitation statistics for analyzing

designs. BetterState Pro costs \$495, including one code generator. Additional code generators for other languages are \$99 each. **R-Active**, Cupertino, CA. (408) 252-2808. **Circle No. 396**


Design-for-test software adds IDDQ, ATPG, and scan-test improvements. FlexTest and FastScan have new algorithms for selecting a compact set of test vectors for IDDQ testing. New algorithms in DFTAdvisor help minimize area on partial-scan designs while providing higher test coverage. FastScan and FlexTest cost \$92,400, and DFTAdvisor costs \$20,000. **Mentor Graphics**, Wilsonville, OR. (503) 685-8000. **Circle No. 397**

Tool links corporate component database with schematic capture. PROdatabook is a PC-based component data-entry and -verification tool that links schematic capture with component databases. The tool costs \$1495 for a single user and \$14,995 for a site license. **Viewlogic Systems Inc**, Marlborough, MA. (508) 480-0881. **Circle No. 398**

IC power-analysis tool lets you analyze power consumption early in the design cycle. DesignPower provides both probabilistic and simulated power-analysis tools. Probabilistic power analysis is useful for evaluating power consumption during early design stages. Simulated power analysis uses switching activity of primary inputs and internal nets from a logic simulator, providing more accurate results in the later stages of gate-level design. DesignPower costs \$30,000. **Synopsys Inc**, Mountain View, CA. (415) 962-5000. **Circle No. 399**

Windows-based pc-board-design tool adds on-line DRC and built-in autorouter. TangoPRO PCB version 2.5 now offers on-line design-rule checking (DRC) that helps you find and fix design problems while you design. The built-in QuickRoute maze router handles simple routing requirements. Editing features have also been improved in the new version. TangoPRO PCB costs \$5950, and TangoPRO PCB Lite, a reduced-function version without on-line DRC, costs \$1995. **Accel Technologies Inc**, San Diego, CA. (619) 554-1000. **Circle No. 400**

Trimmers Anyone?...

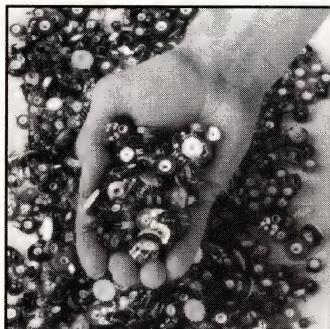

Piher International Corp. has a trimmer to satisfy your needs, regardless of application. For example, our new 6 mm trimmers: the cost efficient N6 Series for automatic insertion use and the cermet PJ6/PS6 Series for use where size is critical.

Consider our enclosed 10mm or 15mm carbon PT Series, or their cermet track counterparts, the PTC Series which offers 86 different adjustment and

mounting combinations. And, Piher offers a large selection of shafts and thumb wheels to suit any requirements.

Contact us for samples, quotations, product literature or more detailed information. As the most widely used trimmers in the U.S., you'll see how Piher beats the competition...hands down.

PI-HER
INTERNATIONAL CORP.
MEGGITT
ELECTRONICS

903 Feehanville Drive

Mt. Prospect, IL 60056

Telephone: 708/390-6680

Toll-Free: 800/323-6693

Faximile: 708/390-9866

CIRCLE NO. 91

FREE INFO, FREE POSTAGE
Use our postage-paid reader-service
cards to get more information on
any of these products.


Open-frame linear supplies sport toroidal transformers. A line of open-frame linear supplies have toroidal transformers. The transformers enable these supplies to have increased efficiency, lighter weight, lower temperature rise, less creepage distance, and lower leakage current than supplies having conventional transformers. Outputs range from 5 to 28V dc. \$72.50 (25), delivery six to eight weeks. **International Power**, Oxnard, CA. (805) 981-1188. **Circle No. 401**

High-density dc/dc converters in 100 to 300W power ranges. These 100 to 300W converters accept inputs from 48 to 300V dc and provide a single output ranging from 1.2 to 15V. HDL series converters deliver full output power with base-plate temperatures as high as 85°C. HDK series converters are similar but have monitoring and control functions referenced to either the primary or the secondary. HDM series converters allow full output power at base-plate temperatures of 100°C. The converters measure 4.6×2.4×0.5 in. and have an MTBF of more than one million hours. From \$137 for the HDK100 series to \$299 for the HDM300 (100). **Digital Power Corp**, Fremont, CA. (510) 657-2635. **Circle No. 402**

DC/DC converters available in surface-mount package. The 1W HL01 and 2W HL02 are available in 24-pin DIP and SMD packages. Up to 48 models of each type are available with input ranges from 5 to 24V dc and single or dual outputs from 5 to 15V. All devices are rated for full power at 70°C with no external heatsink. OEM pricing: \$5 for the HL01; \$6

for the HL02. **Burr-Brown Power Convertibles Corp**, Tucson, AZ. (602) 628-8292. **Circle No. 403**

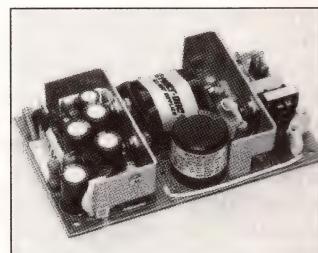Ruggedized dc/dc converters offer up to 200W output power. The LC810 series converters use full military fixed-frequency design and construction and meet MIL-STD-810 environments. \$700 in volume. **EG&G Power Systems Inc**, Covina, CA. (818) 967-9521. **Circle No. 404**



40W triple-output supply has 5V at 5A. The MAP40-3500 supply also has 12V at 1A and -12V at 0.5A. The 3×5×1.6-in. supply provides automatic ac input selection from 90 to 264V ac, onboard filtering that meets FCC and VDE Class B conducted-emission requirements, a variety of safety agencies' certification, and a two-year warranty. \$49 (100). **Power-One Inc**, Camarillo, CA. (805) 987-8741. **Circle No. 405**

0.75W dc/dc converter is available in 14-pin DIP and surface-mount packages. The HPR1XX unregulated converters accept 5, 12, 15, and 24V inputs and have single or dual outputs. The converters are rated for full power operation to 85°C without heatsinks. <\$5 (OEM qty). **Burr-Brown Power Convertibles Corp**, Tucson, AZ. (602) 628-8292. **Circle No. 406**

Triple-output linear power supply designed for pc-board mounting. The Model 3.15.1000 low-noise linear power supply provides

±15V at ±100 mA and 5V at 1A. Typical output noise is 2 mV rms. Line and load regulation is ±0.2% maximum, and voltage accuracy is ±1%. The supply is housed in a 3.5×2.5×1.5-in. case and has an operating temperature of -25°C to +50°C. Standard input is 115V ac, with other modules available for 100, 220, 230, and 240V ac. \$115.76 (100). **Calex Mfg Co Inc**, Concord, CA. (510) 687-4411. **Circle No. 407**


600W switcher has low profile. The series 126 switching power supply measures 5×13.5×2.5 in. and accepts inputs from 90 to 132 and 180 to 264V ac. Model 126-01 offers 5V dc at 100A, 12V dc at 20A, and -12V dc at 10A. Total supply output power is limited to 600W with 50-cfm airflow. \$435 (1000). **Conversion Equipment Corp**, Orange, CA. (714) 637-2970. **Circle No. 408**

5W dc/dc converter operates from -55°C to +125°C. Model 2578 converter is hermetically sealed in a 0.38×1.06×1.06-in. package. The converter operates from 28V dc with MIL-STD-704 or MIL-STD-1275 surge characteristics. Available in single-, dual-, and triple-output configurations, the converters start at \$350 (10). **Modular Devices Inc**, Shirley, NY. (516) 345-3100. **Circle No. 409**

Subminiature linear power supply provides 5V dc at 300mA. The 1.75×2.26×1.0-in. model 21-30 provides a low-noise 5V output from 115V ac input (optionally 100, 220, 230, or 240V ac). The supply has current-limiting short-circuit protection, 1000V-rms isolation, and a case-operating temperature of -25°C to +50°C. \$67.20. **Calex Mfg Co Inc**, Concord, CA. (510) 687-4411. **Circle No. 410**

4W dc/dc converter offers high isolation for medical applications. The HB04 converter has 8000V isolation; 18 models are available with inputs ranging from 5 to 15V and single or dual outputs ranging from 5 to 15V. The converter also offers low isolation-barrier capacitance, suiting the device for driving IGBTs in motor-drive applications. <\$40. **Burr-Brown Power Convertibles Corp**, Tucson, AZ. (602) 628-8292. **Circle No. 411**

Compact dc/dc converters provide bias supply voltage for LCD contrast. Packaged in SIPs, these converters accept either 4.5 to 5.5V dc or 10 to 25V dc. HN and HW models offer outputs of -22, -23, or -24V dc. The EPN series has an output adjustable from -14 to -24V dc, and the RD series' output is adjustable from 24 to 40V dc. Power ratings range from 0.5 to 1.8W. From \$3.50 (OEM qty). **Xentek Inc**, San Marcos, CA. (619) 471-4001. **Circle No. 412**

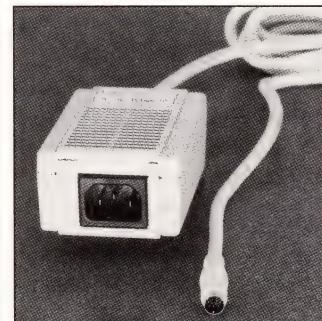

20W desktop power supplies available with single, dual, and triple outputs. Vulcan line switching power supplies are available in desktop versions measuring 3.9×2.5×1.5 in. This power-supply line has all major safety and EMI approvals, including medical. Outputs range from 3.3 to 24V dc. From \$25 (1000). **LZR Electronics Inc**, Gaithersburg, MD. (301) 921-9440. **Circle No. 413**

FREE INFO, FREE POSTAGE
Use our postage-paid reader-service cards to get more information on any of these products.

16-bit, 100k-sample/sec ADC board costs \$699.

The 16-channel (eight differential) CIO-DAS 1602/16 samples twice as fast as boards with which it is compatible. A 512-point FIFO buffer stores new data during DMA transfers, enabling seamless acquisition. Software-programmable gains provide 1.25, 2.5, 5, and 10V unipolar and bipolar ranges. The board also contains two 12-bit DACs, three 16-bit counters, and 32 bits of digital I/O. Computer Boards Inc, Mansfield, MA. (508) 261-1123. **Circle No. 452**

Windows-based tool set simplifies development of DSP applications. Win-Spox speeds the development of Windows 3.1-based instrumentation, data-acquisition, and signal-analysis applications by allowing Windows software to start, stop, and communicate with DSP-resident tasks. Communication occurs via messages and streaming data. The tool set, which is based on the Windows Resource Manager Interface (RMI), is indifferent to the type of DSP chip used (although the DSP must run the vendor's Spox V2.0 DSP OS) and to whether the DSP resides on the PC's system board or on an I/O card. \$3000. Spectron Microsystems Inc, Santa Barbara, CA. (805) 968-5100. **Circle No. 453**

PLD ATPG software generates race-free vectors in minutes. FS-ATG V3.0 software uses a full circuit simulator to analyze PLDs' internal logic. Starting from the simulation, the package develops race-free vectors within minutes. By using menus, you can set the degree of fault coverage you desire, specify the maxi-

mum permissible runtime, and define the information you want presented in testability reports. The package produces vector definitions in JEDEC format. An optional translator converts these into formats suited to programmers, component testers, and in-circuit ATE. From \$1900. Flynn Systems Corp, Nashua, NH. (603) 891-1111. **Circle No. 454**

Stand-alone IC programmer handles gangs, sets, and sets of sets up to 64 bits wide. Model 2000 takes no more time to program 16 devices than it takes to program one. It accepts 8-, 16-, 32-, and 64-bit data and works with devices having as many as 94 pins packaged in PLCCs, QFPs, TSOPs, DIPs, SOICs, and others. The unit programs, verifies, and sum-checks 1-Mbit EPROMs in 18 sec; 2-Mbit parts take 34 sec. \$1995; socket modules, \$995. Bytek Corp, Boca Raton, FL. (407) 994-3520. **Circle No. 455**



Multiproduct calibrator eases ISO 9000 registration. The 5500A calibrates digital and analog multimeters, digital and analog scopes (to 200 MHz), thermometers, power meters, harmonic analyzers, process calibrators, data loggers, current transducers, and chart recorders. The unit provides dc and ac voltages to 1 kV, dc and ac current to 11A, resistance from a short circuit to 330 MΩ, frequencies from 2 Hz to 2 MHz with multiple waveforms, and capacitance from 330 pF to >1 μF. It also simulates thermocouples and RTDs from -250 to +2310°C and dc and ac power to 11 kW. All capabilities reside in a 7-in.-high

rack-mountable unit that operates by itself or with a PC. \$9995; scope-calibration option, \$6500; software, \$2500. Fluke Corp, Everett, WA. (800) 443-5853. **Circle No. 456**

Graphical instrument-control software works with Radisys embedded VXI controller. HP VEE for Windows, a programming system in which you write programs by interconnecting icons, now runs on Radisys Corp's EPC-7 embedded VXIbus controller. Until Nov 30, the controller with VEE for Windows factory-installed on the hard drive costs \$8735—\$750 less than the regular price. Also until Nov 30, either HP VEE for Windows or Data Translation Inc's DT VEE for Windows (a version of VEE that supports Data Translation's data-acquisition boards) cost \$998, 50% less than the regular prices. Hewlett-Packard Co, Santa Clara, CA. (800) 452-4844. **Circle No. 457**


Diagnostic tool for RS-232C or CCITT V.24 data interface. The Model 700 EIA RS-232C interface analyzer helps diagnose communication-interface problems on modems, multiplexers, terminals, and computers. The unit connects between data-terminal equipment and data-communications equipment to provide access and monitoring of all data, timing, and control signals. \$195. Electro Standards Laboratory Inc, Cranston, RI. (401) 943-1164. **Circle No. 458**

Data-logging add-on software for LabView 3.0 provides historical trending. Fast HIST suits data logging at up to 10 samples/sec. Fast HIST and Standard HIST are bundled together in HIST 3. \$250. Gary Johnson, Livermore, CA. (510) 606-1335. **Circle No. 459**

FFT library suits DSP and spectral-analysis-development applications

Prime Factor FFT Library provides routines written in assembly language for fast execution that are callable from any language. The software computes forward and inverse FFTs of signals allowing frequency-domain analysis of signals recorded in the time domain. Windows version, \$395; DOS version, \$295. Alligator Technologies, Costa Mesa, CA. (714) 850-9984. **Circle No. 460**

ISA bus board digitizes waveforms to 12-bit resolution at 60 Msamples/sec. The DA60 board digitizes a single channel at up to 60M samples/sec or two channels at up to 30M samples/sec simultaneously. Each channel has 256k words of memory, or you can use the full 512k words when recording a single channel. Digital attenuators provide a full-scale input-voltage range of 100 mV p-p to 5V p-p with an input impedance of 50Ω. The board includes a library of C functions for developing custom applications. \$4900. Signatec Inc, Corona, CA. (909) 734-3001. **Circle No. 461**

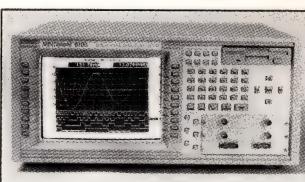

DSO has sourcing and measuring capability that lets you configure system for ATE applications. The System 8100 Series digital storage oscilloscope (DSO) has a variety of plug-in modules that let you configure the system for self-contained mixed-signal test-and-measurement applications. The basic DSO has a 100-MHz bandwidth, 100M sample/sec digitizing rate, and 100-ps timing resolution. The system captures

multiple channels of digital and analog waveforms simultaneously, depending on the plug-ins used. A built-in 3.5-in. floppy-disk drive stores waveforms. The DSO will be available in the fourth quarter. \$3500. Mint Systems Corp., Milpitas, CA. (408) 262-7171.

Circle No. 462

E-beam prober for advanced ICs offers 20× speed improvement.

The IDS 10000 acquires detailed waveform information on advanced chips in less than 1 minute. The speed improvement results from using a thermal-field-emission column. Other prober features are a 5-mV-rms noise specification and the ability to measure ac waveforms down to 50 mV. The prober costs more than \$1 million. Schlumberger Technologies, ATE Division, San Jose, CA. (408) 453-0123.

Circle No. 463

ISA bus and VESA local-bus extender operate at 50 MHz. The FVL/ISAext-S extender brings all 90 VESA local-bus lines and all 88 ISA bus lines to logically ordered rows of push-on test posts, which connect to any logic analyzer or any board mounted on the extender. The logical ordering of signals simplifies test-point connections instead of the confusing physical ordering of conventional extenders. The board also has test jacks that output a voltage proportional to the current drawn by the board under test. \$249. Ultraview Corp., Fremont, CA. (510) 657-9501.

Circle No. 464

turnkey portable-PC-based system costs \$5837. Carman Enterprises, Loveland, OH. (513) 677-5363.


Circle No. 465

Data-acquisition and -analysis software suits real-time applications. Viewdac 2.2 works with the company's instruments and IEEE-488 and RS-232C instruments. Enhancements available in the new version

include a call task that works similarly to a macro or subroutine, letting you use the same instructions more than once in the same application. An array-display task reduces the coding needed to create displays of numeric-value arrays. Added dialog boxes help you create the control lists for controlling task execution. Application Development Package, \$1995; runtime license, \$400. Keithley Metrabyte, Taunton, MA. (508) 880-3000.

Circle No. 466

Our Performance . . . Is Matchless!

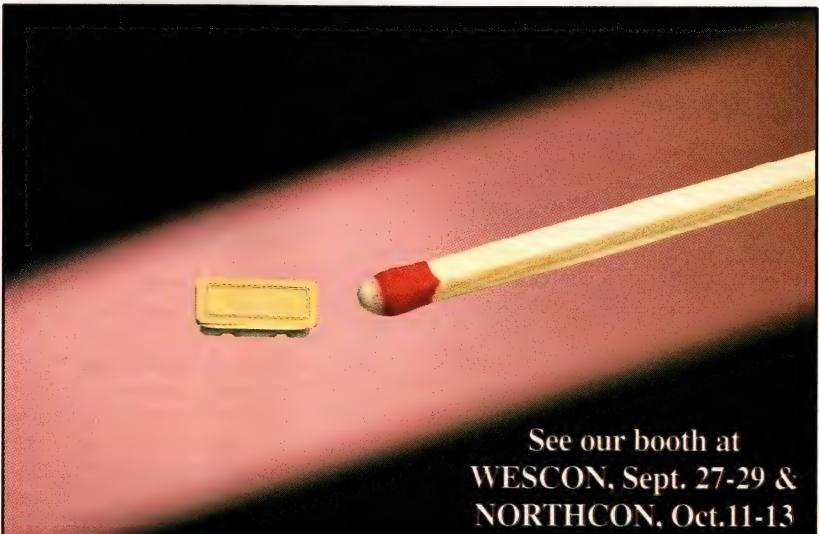

See our booth at
WESCON, Sept. 27-29 &
NORTHCON, Oct. 11-13

Ecliptek Introduces the ECCM2 2.5 MM Ceramic SMT Crystal for PCMCIA

- Designed For All PCMCIA Applications
- Common Chipset Specifications In Stock
- Frequency Range From 3.500MHz to 70.000MHz
- Tape And Reel Standard For Automatic Insertion

Crystals • Clock Oscillators • Inductors

*To Access All Ecliptek Current Data Sheets,
& Our Fax-On-Demand System*


1-800-ECLIPTEK



Fax: (714) 433-1234


3545 Cadillac Ave. • Costa Mesa, CA 92626

CIRCLE NO. 69

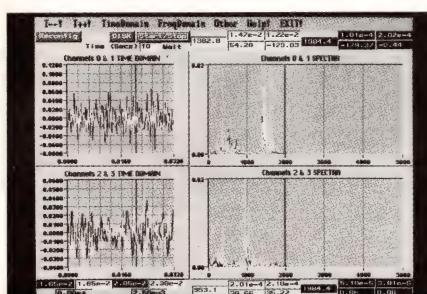

Four-channel PC-based logic analyzer uses National Instruments data-acquisition board. The DBA PC-based spectrum analyzer software runs under DOS or Windows and uses the AT-A2150 data-acquisition board. The spectrum analyzer performs single and double integration, power-spectrum analysis, FFTs, and windowing using Hamming, Blackman, Kaiser, triangular, rectangular, and Hanning windows. Software, \$1195 for DOS systems; \$1495 for Windows systems. A

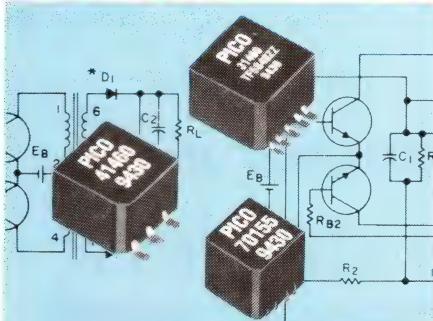ULTRA-MINIATURE
SURFACE MOUNT
Transformers & Inductors



Gull Wing/J Lead

These units have gull wing construction which is compatible with tube fed automatic placement equipment or pick and place manufacturing techniques. Transformers can be used for self-saturating or linear switching applications. The Inductors are ideal for noise, spike and power filtering applications in Power Supplies, DC-DC Converters and Switching Regulators.

- Operation over ambient temperature range from -55°C to +105°C
- All units are magnetically shielded
- All units exceed the requirements of MIL-T-27 (+130°C)
- Transformers have input voltages of 5V, 12V, 24V and 48V. Output voltages to 300V.
- Transformers can be used for self-saturating or linear switching applications
- Schematics and parts list provided with transformers
- Inductors to 20mH with DC currents to 23 amps
- Inductors have split windings

Delivery—
stock to one week

See EEM
or send direct
for Free PICO Catalog.
Call toll free **800-431-1064**
in NY call **914-699-5514**
FAX 914-699-5565

PICO Electronics, Inc.

453 N. MacQuesten Pkwy., Mt. Vernon, N.Y. 10552

CIRCLE NO. 89

FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.

Color X terminals break \$1000 barrier.

The ECX breaks the \$1000 price barrier for a color X terminal system. The base electronics cost \$845 for an entry-level system; adding a low-cost color PC monitor results in a total cost of <\$1000. The ECX is a MC68020-based unit that you can combine with any SVGA VESA-conformant multisync monitor. Network Computing Devices Inc, Mountain View, CA. (415) 694-0650.

Circle No. 380



AT-compatible workstations offer Pentium performance.

The Series 400 industrial, AT-compatible workstations provide Pentium performance and a choice of flat-panel displays. The rugged systems suit industrial-operator-interface, monitoring, and control applications that have severe space constraints or high EMI. The workstations come with a 486SX/33, DX/33, or DX2/66 processor; the CPU board can also accept a 486DX4/100 or Pentium P24T. Display choices include a 10.4-in., high-brightness, monochrome, electroluminescent display or a color TFT LCD. From \$5000. Nematron Corp, Ann Arbor, MI. (313) 994-0591.

Circle No. 381

486-based computer works on passive backplane.

The CAT1015 single-board computer for passive backplanes has processor options that include a 100-MHz 80486 DX4 in a full-size, AT expansion-card form factor. Page-mode DRAM with 8 kbytes (16 kbytes for 80486 DX4) of internal cache provides zero-wait-state performance. Up to 64 Mbytes of onboard system memory are available, accepting 256-kbyte, 1-Mbyte, or 4-Mbyte×36-bit SIMMs. \$2045 without RAM. Diversified Technology, Jackson, MS. (601) 856-4121.

Circle No. 382

Removable drive has 4.2-Gbyte capacity.

The Mercury 4.2-Gbyte Superfast Drive (R4-420XS-ME) uses a fast SCSI-2 interface for data transfers as fast as 10 Mbps. The drive's fully sealed, static-protected enclosure provides isolastic shock absorption. With a 7200-rpm spindle speed, the drive has an average seek time of <8 msec. Additionally, the drive uses an internal 1-Mbyte cache and contains support for fault tolerance, RAID (redundant array of inexpensive disks), and network environments. \$3999. Mega Drive Systems Inc, Beverly Hills, CA. (310) 247-0006.

Circle No. 383

Minicartridge backup drive has 680-Mbyte capacity.

The Tape510 1/4-in. cartridge (QIC)-tape backup drives store 255 Mbytes using standard tape cartridges (510 Mbytes with compression) or, with extended-length cartridges, 340 Mbytes (680 Mbytes with compression). The drive is based on the QIC 3010 minicartridge standard and reads QIC-40 and -80 and Irwin-formatted tapes. The \$399 Tape510 Internal plugs into a floppy-disk controller. The \$599 Tape510 parallel port uses an IEEE 1284 parallel port. Iomega Corp, Roy, UT. (801) 778-1000.

Circle No. 384

PCMCIA fax/modem card operates at 28.8 kbps.

The ST288VFC V.FAST-compatible PCMCIA fax/modem card operates at 28.8 kbps for data and 14.4 kbps for fax. With V.42bis data compression, throughput is equivalent to 115.2 kbps. An ultra-low-power sleep mode extends battery life in mobile applications. The cards comply with V.42 and V.42bis CCITT standards. Phone-line circuitry is built into the card, which comes with a telephone cable. \$499. Smart Modular Technologies, Fremont, CA. (510) 623-1231.

Circle No. 385

PCMCIA SCSI card features plug-and-play and hot-swapping.

The 16-bit RT7000 PCMCIA SCSI card is compatible with most SCSI peripherals and operates in any PCMCIA I type II or III slot. Plug-and-play capability and autoconfiguration make the card easy to install, according to the vendor. The card includes peripheral support for SCSI devices and comes with a 33-pin PCMCIA to 50-pin high-density SCSI-2 cable. \$220. Rancho Technology Inc, Rancho Cucamonga, CA. (909) 987-3966.

Circle No. 386

DSP card has CD-quality audio. The Ambassador DSP-based audio card adds CD-quality audio to the Spectrum Envoy line of telephony board products. Based on IBM's MDS2780 chip, the card has 16-bit stereo sound, CD-ROM interface, Sound Blaster compatibility, and plug-and-play installation. \$100 (OEM). Spectrum Signal Processing Inc, Burnaby, BC, Canada. (604) 421-5422.

Circle No. 387



Quadruple-speed CD-ROM recorder makes CDs in 15 minutes. The CDR4x CD-ROM recorder is a half-height SCSI unit that installs either inside or outside computer systems. PC and Macintosh configurations cost \$5995 and include DiscMaker pre-mastering and mastering software. Unix configurations cost \$7495. DataDisc Inc, Gainesville, VA. (703) 347-2111.

Circle No. 388

Adapter lets you run a Type III PCMCIA device in a Type I or II slot. All PCMCIA card devices that conform to the Type III specification, such as hard drives and global positioning systems, may be used with the adapter. \$49. Greystone Peripherals Inc, Los Gatos, CA. (408) 866-4739.

Circle No. 389

Flash memory cards offer execute-in-place system operation. The 2- to 10-Mbyte PCMCIA memory cards from Hitachi provide execute-in-place (XIP), an application program stored in the flash card that is executed directly from the card instead of being loaded into RAM. According to the com-

pany, this approach produces a smaller, faster, and more rugged system that operates longer on batteries. The 250-nsec, 2-Mbyte HB286116C-25 costs \$230 (500). Hitachi America Ltd, Semiconductor & IC Division, Brisbane, CA. (800) 285-1601, ext 16.

Circle No. 390

PCMCIA interface is available for the Sun SPARCstation. The S-Bus card accepts up to two Type II PCMCIA cards or one Type III PCMCIA card. \$295. Sun Microsystems Computer Corp, Mountain View, CA. (800) 821-4643.

Circle No. 391

PCMCIA-compliant card bay for PCI-local bus-based desktop computers. CardBay-PCI is an internal PC-card bay that allows PCI-based desktop computers to add up to four sockets for PCMCIA 2.0+ Type I, II, and III cards. The card bay may be used with a variety of PCMCIA cards, including SRAM, flash, I/O, hard-disk drive, and communications. The unit includes an onboard speaker for fax/modem applications and is designed for use with DOS 3.3 or Windows 3.0 or above operating systems. \$105 (100). Cardwell International Corp, Folsom, CA. (916) 985-1880.

Circle No. 392

Keyboards may be programmed to make any key a macro key. The Maxi Pro-II is a 124-key keyboard that lets you remap any key or use keys as macro keys to perform multikey functions. A utility included with the keyboard lets you display an image of the keyboard directly on the computer screen. The utility highlights any keys that have been remapped or are macros and shows their functions. \$40 (100). Maxi Switch Inc, Tucson, AZ. (602) 294-5450.


Circle No. 393

The next 12-bit ADC standard drives speed/power performance to new heights.



IT'S ACCURATE.
IT'S CRYSTAL.

THE CS5032 DELIVERS
500kHz FOR ONLY 55mW

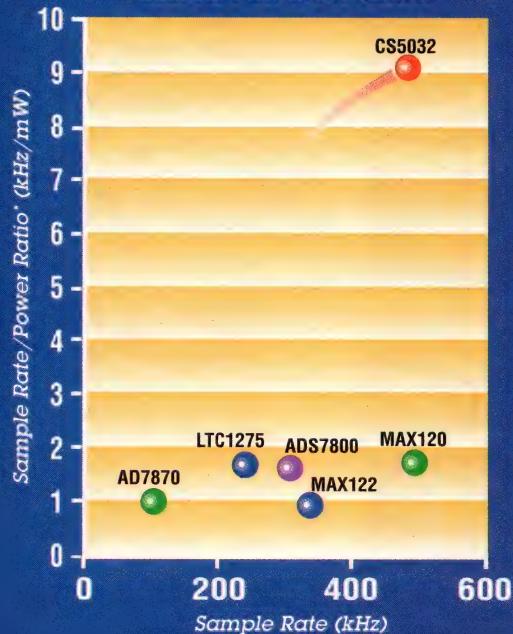

*Datasheet specifications for -55°C / 125°C

CRYSTAL
SEMICONDUCTOR CORPORATION

1-800-550-5030

CIRCLE NO. 65

Company	Page	Circle	Company	Page	Circle	Company	Page	Circle
AMP	9	47	Crystal Semiconductor	117	65	IO Tech	81-82	5
Advanced Micro Devices Inc	22-23		Cypress Semiconductor	C4		ITT Pomona Electronics	119	235
Advin Systems	121	230	Datel Inc	59	31	Incredible Technology	119	231
American Precision Industries	S14		Digi-Key Corp	1	1	Information Handling Services	124	38
Analog Devices Inc	S8-9		ESL Inc	97	66	Innovative Software Design Inc	121	236
	99-102		Eagle-Picher Industries Inc	118	85	Instrument Repair Lab	121	248
Analogic Corp	68	9	Ecliptec Corp	115	69	Integrated Device Technology	S21	
Belden Wire & Cable Co	C2	48	Elanix Inc	108	102	Intelligent Instrumentation	35-46	190-200
Burr-Brown Corp	57	26-30	Electro Automatic Corp	18 A-F				111 77
CEIBO	120	237	Electronic Designs Inc	19	32			120 232
Cermek Microelectronics	121	247	Epson America Inc	104	75	International Rectifier	C3	78
Coilcraft	S23		Fluke Corp	15	36	Linear Technology Corp	70	79
Compugetics Inc	34	49	GE Rental/Lease	65	76			71-72
Condor D.C. Power Supplies	55	64	Harris Semiconductor	29	37	Link Instruments	120	233
			Hewlett-Packard	33	86	Maxim Integrated Products Inc	77	80
							79	81
						Metalink Corp	121	234
						Micro Crystal, Div. of ETA SA	34	82
						MicroSim Corp	13	150-152
						Mini-Circuits	3	83
							75	84
						Mitsubishi Electronics America Inc	S*C4	
						Murata Electronics	10	87
						NCI	120	238
						NCR Corp	20	88
						National Instruments	48-49	204-205
						National Semiconductor	50-51	
						Nohau Corp	119	239
						Philips Semiconductor	S7	
							17	
							31	
							103	
						Pico Electronics	62	89
							116	89
						Picher International	112	91
						Power Trends	69	39
						Safe Soft Systems	121	240
						Samsung Semiconductor Inc	84-85	92
							86-87	93
						Sierra Circuits	119	241
						Siliconix	2	
						Stanford Research Systems	88	103
						Tech Tools	121	242
						Tektronix Inc	67	94
						Texas Instruments	6-7	95
						Tribal Microsystems	119	243
						Unitrode Integrated Circuits	S13	
							52	46
						Vicor Corp	S19	
							61	105
							83	106
						Viewlogic Systems	95	96
						Wavetek	47	97
						Wintek Corp	121	244
						Wintriss Engineering	121	245
						Wolfram Research Inc	109	107
						Z-Communications	S*C3	
						Zworld Engineering	119	246
						Recruitment Advertising	122-123	

No One Is In
Better Shape
To Supply Your
Lithium Batteries
Than We Are!

For more information on how we can fit your circuit board space, no matter how limited, call Eagle-Picher now.

EAGLE  **PICHER**

COMMERCIAL PRODUCTS DEPARTMENT
PO Box 180 Seneca, MO 64865 PH 417-776-2256 FAX 417-776-2257

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.

EDN

PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number
for additional information from manufacturers.

PROTO EXPRESS

*Best Value in the World
for*

POLYIMIDE & FR4
1 to 5 DAY TURN

1 to 12 Layers

PRINTED CIRCUIT PROTOTYPES

2 PIECE PRICES FOR FRC .062 Th.

LAYERS	1	2	3&4	5&6	7&8
SQUARE	15	\$233	\$292	\$639	\$787
INCH	30	264	330	724	891
UP TO	60	311	389	853	1049
TO	90	358	448	980	1207
	120	385	486	1044	1311
				1559	

5 PIECES x 1.34 ■ 5 DAY PRICES ABOVE

10 PIECES x 1.67 ■ UL LISTED

EXTRAS	CAPABILITIES	DISCOUNTS
Photo Plotting	Buried & Blind Vias	■
Testing	Polyimide Multilayer	■
Gold Contacts - \$50	Full Body Gold	5%
25% - Below 8 Mil Hole	Carbon Paste	
- Below 15 Mil Hole	Tin nickel burn-in boards	
SMOBC & LPI - \$50	SMT-SMOBC	
	Up to 22 layers	■ COD
	Impedance control boards	10%

FOR MORE INFORMATION CALL OR FAX

Ken Bahl ■ 1108 W. Evelyn Ave., Sunnyvale, CA 94086
Phone (408) 735-7137 FAX (408) 735-1408 Modem (408) 735-9842

CIRCLE NO. 241

ROM-IT

EPROM EMULATION SYSTEM



The Most Flexible
EPROM Emulator
You Can Get Today

- Emulates up to eight 4-Megabit EPROMs through one standard serial port.
- Downloads 2-Megabit programs in less than 23 seconds.
- Examine and modify individual bytes or blocks.
- Accepts Intel Hex, Motorola S-Record and binary files.
- Software available for IBM PC and compatibles.
- Base 27256 EPROM System \$395.00. Other configurations available.



Incredible Technologies, Inc.
Visa, Mastercard and American Express Accepted

Order Now - It's Easy
Call (708) 870-7027 Or Fax (708) 870-0120
For More Information

CIRCLE NO. 231



See EEM
93/94 Pgs.
D1304-1309

- Rental and 10-day trials available.
- Full Source-level Debugger with complete C-variable support.
- Supports virtually all members of the 8051, 80C196, 68HC11, 68HC16 and 68300 families.

CALL OR WRITE FOR FREE DEMO DISK!


NOHAU
CORPORATION

51 E. Campbell Ave.
Campbell, CA 95008
FAX (408) 378-7869
TEL (408) 866-1820

Call 408-378-2912
Nohai's 24-hour
information center to
receive info via your FAX

CIRCLE NO. 239

UNIVERSAL/GANG PROGRAMMERS

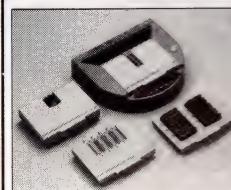

FLEX-700
48 pin from \$945
40 pin from \$845
8 gang from \$845
TUP-400 \$645
TUP-300 \$495

Appreciated by over 70,000 users worldwide


- Supports Altera 7xxx, MACH 435, Xilinx, Intel FX7xxx, nearly all FPGA/CPLD/PLD...
- Support EPROM, 28/29 flash, serial PROM, PSD4XX/5XX, Intel/Motorola/NEC/Hitachi MPU devices. Over 3,000 devices supported.
- Test TTL 74/40/45 series, DRAM(SIP/SIMM), and SRAM. EPROM EMULATION option.
- Gang programming & stand alone option.
- Universal 44,68 pin PLCC modules.

Tribal Microsystems Inc.
44388 S. GRIMMER BLVD., FREMONT, CA 94538
Tel: (510) 623-8859
Fax: (510) 623-9925



CIRCLE NO. 243

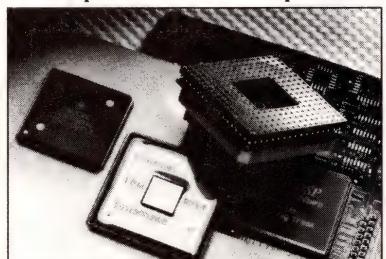ITT Pomona Test Clip Series For 240-pin MC68360 Microprocessors



ITT Pomona has announced the new model 5968 Test Clip designed to access all pins of Motorola's latest 68360, 240-pin microprocessor. For use with TI's DSP chip, the Model 5978 also includes a 240-pin test clip with PGA top-side interface. For user interface options, two additional models, 5891 and 5891-2, provide a PCB interface with high density cable headers. For technical assistance, specifications and model pricing and delivery, call (909) 469-2912.


ITT POMONA ELECTRONICS

1500 E. Ninth St., Pomona, CA 91766-3835
Phone (909) 469-2900 FAX (909) 629-3317

CIRCLE NO. 235

Our new Z104™,
a low-cost, general-
purpose controller,
can be the heart of
your next project.

Quickly develop
C-language programs
using our integrated
development system.

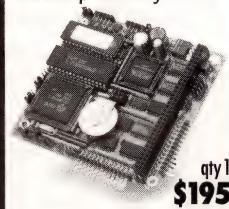

qty 1
\$195



PC/104 Bus
Power Supply
Real-Time Clock
RS485/RS232
Parallel I/O
Printer Port

Call for details!
916-757-3737 or
FAX 916-753-5141.
24-Hour AutoFAX:
Call 916-753-0618
from your FAX. Ask
for catalog 18.



CIRCLE NO. 246

To advertise in Product Mart, call Joanne Dorian, 212-463-6415

A Complete Line of Development Boards, Programmers and In-Circuit Emulators

NEW...NEW...NEW...NEW...

DS-186 - In-Circuit Emulator for 80C186/8/XL/EA/EB/EC, V40/50 8086/8 and other µCs

*** NEW ADDRESS IN THE USA ***

Call today for your free demo and software update


Toll Free: 1-800-833-4084

CEIBO

7 EDGESTONE CT.
FLORISSANT, MO 63033
TEL: 314-830-4084
FAX: 314-830-4083

CIRCLE NO. 237

48 Channel 50MHz Logic Analyzer

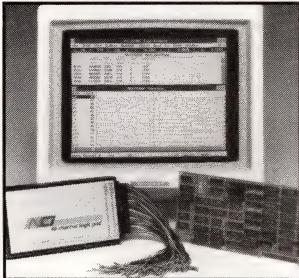

Complete System \$1695.00


New Windows 3.1 Compatible Software

- 48 Chnnls @ 50 MHz 4K words deep
- 16 Trigger Words/16Level Trigger Sequence
- Storage and recall of traces/setups to disk
- Disassemblers available for: 68000, 8088, 8086, 6801, 6811, Z80, 8085, 6502, 6809, 6303, 8031, 64180

NCI □ 6438 UNIVERSITY DRIVE,
HUNTSVILLE, AL 35806
(205) 837-6667 FAX (205) 837-5221

CIRCLE NO. 238

LOW-COST DATA ACQUISITION BOARDS

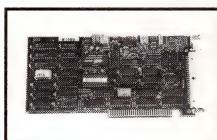

PCI-20428W. Because Your Customers Expect More for Less.


- OEM Pricing: from \$249 (100's)
- 16SE/8Diff Analog Inputs, 100kHz (DMA)
- Gains (1), (1, 2, 4, 8) or (1, 10, 100)
- 2 Analog Outputs, 100kHz (DMA optional)
- 1 Counter/Timer; 2 Rate Generators
- 8 Digital Inputs, 8 Digital Outputs

(800) 685-9911  **INTELLIGENT INSTRUMENTATION™**
Fax: (602) 573-0522
6550 S. Bay Colony Dr., MS130 • Tucson, AZ 85706

CIRCLE NO. 232

200MSa/s

Digital Oscilloscope

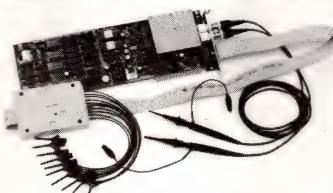


- 200 MSa/s Sampling Rate
- up to 128K Samples/Channel
- PC-BASED INSTRUMENT
- 2 Analog Channels (2 ch. Oscilloscope)
- 8 Digital Channels (8 ch. Logic Analyzer)
- All 10 channels can be used at same time
- Simultaneous use of all 10 channels
- Cross Triggering of Digital and Analog
- 125 MHz Single Shot Bandwidth

\$1799 DSO-28200 (200MSa/s, 4K/Ch)

\$2285 DSO-28264 (200MSa/s, 128K/Ch)

400 MHz

Logic Analyzer

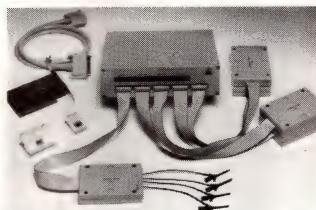

- up to 128 Channels
- up to 400 MHz
- up to 16K Samples/Channel
- Variable Threshold
- 8 External Clocks
- 16 Level Triggering
- Pattern Generator (Option)

\$1299 - LA32200 (200 MHz, 32 Ch) Pods & Software

\$1899 - LA32400 (400 MHz, 32 Ch) included

Also Available:

\$799 - LA12100 (100 MHz, 24 Ch, TTL only)

Universal

Programmer

PAL - GAL - MICRO
EPROM - EEPROM - FLASH



\$475

Call for full device support list

Free software updates on BBS

Call (201) 808-8990

 **Link Instruments**

369 Passaic Ave, #100, Fairfield, NJ 07004 fax: 808-8786

CIRCLE NO. 233

CIRCLE NO. 233

To advertise in Product Mart, call Joanne Dorian, 212-463-6415

Looking for BIG results?

Getting lost in the crowd?

Find out how you can break through the clutter to get big results for a small price, by placing a 4-color ad in EDN Product Mart. Call Joanne Dorian at (212) 463-6415 for details.

This DSP System will help get your new product to market fast.

Blazing-fast, PC-based Turbo C30-II Real-Time DSP Development Board gives you the tools (like TI TMS320C30 32-bit DSP; up to 2MB Dual Access, 0 wait state memory; 4.2MB/sec data transfer; TI & Tartan C/C++ software; and more)—and industry-leading engineering services provide support—for quick product design.

Turbo C30-II
& Prototyping Boards

Call
800-550-7302
for details.



CIRCLE NO. 245

REMOVE HARDWARE LOCKS

PROTECT YOUR INVESTMENT! MAINTAIN PRODUCTIVITY!

Software utility that allows for the removal of hardware locks.

Available for most major
CAD/CAM and PCB
software programs

Easy - Simple - Guaranteed

Programs start at \$99.00 U.S.

Visa and Mastercard Welcome
Call or Fax for more information

SafeSoft Systems Inc.
201-1111 Munroe Ave.
Winnipeg, MB R2K 3Z5
Canada

Phone (204) 669-4639
FAX (204) 668-3566

CIRCLE NO. 240

FLEXIBLE Memory EMULATORS



- 90 day WARRANTY.
- 10 day MONEY-BACK GUARANTEE.
- Supports Read and WRITE access by TARGET.
- Download and VERIFY from HOST.
- View/Edit SRAM contents while target is running.
- Full screen ASCII/HEX editor included.
- Libraries provide high level access to emulator.
- Daisy-chain up to 4 units for multi-EPROM targets.
- Field upgradable to 4Mbit (27040) emulation.
- Battery back-up, PLCC and 16bit adapters available.

TechTools
(214) 272-9392
FAX: 494-5814

Models start at
\$129

CIRCLE NO. 242

Advin



PILOT-U84 Universal Programmer #1 in New Device Support & Expandability

Altera 7064, 7128, 7160, 7192 in 84-, 100- and 160-pin packages
Xilinx 1765D, 17128 etc Intel FLEX, 87C196 KC, KD, JR, MC etc.
Motorola 68HC711, 68HC705, WSI PSD-3XX, -4XX, -5XX, PAC, SAM
Atmel 29C040, ATF22V10 etc. AMD MACH32, 29F040, etc
Lattice pLSI-1000, 2000, -3000, Microchip PIC micros
All packages to 256-pin: PLCC, PGA, QFP, TQFP, TSOP, SOIC
800-627-2456 FAX:(408) 736-2503, Sunnyvale, CA.

CIRCLE NO. 230

8051 68HC11 COP8 68HC05

iceMASTER® In-Circuit Emulators From \$851

- Easy to learn & use
- Windowed interface
- User configurable
- Real-time and non-intrusive
- Source level debug
- Support for structures, arrays, unions and pointers
- Trace buffer with advanced searching capabilities
- Fast serial (RS-232) link to any PC, even laptops
- Broad support of derivative devices/interchangeable probe cards
- Rental and 10-day trials available
- Call today for free demo disk

(800) 638-2423

New
DS80C320
8x51Fx
8xC575

MetaLink
Corporation

Phone: (602) 926-0797
Fax (602) 926-1198

MetaLink Europe GmbH
Telefon: (08091) 2046
TeleFax (08091) 2386

CIRCLE NO. 234

LOW PROFILE MODEM DAA



NEW
IMPROVED

CH1817L

- Low Power
- AC Noise Filter
- Caller I.D. Option
- 0.3" H x 1.0" x 1.0"
- UL 1459 Approved
- FCC Part 68 and DOC Approvable
- Compatible with all modem & Fax chip sets, including V.32

Your Source for Modem Components

Cermek
microelectronics

Tel: 408-752-5000
Fax: 408-752-5004

Cermek Microelectronics, Inc.
1308 Borregas Ave. • Sunnyvale, CA 94089

CIRCLE NO. 247

STRETCH YOUR BUDGET

FLUKE
TEK
HP

YOUR SOURCE FOR
USED, REFURBISHED,
CALIBRATED EQUIPMENT.


All Equipment is
Guaranteed to Meet
Manufacturers Specs.

Popular Models of Scopes, Analyzers,
Meters, Power Supplies and More...

PHONE TOLL FREE
1-800-345-6140
INSTRUMENT REPAIR LABS INC.
(303) 469-5375 • 2100 West 6th Ave. • Broomfield, CO 80020

CIRCLE NO. 248

Relex Reliability Software

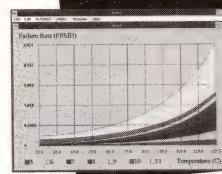

Mac!
DOS!
Windows!

Relex Reliability Software, long known for its power and flexibility, is now available for Windows, the Mac, and DOS! With features such as a powerful CAD interface, system modeling, impressive graphics, and unmatched user-friendliness, Relex is the ultimate, intuitive solution!

- MIL-HDBK-217
- Bellcore • Parts Count
- Mechanical • CNET • FMECA • more •

Call 410-788-9000 Today for a Free Demo!


INNOVATIVE SOFTWARE DESIGNS, INC.

Two English Elm Court
Baltimore, MD 21228 USA
410-788-9000
FAX 410-788-9001

CIRCLE NO. 236

HiWIRE II

Schematic and PCB Software

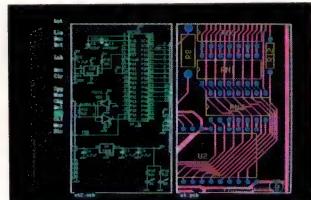

With support for expanded and extended memory, HiWIRE II can handle your most demanding schematic and PCB designs. The unique HiWIRE II editor allows you to display and edit schematics and PCBs simultaneously, using the same commands for each. HiWIRE II is \$995 and is guaranteed.

WINTEK®

Wintek Corporation
1801 South Street
Lafayette, IN 47904
Phone: (317) 446-1903

1 - 8 0 0 - 7 4 2 - 6 8 0 9

CIRCLE NO. 244

To advertise in Product Mart, call Joanne Dorian, 212-463-6415

EDN September 29, 1994 • 121

Engineers

JOIN AN ESTABLISHED LEADER

Engineers

Be a part of a successful team meeting new challenges with state-of-the-art technology. For immediate confidential consideration, fax your resume to 813/381-2000 x 4803 or forward your resume and salary history indicating position of interest to:

*Manager of Staffing
E-Systems, Inc. ECI Division
P.O. Box 12248
St. Petersburg, FL 33733-2248*

E-Systems, ECI Division, located in St. Petersburg, FL, designs, develops, and produces a variety of communications systems for air, land, sea and space applications. We have attained our leading position in the industry through the excellence of our products and people.

Systems Engineers

- BSEE or MSEE; at least 10 years' experience
- Combat/weapon systems integration
- Detection, decision and engagement logic/integration

Digital Engineer

- BSEE or MSEE; at least 3 years' experience
- Knowledge of VME, PALS, FPGAs, and microprocessors
- CADENCE VHDL design tools

Software Engineer

- BSCS/MSCS; at least 3 years' experience
- ADA, C
- Software Methodology

RF/Microwave Engineer

- BSEE or MSEE; at least 3 years' experience
- 2 to 40 GHz
- HP MDS or EESOF CAD systems

Power Converter Engineer

- BSEE or MSEE; at least 3 years' experience
- Design of high and low voltage power converters
- P-Spice

Mechanical Engineer

- BSME or MSEE; at least 5 years' experience
- PRO-Engineer, SDRC, RASNA, ANSYS
- Military electronics packaging

Maintainability Engineer

- BSEE; at least 5 years' experience
- Analysis/BIT design-FOM, FMEA or WSTA, STAT
- Generate test requirements documents and TPS
LEXYS, PAWS

We offer a highly competitive compensation and benefits package that includes comprehensive medical, tuition reimbursement and retirement.



An Equal Opportunity Employer M/F/D/V. U.S. Citizenship Required.

WHAT HAPPENS WHEN YOU DON'T ADVERTISE?

nothing!

If you want to reach over 163,000 engineering professionals, in over 52,000 locations, EDN Career Opportunities is the best place to advertise your positions.

Get the attention of 100% qualified engineers and managers involved in designing or developing electronic products, who look to EDN Magazine's Classified section for career opportunities.

Trish Kennefick
Tel: 1-800-603-4859
Fax: 1-617-630-3925

Position available for Electronics Design Engineer. The position involves the design of electronic circuitry and software systems for utility locating and directional boring equipment including beacons, transmitters, and receivers. Develops concepts for new products, circuits, programming, etc. Develops assembly-level language software to operate and control our digital signal processing receiver and transmitter products. Directs the construction of prototypes. Modifies prototype systems as needed. Masters degree in Electrical Engineering required. One year experience required in job offered or electrical engineering, 45 hours per week, Monday through Friday, 7:00 a.m. til 5:00 p.m. Salary of \$755.00 per week. Send resume to Oklahoma State Employment Service, Job Order #125881, 1201 W. Grand Ave., Ponca City, OK 74601 (ID# 3600)

Without Tears™

COMING TO A CITY NEAR YOU


Washington, DC
Austin, TX San Jose
Scottsdale, AZ
Atlanta Denver
Long Beach, CA

Learn DSP and
put your
knowledge to
work
IMMEDIATELY!

Call 7. Domain Technologies, Inc.

800-967-5034
404-587-4812

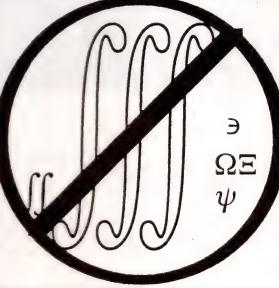Hours 9-5 EST.
Ask for a brochure.
Our 2-Day Advanced
Course is ready. Call for
more info.



By taking this
3-Day Course
you will really
learn DSP.
Guaranteed!

IOWA MIDWEST

RF/TELECOM

WIRELESS

NEBRASKA-MINNESOTA-ILLINOIS
I have immediate openings for Design Engineers and Technical Project Managers with BS/MS plus 3 to 10 years RF/Radio design experience in any of the following areas: RF circuit design (100 MHz to 3.0 GHz), Receivers, Transmitter Exciters, Low-noise Frequency Synthesizers, Power Amplifiers, Spread Spectrum Modulation, Digital Radio DSP. These positions are all with top non-defense companies in good Upper-Midwest locations

DON GALLAGHER, MSEE

Gallagher & Brei Associates
1145 Linn Ridge Rd., Mount Vernon, IA 52314
(319) 895-8042 • Fax (319) 895-6455

PROFESSIONAL SERVICES

PRODUCT ENGINEERING & MFG., INC.

Over 25 Years Experience in
Complete Mechanical Services

- Industrial Design & Rendering
- Enclosure Design
- Mechanism Design
- Reverse Engineering
- Product Evaluation
- Prototyping

From hand held Plastic Products...
.....Too Complete Machines

CALL FOR BROCHURE
Virginia 1-800-848-2553

EDN

MAGAZINE

1994 Editorial Calendar and Planning Guide

ISSUE DATE	AD DEADLINE	EDITORIAL FOCUS & FEATURES
October 13	September 14	• Portable Equipment Design • PLDs • FPGAs
October 27	September 28	• Digital Signal Processing • Embedded Tool
November 10	October 12	• Computer & Peripherals • A/D-D/A Convention
November 24	October 26	• Quality in Design • Connectors • H/W & S/W
December 8	November 9	• Top 100 Hot Products • Monitors & Display
December 22	November 23	• Hot Technologies of 94 • Economic Outlook

For more information, call Trish Kennefick at 1-800-603-4859

GREAT ALONE. BETTER TOGETHER.

Introducing CAPS^{Xpert}.® The best of two component databases combined into one Windows™ tool.


Some of the finest things in life result from ideal combinations. When IHS® wanted to create the world's most

powerful component selection tool, we combined the strengths of CAPS and

IC/Discrete with the functionality of Windows to bring you the ultimate — CAPS^{Xpert}.


CAPS^{Xpert} will revolutionize the way you search and compare components. CAPS^{Xpert} gives you:

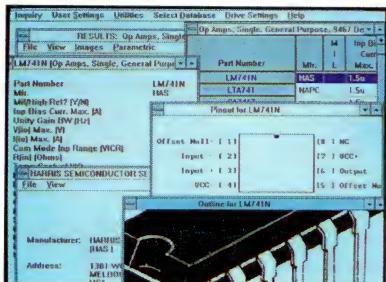- More data • Unbeatable currency
- User-defined upgrade and downgrade criteria • Graphical pinout and package



displays • Distributor and sales office listings. Innovative search commands and multiple window capabilities make finding the current information your engineering team needs faster and easier than ever before. CAPS^{Xpert} is the tool you need to reduce redesign costs, avoid expensive product delays, and meet critical design cycles.

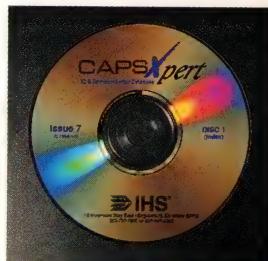
For the ultimate solution to faster, easier component selection, upgrade to CAPS^{Xpert} today! Call 1-800-241-7824 or 303-790-0600, ext. 59.



 **IHS**®

CAPS^{Xpert}. Nobody Puts It Together Like IHS.®

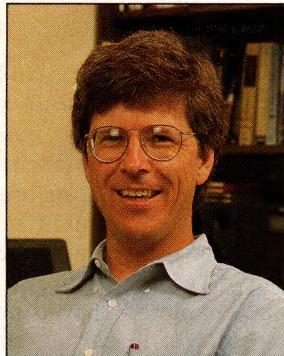Available in Windows for PCs and network configurations. Call for UNIX update.



JACK GANSSLE,
EMBEDDED-SYSTEMS
CONTRIBUTING EDITOR

Troubleshooting

Avoiding the bog

There comes a time in any project when your new design is finally assembled, awaiting your special expertise to "make it work." Sometimes, it seems like the design end of this business is the easy part; troubleshooting prototype hardware can make even the toughest engineer a Maalox addict.

You can't fix any embedded system without the right world view—suspicion tempered with trust in the laws of physics, curiosity dulled only by the determination to stay focused on a single problem, and a zealot's regard for the scientific method.

Perhaps these are successful characteristics of all who pursue the truth. In a world that surrounds us with complexity, we deal daily with equipment and systems we only half understand. So, it seems wise to follow understanding by an iterative loop of focus, hypothesis, and experiment.

Too many engineers fall in love with their creations, only to be continually blindsided by the design's faults. They are quick to assume, overtly or subconsciously, that the problem is due to the software, the lousy chips, or the power company, when simple experience teaches us that any new design is rife with bugs.

Assume it's broken. Never figure anything is working right until proven by repeated experiment; even then, continue to view with suspicion the "fact" that it seems to work. Bugs are not bad; they're merely a test of your troubleshooting ability.

Armed with a healthy skeptical attitude, the basic philosophy of debugging any system is to complete the following steps:

For (i=0; i < # findable bugs; i++)

```
{
  while (bug(i))
```

```
{
```

Observe the behavior to find the apparent bug;

Observe collateral behavior to gain as much information as possible about the bug;

Round up the usual suspects;

Generate a hypothesis;

Generate an experiment to test the hypothesis;

Fix the bug;

```
};
```

```
};
```

Now, you're ready to start troubleshoot-

ing, right? Wrong! Stop a minute and make sure you have good access to the system. No matter how minor the problem seems to be, troubleshooting is like a bog where we all get trapped for far too long. Take a minute to ease your access to the system.

Do you have extender cards if they're needed to scope any point on the boards? How about special long cables to reach the boards once they are extended?

If there's no convenient point to *reliably* scope on the scope's ground lead, solder a resistor lead onto the board, so that you're not fumbling with leads that keep popping off.

Some systems have signals that regulate major operating modes. Solder a resistor lead on these points as well, because you'll need to scope them at some point. This small investment in time up front will pay off in spades later.

Following the loop

Let's cover each step of the troubleshooting sequence in detail:

Step 1: Observe the behavior to find the apparent bug. In other words, determine the bug's symptoms. Remember that many problems are subtle and exhibit themselves via a confusing set of symptoms. The fact that the first digit of the LCD fails to display may not be a useful symptom—but the fact that none of the digits work may mean a lot.

Step 2: Observe collateral behavior to gain as much information as possible about the bug. For example, does the LCD's problem correlate to a relay's clicking in? Avoid studying a bug in isolation but beware of trying to fix too many bugs at once. Address such problems as ROM accesses' unreliability and a not-bright-enough front-panel display one at a time. No one is smart enough to deal with multiple bugs all at once, unless they are all manifestations of something more fundamental.

Step 3: Round up the usual suspects. In other words, many computer problems stem from the same few sources. Clocks must be stable and meet specific timing and electrical specs, or all bets are off. Reset too often has unusual timing parameters. When things are just "weird," take a minute to scope all critical inputs to the µP, such as clock, hold, ready, and reset.

Always remember to check V_{cc}. Time and

time again at Softaid, we see systems that don't run right because the 5V supply is putting out only 4.5 or 5.6V, or 5V with lots of ripple. The systems come in after their designers have spent weeks sweating over some obscure problem that, in fact, never existed, but was simply the specter of the more profound power-supply issue.

Step 4: Generate a hypothesis. Don't be like "shotgunners," those poor fools who address problems by simply changing things—ICs, designs, PLD equations—with no rationale for the changes. Shotgunning is for amateurs. It has no place in a professional engineering lab.

Before changing things, formulate a hypothesis about the cause of the bug. You probably don't have the information to do this without gathering more data. Use a scope, an emulator, or logic analyzer to see exactly what is going on; compare that with what you think *should* happen. Generate a theory about the cause of the bug from the difference in these.

Sometimes, you have no clue to what the problem is. Scoping the logical places might not generate much information. Or, a grand failure, such as an inability to boot, occurs that is so systemic that it's hard to tell where to start looking. When desperation sets in, it's worthwhile to scope around the board practically at random. You might find a floating line, an unconnected ground pin, or something unexpected. Scope around, but always be on the prowl for a working hypothesis.

Step 5: Generate an experiment to test the hypothesis. Most of the time, you can resolve this step when gathering data to come up with the theory in the first place. For example, if an emulator reads all ones from a programmed ROM, a reasonable hypothesis is that CS or OE isn't toggling. Scoping the pins proves this one way or the other, but requires you to formulate another hypothesis and experiment to figure out why the selects are not where you expect to see them.

Sometimes, though, you should apply the hypothesis-experiment model more formally. When we first started to use Intel's XL version of the 186 (supposedly compatible with the older series), none of our systems worked. Scoping around showed the

processor to be stuck in a weird tristate, although all of its inputs seemed reasonable. One hypothesis was that the 186XL was not properly coming out of reset, a hard thing to capture because reset is basically a nonscopable, one-time event. We finally built a system to reset the processor repeatedly, giving us something to scope. The experiment proved the hypothesis, and a fix was easy to design.

It's much faster to think out the change than to implement it and perhaps troubleshoot it over again.

An alternative would have been to glue in a new reset circuit at the beginning to see if the problem would go away. Problems that mysteriously go away tend to mysteriously come back; unless you can prove that the change *really* fixed the problem, there may still be a time bomb lurking in the system.

Occasionally, a bug is too complicated to yield to such casual troubleshooting. If you have to adjust the timing of a PLD, visualize or draw the new timing before wildly making changes. Will it work? It's much faster to think out the change than to implement it and perhaps troubleshoot it over again.

Rapid troubleshooting is as important as accurate troubleshooting. Decide what your experiment will be and then stop and think it through again. What will this test prove? I like experiments with binary results: The signal is there, or it isn't; the signal meets specified timing, or it doesn't. Either result gives me a direction in which to proceed. Binary results have another benefit: They sometimes let you skip the experiment altogether. Always think through the actions you'll take *after* the experiment is complete, because sometimes you find yourself taking the same path, regardless of the result, making the experiment superfluous.

If the experiment is a nuisance to set up, is there a simpler approach? Hooking up 50 logic-analyzer probes is rather painful if you can get the same infor-

mation in an easier way. I'd hate to be in a lab without a logic analyzer because they're useful for so many things, but I try to relegate it to the tool of last resort, because you can often construct an easier experiment in a fraction of the time it takes to connect the logic analyzer.

Don't be so enamored of your new hypothesis that you miss data that might disprove it. The purpose of a hypothesis is simply to crystallize your thinking: If it's right, you'll know the step to take next. If it's wrong, collect more data to formulate yet another theory.

Step 6: Fix the bug. There's more than one way to fix a problem. Hanging a capacitor on a PLD output to skew it a few nanoseconds is one way; another is to adjust the design to avoid the race condition entirely.

Sometimes, a quick and dirty fix might be worthwhile to avoid getting hung up on one little point. Revisit the kludge and re-engineer it properly. Electronics have an unfortunate tendency to work in the engineering lab and not go wrong until the 5000th unit is built. If a fix feels bad, or if you have to furtively look over your shoulder and glue it in when no one is looking, then it's bad.

Finally, never fix the bug and assume it's OK because the symptom has disappeared. Apply a little common sense and scope the signals to make sure you haven't fixed the problem by creating a new one.


Some final advice

At 3:00 am, when the problems seem intractable and you're ready to give up engineering, remember that the system is only a computer. Never panic: You are smarter than it is.

Jack Ganssle is the president of Softaid, a vendor of emulators and other embedded-systems tools. His idea of heaven is sailing across oceans, although the ugly face of common sense precludes these dreams too often. He can be contacted via CompuServe at "76366.3333," or via Internet at "76366.3333@compuserve.com." For those users of the Pony Express, send mail c/o Softaid, 8310 Guilford Rd, Columbia, MD 21046.

Motor control savings.

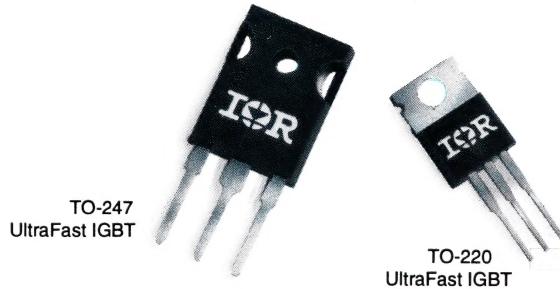Or how to design noise-free inverters
that switch faster for less money.
The 1200V IGBT *CoPack*.




Now you can design simpler, more efficient motor control inverters. That switch at 20kHz. Quietly. Without snubbers. All it takes is our UltraFast 1200V *CoPack* with built-in diode.

You cut system costs with less parts. Get the lowest conduction loss. Fastest switching speed. Short circuit withstand. And super-soft recovery. All from more than 200 IGBT part numbers.


Rated from a few amps up to 50 amps. And value-priced to save you money. Delivery? Right from stock. Call for data on today's most cost effective IGBT line. 310-322-3331, ext. 2529.

You'll save more than you think.

Available now at key IR distributors.

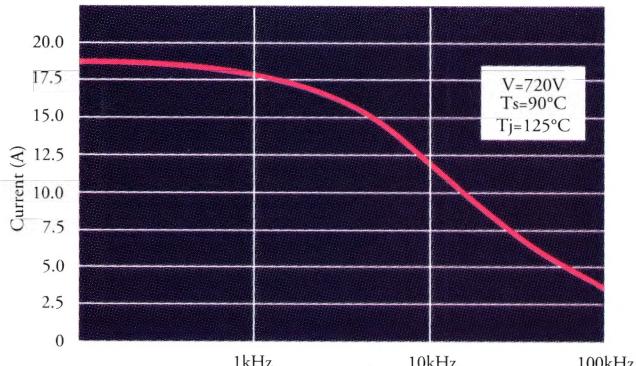

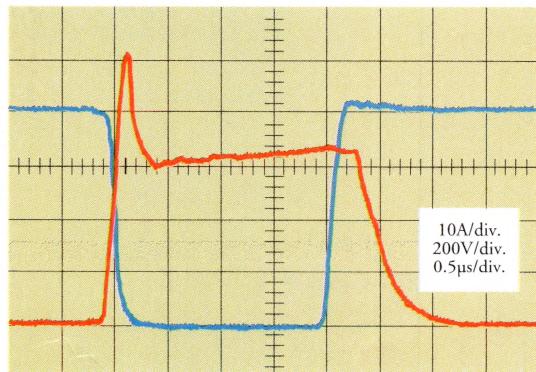Output current vs frequency for two IRGPH50KD2 in half-bridge, 50% duty cycle.



Switching waveforms of the IRGPH50KD2 in a clamped inductive load at Tj = 90°C.


IR International Rectifier

WORLD HEADQUARTERS: 233 KANSAS ST., EL SEGUNDO, CA 90245, USA 310-322-3331, FAX 310-322-3332, TELEX 66-4464. EUROPEAN HEADQUARTERS: HURST GREEN, OXTED, SURREY RH8 9BB, ENGLAND (0883) 713215, FAX (0883) 714234

HEXFET Power MOSFETs • IGBTs • Schottkys • Power ICs • SMDs • Modules • Rectifiers • SCR_s • Bridges

FOLD PAGE
HERE


TO
HERE

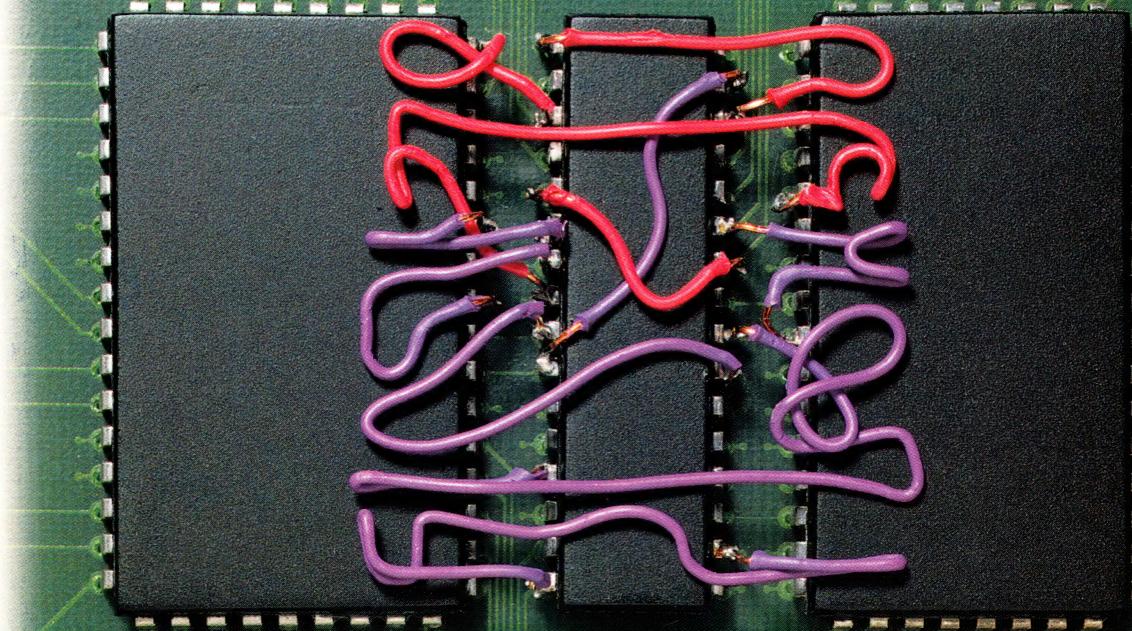

You found it! FLASH370 is a family of seven erasable complex PLDs—with up to a whopping 256 macrocells and 256 I/O pins. Even more remarkable is their 100% routability. This combines with the shortest pin-to-pin delays of any architecture through all speed paths—a blazing 8.5 ns for the 32-macrocell, 44-pin CY7C371. What's more, you get this high speed with 100% timing predictability. So you never have to struggle with variable timing again.

SURE, RECORD-BREAKING
SPEED IN A COMPLEX PLD IS A BIG PLUS
BUT IT SHOULDN'T
ROUTINELY BE A TEST OF YOUR ABILITY
TO HANDLE PLIERS.

(FOLD AS SHOWN FOR THE ALTERNATIVE.)

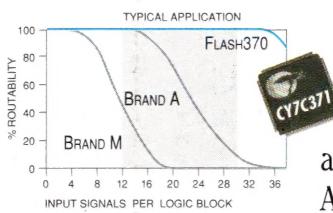

The FLASH370 family's exceptionally clean and simple architecture helps get your products to market faster. And as part of Cypress's comprehensive UltraLogic™ family, the FLASH370 is supported by *Warp*™ VHDL open design tools. So start designing with a data sheet instead of a soldering iron. And watch the competition fold.

Call for your free FLASH370 design kit: *Warp2*™ design tool for the CY7C371, sample certificate and product data. 1-800-858-1810*, Dept. C412.

*In Europe, fax requests to the above Dept. at (32) 2-652-1504 or call (32) 2-652-0270. In Asia, fax requests to the above Dept. at 1 (415) 940-4337. *Warp* and UltraLogic are trademarks of Cypress Semiconductor © 1994 Cypress Semiconductor, 3901 North First Street, San Jose, CA 95134 Phone 1-408-943-2600.

ULTRA
L O G I C

CYPRESS